



**Module-4**

- 7 a. Explain the working of JK master slave flip-flop with a sketch, truth table and symbol. (06 Marks)  
b. Give a brief account an flip flop as finite state machine. (05 Marks)  
c. Briefly describe about sequential logic circuit. (05 Marks)

**OR**

- 8 a. Enumerate different types of shift registers. Explain Serial In Serial Out (SISO) register. (06 Marks)  
b. Mention the applicators of shift registers. (05 Marks)  
c. Using behavioral model write verilog HDL code for a 'D' flipflop with reset input. (05 Marks)

**Module-5**

- 9 a. Explain digital clock with block diagram. (06 Marks)  
b. Design a 3 bit synchronous binary counter using JK flip flop. (05 Marks)  
c. Mention different types of A/D converters and test its specifications. (05 Marks)

**OR**

- 10 a. Explain binary weighted resistor D/A converter. Mention its drawbacks. (06 Marks)  
b. Describe about successive approximation type ADC. (05 Marks)  
c. What is the resolution of a 12 bit D/A converter which uses a binary ladder, if the full scale output is +10V? (05 Marks)

\* \* \* \* \*