

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define canonical minterm form and canonical maxterm form. (05 Marks)
- b. Compare between prime implicant and essential prime implicant. Identify all the prime implicants and essential prime implicants of the following functions using k-map :
 $f(a, b, c, d) = \pi_M (0, 2, 3, 8, 9, 10, 12, 14)$. (07 Marks)
- c. Simplify the following boolean function using k-map, and implement by logic gates.
 $f(A, B, C, D, E) = \sum_m (3, 7, 10, 11, 12, 13, 14, 15, 17, 19, 21, 23, 25, 27, 28, 29, 31) + \sum_d (2, 6, 26, 30)$ (08 Marks)

OR

- 2 a. Convert the given boolean function into minterm canonical form.
 $f(a, b, c) = (\bar{a} + b)(b + \bar{c})$. (05 Marks)
- b. Simplify the following boolean function using k-map
 $f(P, Q, R, S) = \sum_m (0, 2, 4, 5, 6, 8, 10, 15) + \sum_d (7, 13, 14)$. (07 Marks)
- c. Using Quine – McCluskey method, obtain a minimal SOP expression for
 $f(a, b, c, d) = \sum_m (2, 3, 4, 5, 13, 15) + \sum_d (8, 9, 10, 11)$. (08 Marks)

Module-2

- 3 a. Design two bit magnitude comparator and draw the logic diagram. (10 Marks)
- b. Write a short note on encoders. (05 Marks)
- c. Design full adder using two numbers of 4:1 MUX. (05 Marks)

OR

- 4 a. Explain look ahead carry adder. (10 Marks)
- b. Implement following multiple output function using IC74138 and external gates.
 $F_1 (A, B, C) = \sum_m (1, 4, 5, 7)$ and $F_2 (A, B, C) = \pi_m (2, 3, 6, 7)$. (05 Marks)
- c. Design 16:1 multiplexer using 8:1 MUX. (05 Marks)

Module-3

- 5 a. Explain the working of master slave JK flip-flops with functional table and timing diagram. Show how race around condition is overcome. (08 Marks)
- b. Obtain characteristic equation of SR flip-flop. (05 Marks)
- c. Explain working of 3-bit binary ripple counter with the suitable logic and timing diagram. (07 Marks)

OR

- 6 a. Convert JK flip-flop to D flip flop. (05 Marks)
- b. Explain the 4 modes of operation of shift register with suitable logic diagram and truth table. (08 Marks)
- c. Design MOD – 6 synchronous counter using D flip-flop. (07 Marks)

Module-4

- 7 a. Analyze the following sequential circuit given in Fig Q7(a) and obtain excitation, transition and state table. Also write the state diagram.

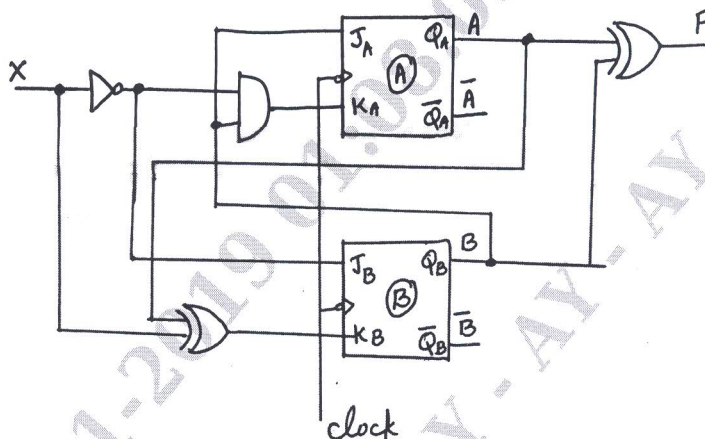


Fig Q7(a)

(12 Marks)

- b. Design a synchronous counter with the sequence 0, 1, 3, 7, 6, 4, 0 using JK flip-flop. (08 Marks)

OR

- 8 a. Design a clocked sequential circuit that operates according to the state diagram shown in Fig Q8 (a) implement the circuit using D flip flop.

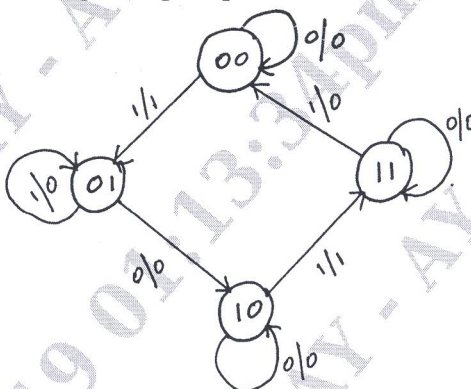


Fig Q8(a)

(12 Marks)

- b. With the help of block diagram explain Mealy and Moore model in a sequential circuit analysis. Give the example circuits. (08 Marks)

Module-5

- 9 a. Write the comparison between VHDL and verilog. (08 Marks)
 b. Explain the various data types available in VHDL. (06 Marks)
 c. Write HDL code of a 2×1 multiplexer – VHDL. (06 Marks)

OR

- 10 a. Write a data flow description for a full adder with active high enable in both VHDL and verilog. (08 Marks)
 b. Explain shift and rotate operators in HDL with an example. (08 Marks)
 c. Explain the structure of verilog module. (04 Marks)
