

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC33

## Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Analog Electronics

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Derive an expression for input impedance, output impedance, voltage gain and current gain of un bypassed RE common emitter amplifier using  $r_e$  model. (10 Marks)
- b. For the network of Fig.Q1(b), determine : i)  $r_e$  ii)  $Z_i$  iii)  $Z_o$ , ( $r_o = \infty\Omega$ ) iv)  $A_V(r_o = \infty\Omega)$  v) the parameters of parts ii through iv if  $r_o = 50K\Omega$  for  $R_1 = 56K\Omega$ ,  $R_2 = 8.2K\Omega$ ,  $C_1 = 10\mu f$ ,  $C_2 = 10\mu f$ ,  $R_E = 1.5K\Omega$ ,  $C_E = 20\mu f$ ,  $R_C = 6.8K\Omega$ ,  $\beta = 90$  and  $V_{CC} = 22V$ . (10 Marks)

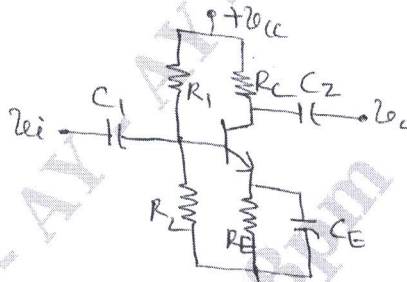


Fig.Q1(b)

**OR**

- 2 a. Derive an expression of input impedance, output impedance, voltage gain and current gain of fixed bias CE amplifier using h-parameter. (10 Marks)
- b. Determine  $r_e$ ,  $h_{fe}$ ,  $h_{ie}$ ,  $Z_i$ ,  $Z_o$ ,  $A_V$  and  $A_i$  for the circuit shown in Fig.Q2(b) using hybrid equivalent model. (10 Marks)

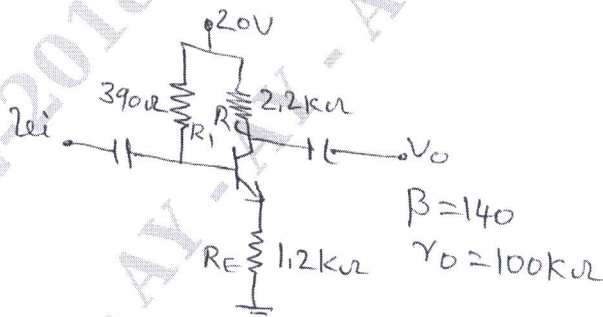


Fig.Q2(b)

### Module-2

- 3 a. Explain the working principle of JFET, and explain the transfer characteristics of JFET. (08 Marks)
- b. Derive an expression for input impedance, output impedance, voltage gain and current gain of fixed bias FET amplifier. (08 Marks)
- c. Distinguish between JFET and MOSFET. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 4 a. With neat diagram explain construction and working principle of n-channel depletion type MOSFET. (10 Marks)
- b. Derive an expression for input impedance, output impedance and voltage gain of common – Gate FET amplifier. (10 Marks)

**Module-3**

- 5 a. Derive an expression for low frequency response of BJT amplifier due to capacitors  $C_S$ ,  $C_E$  and  $C_C$ . (10 Marks)
- b. Determine the lower cutoff frequency for the network of Fig.Q5(b) using the following parameters  $C_i = 10\mu\text{f}$ ,  $C_E = 20\mu\text{f}$ ,  $C_C = 1\mu\text{f}$ ,  $R_S = 1\text{k}\Omega$ ,  $R_1 = 40\text{K}\Omega$ ,  $R_2 = 10\text{K}\Omega$ ,  $R_E = 2\text{K}\Omega$ ,  $R_C = 4\text{K}\Omega$ ,  $R_L = 2.2\text{K}\Omega$ ,  $\beta = 100$ ,  $r_o = \infty\Omega$  and  $V_{CC} = 20\text{V}$ , plot the response. (10 Marks)

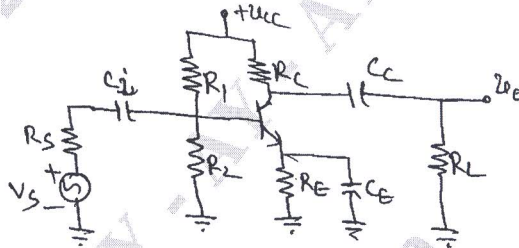


Fig.Q5(b)

OR

- 6 a. Define Miller's theorem, determine equivalent input and output capacitances of the circuit. (10 Marks)
- b. Determine the lower cutoff frequency for the network of Fig.Q6(b) using the following parameters.  $C_G = 0.01\mu\text{f}$ ,  $C_C = 0.5\mu\text{f}$ ,  $C_S = 2\mu\text{f}$ ,  $R_{\text{sig}} = 10\text{K}\Omega$ ,  $R_G = 1\text{M}\Omega$ ,  $R_0 = 4.7\text{K}\Omega$ ,  $R_S = 1\text{K}\Omega$ ,  $R_L = 2.2\text{K}\Omega$ ,  $I_{\text{DSS}} = 8\text{mA}$ ,  $V_P = -4\text{V}$ ,  $r_d = \infty\Omega$ ,  $V_{\text{DD}} = 20\text{V}$ ,  $V_{\text{GSQ}} = -2\text{V}$  and  $I_{\text{DQ}} = 2\text{mA}$ . Plot the frequency response. (10 Marks)

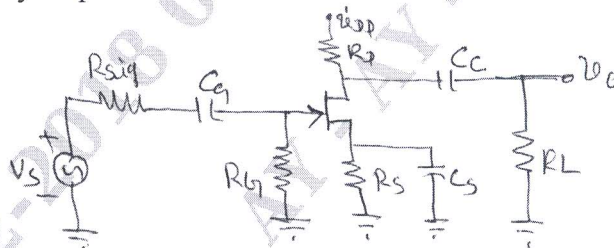


Fig.Q6(b)

**Module-4**

- 7 a. Determine input resistance and output resistance of voltage shunt feedback amplifier. (06 Marks)
- b. Determine the voltage, input and output impedance with feedback for voltage series feedback having  $A = 100$ ,  $R_i = 10\text{K}\Omega$  and  $R_o = 20\text{K}\Omega$  for feedback of i)  $\beta = 0.1$  ii)  $\beta = 0.5$ . (07 Marks)
- c. Explain the characteristics of negative feedback amplifier. (07 Marks)



OR

- 8 a. What is Barkhasen criteria for sustained oscillation? Explain basic principle of operation of oscillators. (08 Marks)
- b. Explain the working of Wein bridge oscillator. Write the equation for frequency of oscillations. (08 Marks)
- c. For the colpitts oscillators,  $C_1 = 0.005\mu\text{f}$ ,  $C_2 = 0.01\mu\text{f}$ ,  $L = 100\mu\text{H}$ ,  $L_{\text{PFC}} = 0.5\text{mH}$ ,  $C_C = 10\mu\text{f}$  and  $h_{fe} = 110$ .
- Calculate frequency of oscillation
  - Check the condition for oscillation is satisfied. (04 Marks)

**Module-5**

- 9 a. Explain the operation of transformer coupled class – A power amplifier and show that the maximum percentage efficiency is 50%. (07 Marks)
- b. Explain with neat circuit diagram, the working of a complementary symmetry class – B amplifier. (07 Marks)
- c. Derive an expression for second harmonic distortion using 3 – point method. (06 Marks)

OR

- 10 a. Define voltage regulator. Explain the operation of series regulator circuit. (07 Marks)
- b. Explain the operation of shunt regulator using OP-Amp with neat circuit diagram. (07 Marks)
- c. Calculate the output voltage and Zener current in the regulator circuit of Fig.Q10(c) for  $R_L = 1\text{K}\Omega$ ,  $V_Z = 12\text{V}$ ,  $R = 220\Omega$ ,  $v_i = 20\text{V}$  and  $\beta = 50$ . (06 Marks)

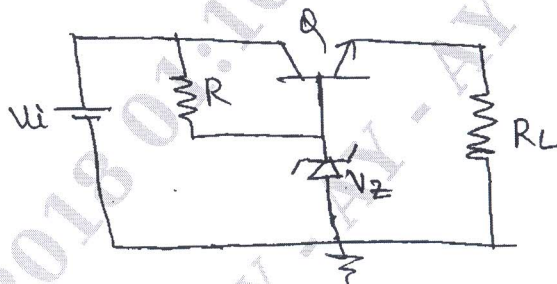


Fig.Q10(c)

\*\*\*\*\*