

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019
Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. For the circuit shown in Fig Q1(a) find the mesh current I_3 .

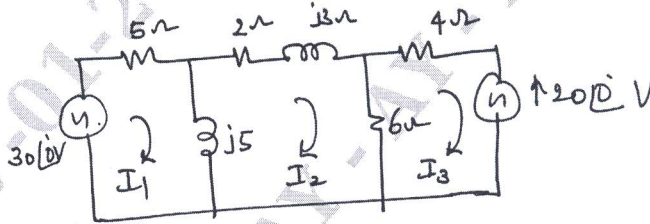


Fig Q1(a)

(06 Marks)

- b. Using node voltage analysis find the currents in each branch of the network shown in Fig Q1(b).

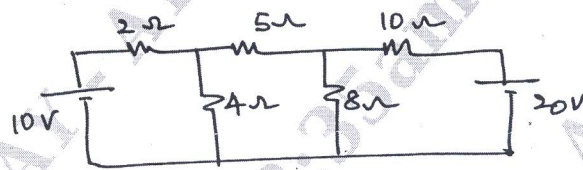


Fig Q1(b)

(07 Marks)

- c. Find the resistance between the terminals A and B in the circuit shown in Fig Q1(c)

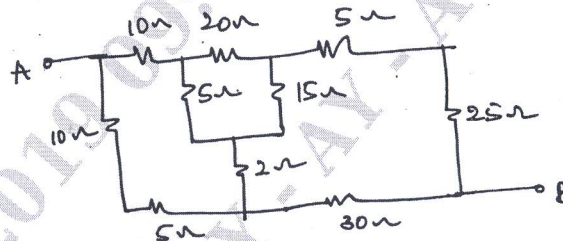


Fig Q1 (c)

(07 Marks)

- 2 a. Define the following terms with respect to the network topology.
i) True ii) Graph iii) Co-tree iv) Tieset v) Cutset (10 Marks)
- b. In the network shown in Fig Q2(b) consider branches 1, 3, 4 forming a tree. Write tie set schedule and hence write equilibrium equation on loop current basis and find the values of loop currents.

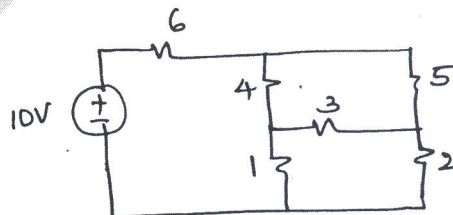


Fig Q2(b)

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 3 a. State and explain (i) Reciprocity theorem (ii) Millman's theorem as applied to electrical circuits. (10 Marks)
- b. By using superposition theorem, find the current through $R_L = 7.5\Omega$ in the network shown in Fig Q3(b).

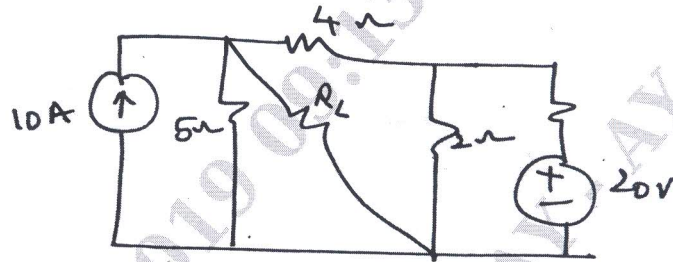


Fig Q3(b)

(10 Marks)

- 4 a. Determine the current through 1Ω resistor connected across AB in the network shown in Fig Q4(a) using Norton's theorem.

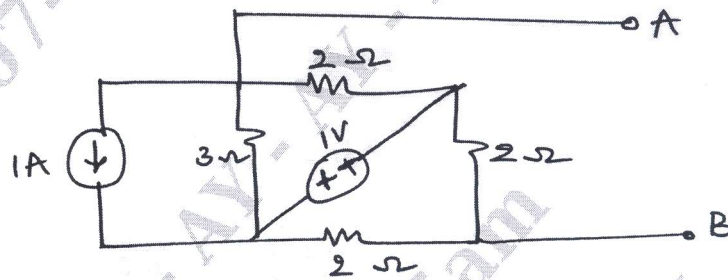


Fig Q4(a)

(08 Marks)

- b. State and explain Thevenin's theorem. (04 Marks)
- c. Find the value of R for which the power transferred across AB of the circuit shown in Fig Q4(c) is maximum and the maximum power transferred.

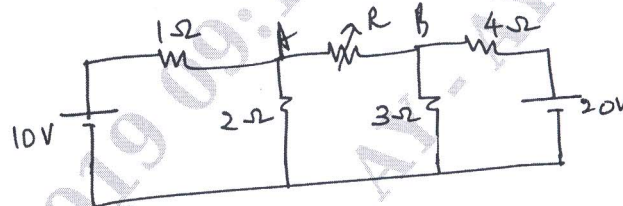


Fig Q4(c)

(08 Marks)

PART - B

- 5 a. An RLC series circuit has a resistance of 10Ω a capacitance of $100\mu\text{F}$ and a variable inductance.
- Find the value of the inductance of which the voltage across the resistance is maximum
 - Q factor
 - Voltage drops across R , L and C .
- The applied voltage is 230V , 50Hz . (06 Marks)
- b. Give the comparison between series resonance and parallel resonance. (06 Marks)
- c. Derive an expression for the resonance frequency of a resonant circuit consisting of R_L , L in parallel with R_C , C . draw the frequency response curve of the above circuit, indicating the half power frequencies (08 Marks)

- 6 a. In the network of Fig Q6(a), the switch K is closed at $t = 0$, with the capacitor uncharged. Find the values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$, for elements $V = 100V$, $R = 1000\Omega$, $C = 1\mu F$. (10 Marks)
- b. For the circuit shown in Fig Q6(b) the switch is opened at $t = 0$. Find the value of V , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0^+$

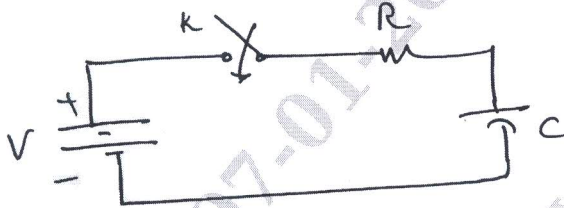


Fig Q6(a)

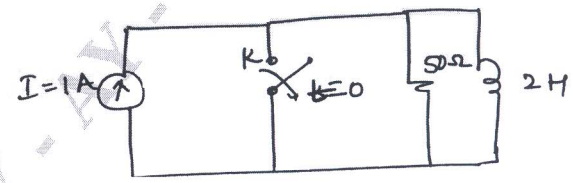


Fig Q6(b)

(10 Marks)

- 7 a. In the circuit shown in Fig Q7(a), the switch is closed at $t = 0$. Calculate the expression of the resulting currents using Laplace transform.

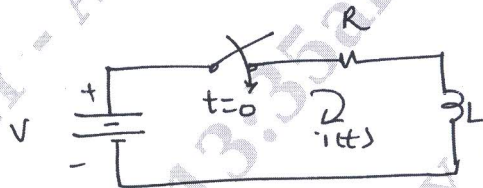


Fig Q7(a)

(10 Marks)

- b. Use initial and final value theorem to find $f(0)$ and $f(\infty)$ for the following

i) $f(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)}$

ii) $f(s) = \frac{e^{-2s}(s+2)}{s^2 + 5}$

(10 Marks)

- 8 a. Find Y parameters for the network shown in Fig Q8(a) (08 Marks)
- b. Determine the ABCD parameters for the network shown in Fig Q8(b). (12 Marks)

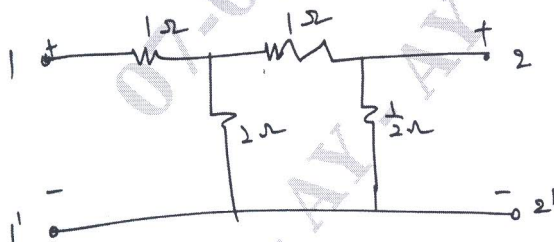


Fig Q8(a)

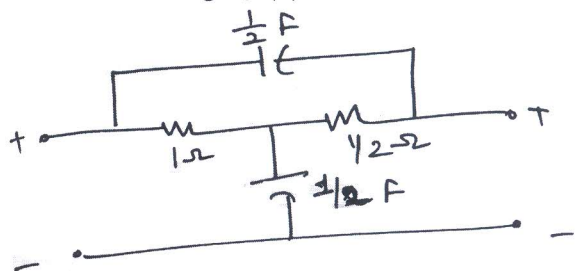


Fig Q8(b)
