

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--	--

15EC663

Sixth Semester B.E. Degree Examination, June/July 2018 Digital System Design Using Verilog

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. What are the two sources of power consumption in digital components? Explain. (04 Marks)
b. Develop a verilog model for a 4 : 1 multiplexer. (04 Marks)
c. Design an encoder for the buglar alarm that has sensors for each of the 8 zones as a priority encoder with zone 1 having highest priority down to zone 8 having lowest priority. (08 Marks)

OR

- 2 a. Explain the simple design methodology followed in IC industry. (08 Marks)
b. Develop a datapath to perform complex multiplication of two complex number whose real and imaginary parts are represented as signed fixed point numbers with 4-pre binary points and 12 post-binary points. Real and imaginary parts of the product are represented with 8 pre-binary points and 24 post-binary points. Area is the main constraint. Also write the verilog model of the complex multiplier datapath. (08 Marks)

Module-2

- 3 a. Design a 1m × 8 bit composite memory using 512 K × 8 bit memory component. (04 Marks)
b. Design a 16K × 48 – bit memory using 16K × 16 – bit memory component. (04 Marks)
c. Explain flowthrough and pipelined SSRAM with the help of timing diagram. (08 Marks)

OR

- 4 a. Determine whether there is an error in the ECC word 000111000100 and if so, correct it. (06 Marks)
b. Develop a verilog model of a dual – port 4K × 16 bit flow through SSRAM. One port allows data to be written and read, while the other port allows data to be read. (06 Marks)
c. Explain dynamic RAM operation. (04 Marks)

Module-3

- 5 a. Write and explain the internal organization of a CPLD. (08 Marks)
b. What are the two main design and manufacturing techniques for ASIC's. Explain. (08 Marks)

OR

- 6 a. Write and explain the internal organization of FPGA. (08 Marks)
b. Explain differential signaling in detail. (08 Marks)

Module-4

- 7 a. Explain Flash ADC and successive approximation ADC with the help of necessary diagrams. (08 Marks)
b. Design an input controller that has 8-bit binary-coded input from a sensor. The value can be read from an 8-bit input register. The controller should interrupt the embedded Gumnut core when the I/P value changes. The controller is the only interrupt source in the system. Also develop a verilog model of the I/P controller. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 8 a. Explain the following serial interface standards for connecting I/O devices:
(i) I²C (ii) USB (08 Marks)
b. With a neat diagram, explain R-string DAC and R/2R ladder DAC. (08 Marks)

Module-5

- 9 a. Explain the design flow of hardware/software co-design. (10 Marks)
b. Explain floorplan, placement and routing of ASIC physical design. (06 Marks)

OR

- 10 a. Explain Built-In Self Test (BIST) techniques. (08 Marks)
b. Explain the terms scan design and boundary scan. (08 Marks)

* * * * *