

USN

--	--	--	--	--	--	--	--	--	--

14EPS41

Fourth Semester M.Tech. Degree Examination, June/July 2018
FACTS Controllers

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1
 - a. Discuss control of power flow in AC transmission lines. (10 Marks)
 - b. Formulate the benefits of applying FACTS controllers. (04 Marks)
 - c. Describe the operation of 3 phase , 6 pulse VSC with neat schematic circuit diagram. (06 Marks)

- 2
 - a. Evaluate the equations for current and voltage at any point X on a transmission line $\{V(x), I(x)\}$ in terms of receiving end voltage and current $\{V_R, I_R\}$ for a transmission line supplying a UPF load. (12 Marks)
 - b. A 400 KV, 50Hz , 600 km long symmetrical line is operating at the rated voltage.
 - i) What is the theoretical maximum power that can be carried by the line?
 - ii) A series capacitor is connected at the midpoint of the line to double the power transmitted. Calculate the value of series reactance. The line data $\ell = 1\text{mH/km}$, $C = 11.1 \times 10^{-9} \text{ F/km}$. (08 Marks)

- 3
 - a. Elaborate the construction and working of SVC controller with the help of a basic block diagram. (10 Marks)
 - b. Discuss the applications of SVC and mark the control characteristics. Also describe the operation of SVC located at midpoint of a transmission line. (10 Marks)

- 4
 - a. Explain the operation of TCSC with the help of a single line diagram. (10 Marks)
 - b. With relevant current and voltage waveform, describe the working of a GCSC. (10 Marks)

- 5
 - a. Explain the following with respect to SPST :
 - i) Point – on – wave controlled phase angle regulator.
 - ii) Discrete – step controlled phase angle regulator.
 - iii) Based on VSC. (10 Marks)
 - b. Describe how the transient stability of a SMIB (Single Machine connected to an Infinite bus) System can be improved by using SPST. (10 Marks)

- 6
 - a. Analyse and explain three phase six pulse STATCOM, with a neat circuit diagram. (10 Marks)
 - b. Describe principle of operation of STATCOM, with neat sketches. (10 Marks)

- 7
 - a. Illustrate the operation of SSSC, with neat schematic and equivalent circuit. (10 Marks)
 - b. Describe the principle of operation of UPFC, with a neat diagram. (10 Marks)

- 8
 - a. Point out the applications of UPFC. (04 Marks)
 - b. Explain how UPFC can be modeled for power flow studies. (04 Marks)
 - c. Describe the operation of Interline power flow controller, with neat sketch. (12 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.