

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

16/17EPS21

Second Semester M.Tech. Degree Examination, June/July 2018 Power Electronic Converters

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Explain with figure galvanically isolated forward converter. (08 Marks)
- b. Explain with circuit and relevant waveforms operation of Buck-Boost in d.c steady state. (08 Marks)

OR

- 2 a. Explain with circuit diagram the operation of cuk converter, mentioning its advantages and disadvantages. (08 Marks)
- b. The average output voltage of the push-pull converter is $V_0 = 24$ volts at a resistive load of $R = 0.8\Omega$. The on state voltage drops of transistors and diodes are $V_t = 1.2$ volts and $V_d = 0.7$ volt respectively. The turn ratio of transformer is $a = N_s / N_p = 0.25$, if the input power is 750 watts. Determine :
 - i) output current
 - ii) output power
 - iii) input voltage
 - iv) input current
 - v) the efficiency. (08 Marks)

Module-2

- 3 a. Draw the block diagram of voltage controlled PWM control module and explain its operation. (08 Marks)
- b. With relevant circuit and waveforms, explain single phase inverter. (08 Marks)

OR

- 4 a. Enumerate the difference between bipolar and unipolar inverter. Explain with waveform the operation of unipolar PWM inverter. (08 Marks)
- b. Write a note on Asynchronous PWM and space vector modulation. (08 Marks)

Module-3

- 5 a. Draw the circuit of full wave rectifier using centre tapped transformer and explain. (08 Marks)
- b. Explain the operation of voltage doubler circuit along with its waveforms. (08 Marks)

OR

- 6 a. Draw the circuit diagram of Twelve -pulse rectifier and explain. (08 Marks)
- b. Explain the operating principle of single phase power factor correction. (08 Marks)

Module-4

- 7 a. Explain class D, DC-DC resonant converter with basic circuit. (08 Marks)
- b. Explain the process of parallel resonant converter. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 8 a. Explain the operation of phase shift modulated DC-DC converter. (08 Marks)
b. Write a brief note on :
i) Frequency converter
ii) Selective harmonic elimination. (08 Marks)

Module-5

- 9 a. Explain with relevant circuit and waveforms the operation of 3-phase AC-AC voltage converter having star connected resistive load. (10 Marks)
b. Write a note on bi-directional switches used in power electronic converter. (06 Marks)

OR

- 10 a. What are the main advantages of multilevel converters? (06 Marks)
b. Explain with sketch multilevel DC-DC converter. (10 Marks)

* * * * *