

**Second Semester M.Tech. Degree Examination, June/July 2018**  
**RF and Microwave Circuit Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions.**

- 1 a. Explain the properties, reasons for using and applications of RF/microwaves. (08 Marks)  
 b. Define the following and explain their behavior at radio frequencies:  
 (i) Wire (ii) Capacitor (iii) Inductor. (06 Marks)  
 c. Use the absorption method to match the source ( $100 + j126\Omega$ ) to a load ( $100011 - j795.8\Omega$ ) at 100 MHz as shown in Fig. Q1 (c). (06 Marks)

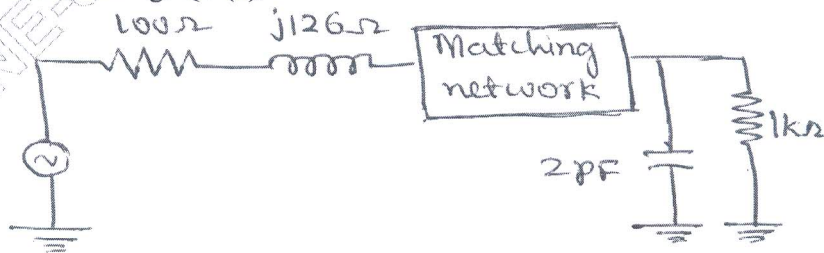


Fig. Q1 (c)

- 2 a. Define and derive the expressions for the following:  
 (i) Reflection co-efficient. (08 Marks)  
 (ii) Standing wave ratio. (06 Marks)  
 b. Consider a  $50\Omega$  lossless transmission line of length  $l = 1\text{ m}$ , connected to a generator operating at  $f = 1\text{ GHz}$  and having  $V_g = 10\text{ V}$  with  $Z_g = 50\Omega$  at one end and connected to a load  $Z_L = 100\Omega$  at the other. Determine  
 (i) The voltage and current at any point on the transmission line.  
 (ii) The voltage at the generator ( $V_i$ ) and load ( $V_L$ ) ends.  
 (iii) The reflection co-efficient and VSWR at any point on the line.  
 (iv) The average power delivered to the load. (06 Marks)  
 c. What are scattering parameters? Define and also explain formation of S-parameters for two port network. (06 Marks)
- 3 a. A microwave signal at frequency of  $f = 1\text{ GHz}$  is traveling on a transmission line having  $Z_0 = 50\Omega$  and terminated in a load of  $Z_L = 20\Omega$ . Find the values of  $Z_{\text{max}}$  and  $Z_{\text{min}}$  and their location on the transmission line. (08 Marks)  
 b. Given the circuit shown in Fig. Q3 (b) below, design a lumped matching network at 1 GHz that would transform  $Z_L = 10 + j10\Omega$  into a  $50\Omega$  transmission line. (12 Marks)

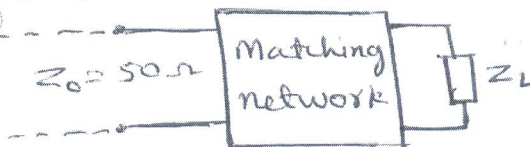


Fig. Q3 (b)

- 4 a. Explain the graphical solution of stability criteria. (08 Marks)  
b. For a single stage microwave transistor amplifier define the following:  
(i) Transducer power gain.  
(ii) Operating power gain.  
(iii) Available power gain. (06 Marks)  
c. Define noise figure. Obtain the noise figure of a lossy network. Show that the noise figure (F) of a lossy network at room temperature equals to the attenuation factor (L). (06 Marks)
- 5 a. Explain the design of,  
(i) Maximum – Gain Amplifier (MGA) (10 Marks)  
(ii) Low Noise Amplifier. (LNA) (10 Marks)  
b. Explain the design procedure for microwave transistor oscillator. (10 Marks)
- 6 a. Design and briefly explain the following conversion loss for SSB mixers:  
(i) Diode loss (ii) Mismatch loss (iii) Harmonic loss (10 Marks)  
b. What are the two types of semiconductor phase shifters? Briefly explain any one type. (10 Marks)
- 7 a. Briefly explain MIC materials. (10 Marks)  
b. Compare Hybrid microwave integrated circuits (HMICs) and microwave monolithic integrated circuits (MMICs). (10 Marks)
- 8 Write short notes on:  
a. Smith chart.  
b. One diode mixer.  
c. Detector losses.  
d. Chip mathematics. (20 Marks)

\* \* \* \* \*