



USN

--	--	--	--	--	--	--	--	--	--	--

14ELN15/25

First Semester B.E. Degree Examination, June/July 2019

Basic Electronics

Time: 3 hrs.


Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast ONE question from each part.

PART - 1

- 1
 - a. Sketch and discuss the forward and reverse characteristics of a silicon diode. (05 Marks)
 - b. Define rms and dc or average value of voltage, peak inverse voltage, ripple factor and conversion efficiency with respect to Half wave rectifier. (10 Marks)
 - c. A full wave rectifier circuit provides peak secondary voltage of 35V, the load resistance $R_L = 1\text{ k}\Omega$, $R_f = 13\Omega$, $R_s = 12\Omega$. Find the dc and rms value of output voltage. Also find the regulation. (05 Marks)
- 2
 - a. The diode clamping circuit in fig. Q2(a) has $\pm 10\text{V}$, 1 kHz square wave input. Calculate the tilt, and draw the output waveform. (06 Marks)

Fig. Q2(a)

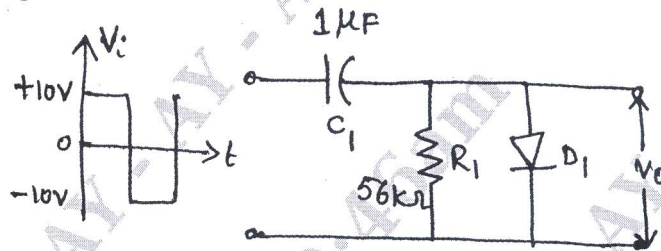

- b. Sketch and explain Zener diode voltage regulator. Discuss the effects of load current. (06 Marks)
- c. Explain BJT common emitter configuration with a suitable circuit, to draw the input and output characteristics. (08 Marks)

PART - 2

- 3
 - a. Explain the operation of Base bias circuit and write the equations for I_B , I_C and V_{CE} . (04 Marks)
 - b. A voltage divider bias circuit has $V_{CC} = 10\text{V}$, $R_C = 2.2\text{ k}\Omega$, $R_1 = 82\text{ k}\Omega$, $R_2 = 18\text{ k}\Omega$, $R_E = 0.5\text{ k}\Omega$. Find the 'Q' point and terminal voltages (V_B , V_C , V_E). Draw the load line and locate the operating point. (08 Marks)
 - c. Mention the ideal characteristics of an Op - amp and explain the concept of virtual ground. (08 Marks)
- 4
 - a. Derive an expression for output voltage of an Non - Inverting summing circuit. Draw the circuit. (10 Marks)
 - b. The two input voltages of an op-amp are 2V and 3V. The common output voltage is 2mV and the difference mode output voltage is 9V. Find CMRR. (05 Marks)
 - c. For a base bias circuit configuration $R_B = 470\text{ k}\Omega$, $R_C = 2.2\text{ k}\Omega$ and $V_{CC} = 18\text{V}$ and $\beta = 100$. Find I_B , I_C , V_{CE} . (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

PART - 3

- 5 a. Convert : i) $(47.8125)_{10} = (?)_2$ ii) $(1011101.1011)_2 = (?)_{16}$ iii) $(BCDE)_{16} = (?)_8 = (?)_{10}$. (06 Marks)
- b. Subtract i) 101000_2 from 0101111 using one's complement (05 Marks)
ii) $(15)_{10} - (18)_{10}$ using 2's complement.
- c. State and prove De – Morgan's theorem for two input variables by induction method. (05 Marks)
- d. Realize 'AND' gate using 'NOR' gate and 'OR' gate by 'NAND' gates only. (04 Marks)
- 6 a. Simplify the following Boolean expressions and implement the same using NOR gates only.
i) $F = \bar{X} \bar{Y} \bar{Z} + \bar{X} \bar{Y} \bar{Z} + \bar{X} \bar{Y} + X \bar{Y}$ ii) $F = (X + Y) (\bar{X} + Z) (\bar{Y} + Z)$. (07 Marks)
- b. For the given Boolean expression, draw the logic diagram using basic gates.
i) $Y = \overline{AB(C+D)}$ ii) $Z = \overline{X+AB}$. (05 Marks)
- c. Design Full adder using Half address. Write the expressions for SUM and CARRY. Also write the Truth Table. (08 Marks)

PART - 4

- 7 a. Draw NOR gate latch and its truth table. Explain the working of a NOR gate latch. (04 Marks)
- b. With a block diagram, explain the working of 8085 μ p. (06 Marks)
- c. Explain the working of clocked RS flip – flop. (05 Marks)
- d. What is Transducer? Compare active and passive transducers. (05 Marks)
- 8 a. Explain the working of LVDT. (06 Marks)
- b. Define Seebeck effect, Peltier and Thompson effect. (06 Marks)
- c. What is a microcontroller? List specific features of 8051 architecture. (06 Marks)
- d. Bring out the differences between piezoelectric and photo electric transducers. (02 Marks)

PART - 5

- 9 a. Derive an expression for AM wave. Write the spectrum. (06 Marks)
- b. Show that the total power in the modulated wave is 1.5 times the power in carrier. (06 Marks)
- c. Derive an expression for frequency modulated wave. (08 Marks)
- 10 a. Compare AM and FM. (05 Marks)
- b. Explain the operation of mobile communication with a block diagram. (05 Marks)
- c. Write a note on ISDN. (05 Marks)
- d. What are the advantages and disadvantages of an optical fiber communication? (05 Marks)
