

# CBCS SCHEME

									4	2	2
--	--	--	--	--	--	--	--	--	---	---	---

17EE34

## Third Semester B.E. Degree Examination, June/July 2019 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. With a neat circuit diagram, explain Emitter stabilized bias circuit, write the necessary equation. (08 Marks)
- b. Determine output voltage for the following circuit in Fig.Q.(b). Assume  $f = 1000\text{Hz}$  and ideal diode. (06 Marks)

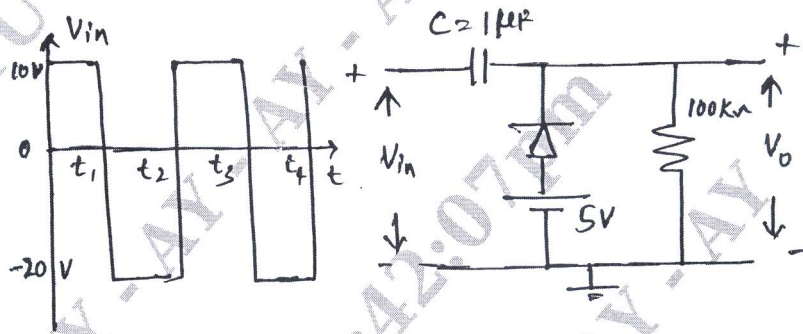


Fig.Q.1(b)

- c. Derive the expression for stability factors of fixed bias circuit with respect to  $I_{CO}$ ,  $V_{BE}$ ,  $\beta$  and draw the circuit diagram. (06 Marks)

OR

- 2 a. Explain the circuit of a transistor switch being used as an inverter. (06 Marks)
- b. Determine the voltage  $V_{CE}$  and the current  $I_C$  for the voltage divider configuration. Given:  $R_1 = 39\text{K}\Omega$ ,  $R_2 = 3.9\text{K}\Omega$ ,  $R_C = 10\text{K}\Omega$ ,  $R_E = 1.5\text{K}\Omega$ ,  $C_E = 50\mu\text{F}$ ,  $\beta = 100$ ,  $V_{BE} = 0.7$ . (08 Marks)
- c. Sketch the output waveform for the network shown in Fig.Q.2(c). If the peak value of the a.c input is 15V and draw the transfer characteristics. (06 Marks)

 


Fig.Q.2(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. With a neat circuit diagram, derive an expression for  $Z_i$ ,  $Z_o$  and  $A_v$  of fixed bias circuit using  $r_e$  - model. (08 Marks)  
 b. For the Emitter follower network shown in Fig.Q.3(b). Determine  $r_e$ ,  $Z_i$ ,  $Z_o$  and  $A_v$ . (06 Marks)

 


Fig.Q.3(b)

- c. Prove that Miller effect of input capacitance  $C_{Mi} = (1-A_v)C_f$  and output capacitance  $C_{Mo} = \left(1 - \frac{1}{A_v}\right)C_f$ . (06 Marks)

OR

- 4 a. For the following circuit determine  $Z_i$ ,  $Z_o$ ,  $A_v$ ,  $A_i$   $h_{fb} = -0.99$ ,  $h_{ib} = 14.3\Omega$ . (08 Marks)

 


Fig.Q.4(a)

- b. What are the advantages of h-parameters? (06 Marks)  
 c. Define h-parameters and obtain h-parameter equivalent circuit of CE configuration. (06 Marks)

**Module-3**

- 5 a. Obtain expression for voltage gain, current gain, input and output impedance of a Darlington Emitter follower circuit. Draw necessary equivalent circuit. (12 Marks)  
 b. With a neat block diagram, obtain expression for  $Z_{if}$  and  $Z_{of}$  for voltage series feedback amplifier. (08 Marks)

OR

- 6 a. Explain the general characteristics of negative feedback amplifier. (08 Marks)  
 b. Explain the need of cascading amplifier. A given amplifier arrangement has the following gains.  $A_{v1} = 10$ ,  $A_{v2} = 20$  and  $A_{v3} = 40$ . Calculate overall voltage gain and total voltage gain in dB. (06 Marks)  
 c. With a simple block diagram, explain the concept of feedback amplifier. (06 Marks)





**Module-4**

- 7 a. With a neat circuit diagram, explain the operation of a class B push pull power amplifier and maximum conversion efficiency is 78.5%. (08 Marks)
- b. With a neat circuit diagram, explain the operation of RC-phase shift oscillator using BJT and write  $f_{osc}$  equation. (06 Marks)
- c. A series fed class A amplifier as shown in Fig.Q.7(c). Operates from a DC source and applied sinusoidal input signal generates peak base current 9mA. Calculate  $I_{CQ}$ ,  $V_{CEQ}$ ,  $P_{dc}$ ,  $P_{ac}$  and efficiency. (06 Marks)

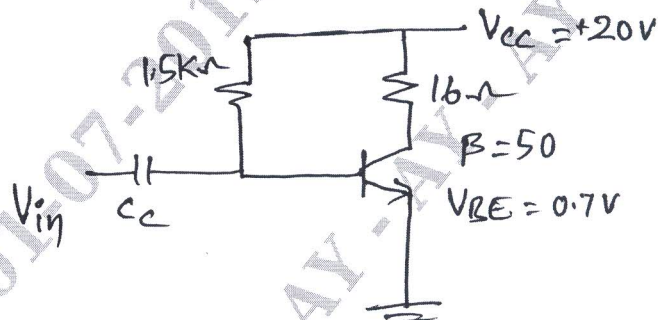


Fig.Q.7(c)

OR

- 8 a. The frequency selective circuit arms of wein bridge oscillator uses  $C_1 = C_2 = 0.001\mu F$ ,  $R_1 = 10K\Omega$  while  $R_2$  is kept variable. The frequency is to be varied from 10Hz to 50kHz by varying  $R_2$ . Find the range of  $R_2$ . (06 Marks)
- b. With a neat circuit diagram, explain the operation of a transformer coupled class A power amplifier and prove that conversion efficiency is 50%. (08 Marks)
- c. With a neat circuit diagram, explain the working principle of crystal oscillator in series resonant mode. (06 Marks)

**Module-5**

- 9 a. Explain the operation of JFET amplifier using fixed bias. Draw the JFET small signal model and derive the expression for  $Z_i$ ,  $Z_o$  and  $A_v$ . (06 Marks)
- b. Explain the construction, working and characteristics of n-channel enhancement type MOSFET. (08 Marks)
- c. Determine the following for network shown in Fig.Q.9(c)  $V_{GSQ}$ ,  $V_{DS}$ ,  $V_S$ ,  $V_G$ ,  $V_D$ . (06 Marks)

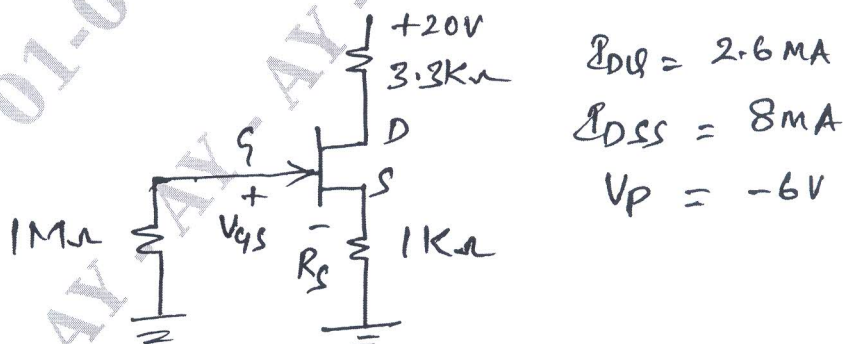


Fig.Q.9(c)

OR

- 10 a. Compare FET over BJT. (06 Marks)
- b. With neat diagrams, Explain the construction, working and characteristics of n-JFET's. (08 Marks)
- c. Design the fixed bias network as shown in Fig.Q.10(c) having an a.c. gain of 10. Determine the value of  $R_D$ . (06 Marks)

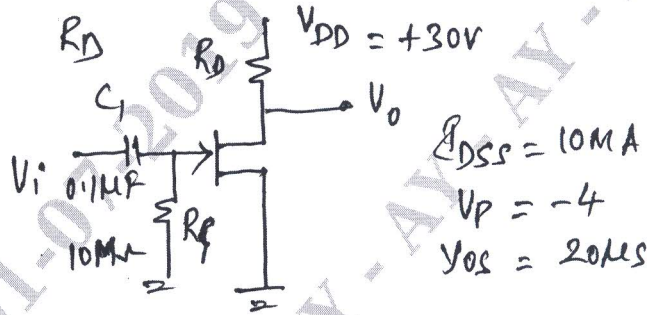


Fig.Q.10(c)

\*\*\*\*\*