

CBCS SCHEME

17EE46

Fourth Semester B.E. Degree Examination, June/July 2019 Operational Amplifiers and Linear ICs

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define and explain the following terms:
 - i) Input bias current
 - ii) Input offset current
 - iii) CMRR. (06 Marks)
- b. With a neat circuit diagrams, explain working and design procedure of capacitor coupled voltage follower. (08 Marks)
- c. For the circuit shown in Fig.Q.1(c), find V_0 given $R_F = 50K\Omega$ and $R_1 = 10K\Omega$ (06 Marks)

 


Fig.Q.1(c)

OR

- 2 a. What is an instrumentation amplifier? Obtain an expression for output voltage V_0 , in terms of change in resistance ' ΔR ' of an instrumentation amplifier using transducer bridge. (12 Marks)
- b. Explain with a neat circuit, scaling and averaging amplifier using op-amp in inverting configuration. (08 Marks)

Module-2

- 3 a. Explain the following terms with respect to voltage regulator: i) Line regulation ii) Load regulation iii) Ripple rejection. (06 Marks)
- b. With a neat circuit diagram, explain working of I order high pass filter and draw its typical frequency response curve. (10 Marks)
- c. A first order low pass filter has cut off frequency of 1kHz the resistance value designed is $15.6K\Omega$. Calculate the new value of resistance. If the cut off frequency is to be changed to 1.6kHz. Assume capacitor value as constant. (04 Marks)

OR

- 4 a. Explain working and design of voltage follower regulator. (07 Marks)
- b. An LM 317 voltage regulator is required to provide 6V output from 15V supply. Load current is 200mA. Design the circuit. Assume $I_1 = 1mA$ $V_{ref} = 1.25V$. (06 Marks)
- c. Design a wide band pass filter with $f_L = 200Hz$, $f_H = 1kHz$ and pass band gain = 4. Assume capacitor values of high pass and low pass sections as $0.05\mu F$ and $0.01\mu F$ respectively. Also calculate Q-factor, band width and center frequency. (07 Marks)

Module-3

- 5 a. Explain the working of an inverting voltage comparator circuit. Draw the input, output waveforms when ' V_{ref} ' is positive and negative. (06 Marks)
- b. A triangular/rectangular waveform generator uses $\mu A741$ opamp with $\pm 15V$ supply. Design a suitable circuit to obtain triangular output of $5V_{p-p}$, frequency variation from 200Hz to 2kHz and duty cycle adjustment from 20% to 80% of total time period. (08 Marks)
- c. With a neat circuit diagram, explain working and design procedure of RC phase shift oscillator. (06 Marks)

OR

- 6 a. With a neat circuit diagram, explain non inverting Schmitt trigger, if UTP is to be made OV, explain the modification to be done in circuit, draw the relevant input/output waveforms. (10 Marks)
- b. Explain the working of voltage to current converter with grounded load. (04 Marks)
- c. With a neat circuit diagram, explain Sawtooth wave oscillator. (06 Marks)

Module-4

- 7 a. With a neat circuit diagram, explain working of a non saturation precision half wave rectifier and draw its input and output waveforms. (08 Marks)
- b. Explain the working principle of linear RAMP analog to digital converter. (06 Marks)
- c. Design a precision full wave rectifier to produce 2V peak output from sine wave input of peak value 0.5V and frequency of 1MHz, use 741 opamp with $\pm 12V$ supply. (06 Marks)

OR

- 8 a. Explain R-2R ladder digital to analog converter circuit. (10 Marks)
- b. Digital input for a 4-bit DAC is 0110. Calculate its analog equivalent output voltage. (04 Marks)
- c. Explain working ADC using successive approximation method. (06 Marks)

Module-5

- 9 a. With a neat diagram, explain the internal architecture of IC555 timer. (10 Marks)
- b. Explain the operating principle of phase locked loop. (06 Marks)
- c. Define the terms related to PLL
- i) Lock range
 - ii) Capture range
 - iii) Pull in time
 - iv) Tracking range. (04 Marks)

OR

- 10 a. Explain how XOR gates can be used as phase detector in PLL. (06 Marks)
- b. Explain monostable multivibrator, realized using IC555 timer. (07 Marks)
- c. A PLL system with 105 kHz input has VCO with 100kHz free running frequency and sensitivity of 3.3 kHz/V. Phase detector has sensitivity of 0.68V/rad and amplifier gain of 5. Calculate : i) Loop gain ii) Phase difference iii) Static error voltage iv) Tracking range. (07 Marks)

* * * * *