



CBCS SCHEME

15EC63

Sixth Semester B.E. Degree Examination, June/July 2019 VLSI Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Derive the CMOS inverter DC characteristics graphically from p device and n device characteristics and show all operating regions. (08 Marks)
- b. Explain the working of nMOS enhancement mode transistor with suitable diagrams. (08 Marks)

OR

- 2 a. Derive expression for drain current in linear and saturation region for nMOS transistor. (08 Marks)
- b. With neat sketches explain the CMOS P-well process steps to fabricate a CMOS inverter. (08 Marks)

Module-2

- 3 a. Write the lambda based design rules for separation of layers and transistors. (06 Marks)
- b. Draw circuit, stick and layout diagram for nMOS shift register cell. (10 Marks)

OR

- 4 a. Define sheet resistance (R_s) standard unit of capacitance ($\square C_g$) and delay unit (τ) (06 Marks)
- b. Calculate the capacitance of the structure given below in Fig.Q4(b). (10 Marks)

 


Fig.Q4(b)

- Area capacitance value for metal 1 to substrate = $0.3\text{pF} \times 10^{-4}/\mu\text{m}^2$ (0.075 relative value)
- Area capacitance value for diffusion to substrate = $1\text{pf} \times 10^{-4}/\mu\text{m}^2$ (0.25 relative value)
- Area capacitance value for polysilicon to substrate = $0.4\text{ pF} \times 10^{-4}/\mu\text{m}^2$ (0.1 relative value).

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Obtain the scaling factor for the following device parameters :
- gate capacitance
 - gate area
 - saturation current (I_{dss})
 - channel resistance (R_{on})
 - maximum operating frequency (f_0)
 - power dissipation per gate (P_g)
 - current density (J)
 - gate delay (T_d).
- (08 Marks)
- b. With a neat diagram explain 4×4 Barrel shifter. (08 Marks)

OR

- 6 a. Explain the general arrangement of a 4 bit data path for processor. (08 marks)
- b. Describe Manchester carry chain element. (08 Marks)

Module-4

- 7 a. Discuss the architectural issues to be followed in the design of VLSI sub system. (05 Marks)
- b. Explain in detail the general structure of an FPGA fabric. (06 Marks)
- c. Explain switch logic implementation of CMOS 5 way selector with neat circuit diagram. (05 Marks)

OR

- 8 a. Explain the structured design approach for the implementation of a parity generator. (08 marks)
- b. Explain dynamic CMOS logic with example. (08 Marks)

Module-5

- 9 a. Explain 3 transistor dynamic RAM cell with schematic diagram. (06 Marks)
- b. Explain any two fault models in combinational circuits. (06 Marks)
- c. Write a note on automatic test pattern generation. (04 Marks)

OR

- 10 a. write short notes on :
- observability and controllability
 - Built In Self Test (BIST).
- (08 Marks)
- b. Explain nMOS pseudo static RAM cell with schematic diagram. (08 Marks)

* * * * *