

# CBCS SCHEME

15MT35



## Third Semester B.E. Degree Examination, June/July 2019 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- Explain the operation of P-N junction diode under :
    - No-bias condition
    - Forward bias condition
    - Reverse bias condition.

(08 Marks)
  - A zener diode regulator shown below in Fig.Q1(b) has the following circuit parameters :  $V_1 = 10V$ ,  $V_Z = 5V$ ,  $R_Z = 100\Omega$  and  $R_D = 500\Omega$ . Find : i) The percentage change in  $V_1$  for a 25 percent change in  $V_i$  ii) Output reactance  $R_0$  iii) Power dissipation in the regulator circuit iv) Voltage regulation assuming  $R_L = 0.5\Omega$ .

(08 Marks)

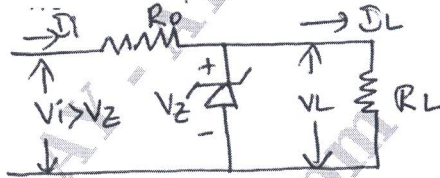


Fig.Q1(b)unregulated rectifier filter circuit.

OR

- Explain how a diode acts as a switch and also explain switching response of the diode with necessary circuit and timing diagram. 

(06 Marks)
  - Explain bridge wave rectifier with capacitor filter with neat circuit diagram and waveform, also derive the equation for ripple factor. 

(10 Marks)

### Module-2

- Explain first order low pass Butterworth filter and derive the gain and phase angle equations. 

(08 Marks)
  - Design a wide band pass filter with  $f_L = 200\text{hz}$ ,  $f_H = 1\text{KHz}$  i) passband gain = 4 ii) draw the frequency response of the filter ii) calculate the value of Q for the filter. 

(08 Marks)

OR

- Explain second order high pass Butterworth filter with necessary circuit diagram and equations. 

(04 Marks)
  - Design Wein bridge oscillator for the Fig.Q4(b) below so that  $f_0 = 965\text{hz}$ . 

(04 Marks)

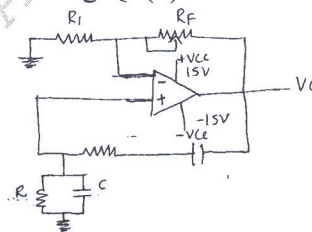


Fig.Q4(b)

- State Backhausen criterion for sustained oscillations and explain phase shift oscillator with necessary circuit and equations. 

(08 Marks)

**Module-3**

- 5 a. Explain basic non-inverting comparator with the input and output wave form if  $V_{ref}$  is positive and  $V_{ref}$  is negative. (08 Marks)
- b. With neat circuit and necessary equations explain squaring circuit with the input and output waveform and also plot the hysteresis voltage. (08 Marks)

**OR**

- 6 a. Explain how 555 timer can be configured for monostable operation with the internal block diagram. (10 Marks)
- b. Explain how an astable multivibrator can be used as free Ramp generator with necessary circuit, equations and waveforms. (06 Marks)

**Module-4**

- 7 a. Draw Rs latch with NAND and NOR gate circuit. (04 Marks)
- b. Explain clocked master-slave JK flip-flop with necessary logic circuit. (06 Marks)
- c. Explain bi-directional shift register with parallel load. (06 Marks)

**OR**

- 8 a. Explain 3-bit synchronous – Binary up-down counter. (08 Marks)
- b. Explain how read and write information transfer takes place in magnetic core-memory. (08 Marks)

**Module-5**

- 9 a. What is a multiplexer?  $F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$ . Implement the following Boolean function with 8 : 1 MUX. (06 Marks)
- b. Design BCD – to decimal decoder. (06 Marks)
- c. Implement a fulladder using 3: 8 a decoder. (04 Marks)

**OR**

- 10 a. What is quantization of analog signal? (02 Marks)
- b. What output voltage would be produced by D/A converter whose output range is 0 to 10V and whose input binary number is :  
 i) 10 (for a 2-bit D/A converter)  
 ii) 010 (for a 4-bit D/A converter)  
 iii) 10111100 (for a 8-bit D/A converter). (06 Marks)
- c. Explain SAR–ADC with necessary functional diagram. (08 Marks)

\*\*\*\*\*