



--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020
Logic Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer FIVE full questions, selecting atleast TWO questions from each part.

PART – A

- 1 a. Define canonical minterm forms and canonical maxterm forms. (04 Marks)
b. Design a three input, one output minimal two level gate combinational logic circuit which has an output 1 when majority of its inputs are at logic-0 and has an output equal to 0 when majority of its inputs are at logic 1. (06 Marks)
c. Use k-map to simplify the following functions :
i) $F(A, B, C, D) = ABD + \overline{A} \overline{C} \overline{D} + \overline{A} B + \overline{A} C \overline{D} + \overline{A} B D$
ii) $F(W, X, Y, Z) = \sum_m(1,3,7,11,15) + \sum_d(0,2,5)$
and realize simplified expressions using Basic Gates. (10 Marks)
- 2 a. Obtain all the prime muplicants of the following Boolean function using Quine – Mocluskey method.
 $F(A, B, C, D) = \sum_m(1,2,3,5,9,12,14,15) + \sum_d(4,8,11)$
And verify the result by using k-map. (10 Marks)
b. Simplify the function $f(a, b, c, d) = \sum_m(2, 3, 4, 5, 13, 15) + \sum_d(8, 9, 10, 11)$ by using MEV-Map technique and verify the result by using K-map. (10 Marks)
- 3 a. Describe general working principle of Decoder. (04 Marks)
b. Implement the following with a suitable decode with active low enable input and active high output
 $f(w, x, y, z) = \sum(4, 8, 10)$
 $g(a, b, c) = \pi(1, 3, 6)$. (08 Marks)
c. Draw the interfacing diagram of TEN key, key-pad interface to a digital system using decimal to BCD–encoder. (08 Marks)
- 4 a. Design a 2-bit comparator. (05 Marks)
b. Implement the following function using 8 : 1MUX
 $F(P, Q, R, S) = \sum_m(0, 1, 3, 4, 8, 15)$. (05 Marks)
c. With a neat logic diagram explain carry look ahead adder. (10 Marks)

PART – B

- 5 a. Explain how to use SR–latch as a switch de-bounces and draw the relevant timing diagram. (06 Marks)
b. Explain the working of master –slave flip-flop with the help of logic diagram, function table, logic symbol and timing diagram. (10 Marks)
c. How do you convert SR flip-flop to JK flip-flop. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 6 a. With the help of a diagram explain the following with respect to shift-registers.
 i) Parallel in serial out
 ii) Ring counter and twisted ring counter. (08 Marks)
- b. Design a MOD-6 synchronous counter using JK- flip-flop. (12 Marks)
- 7 a. Draw and explain the block diagram of Mealy and Moore model in a sequential circuit analysis. (10 Marks)
- b. Realize the system represented by the state diagram shown in Fig.Q7(b) using D-Flip-flop. (10 Marks)

 


Fig.Q7(b)

- 8 a. Design a counter using JK flip-flop whose counting is 000, 001, 100, 110, 111, 101, 000 etc by obtaining its minimal sum equations. (08 Marks)
- b. Construct the excitation table, transition table state table and state diagram for the sequential circuit shown in Fig.Q8(b) below. (12 Marks)

 


Fig.Q8(b)
