



# CBCS SCHEME

15EC34

## Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Network Analysis

Time: 3 hrs.

Max. Marks: 80

**Note:** 1. Answer any FIVE full questions, choosing ONE full question from each module.  
2. Missing data, if any, may be suitably assumed.

### Module-1

- 1 a. Derive expression for converting star to delta. (08 Marks)
- b. Using Mesh current find  $V_2$  which result a zero current in 4 ohm resistor in the network shown in Fig.Q1(b). (08 Marks)

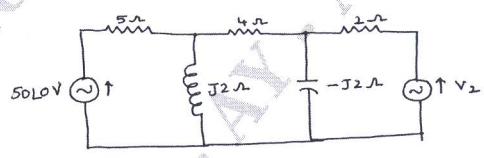


Fig.Q1(b)

### OR

- 2 a. For the network of Fig.Q2(a), determine the  $v_1$  and  $v_2$  by nodal analysis. (08 Marks)

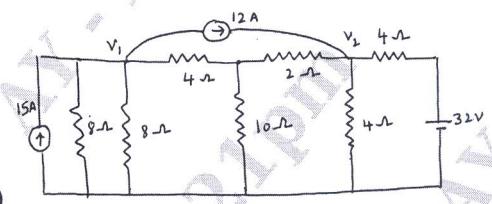


Fig.Q2(a)

- b. Find the current  $I$  in 28 ohm resistor by Mesh analysis in Fig.Q2(b). (08 Marks)

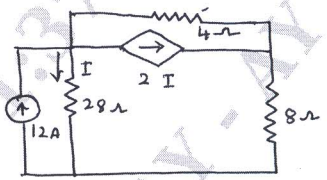


Fig.Q2(a)

### Module-2

- 3 a. State and prove superposition theorem. (06 Marks)
- b. Using Milliman's theorem, find  $I_L$  through  $R_L$  for the network shown in Fig.Q3(b). (04 Marks)

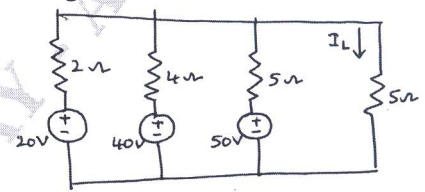


Fig.Q3(b)

- c. Obtain Norton equivalent of the network of Fig.Q3(c) between terminals A and B. (06 Marks)

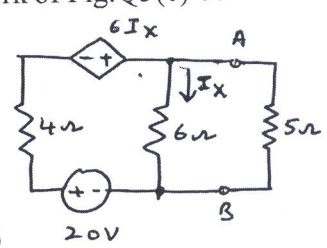


Fig.Q3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 4 a. State maximum power transfer theorem. Prove that  $Z_L = Z_0^*$  for AC circuits. (08 Marks)  
 b. Verity reciprocity theorem to find value of  $V_X$  in the circuit shown Fig.Q4(b). (08 Marks)

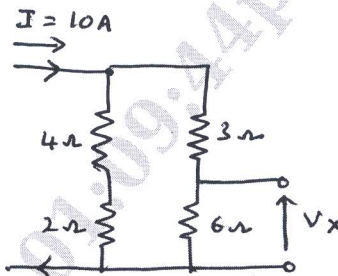


Fig.Q4(b)

**Module-3**

- 5 a. In the network shown in Fig.Q5(a), K is changed from position a to b at  $t = 0$ . Solve for  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , if  $R = 1000\Omega$ ,  $L = 1H$ ,  $C = 0.1\mu F$  and  $V = 100V$ . Assume that the capacitor is initially uncharged. (08 Marks)

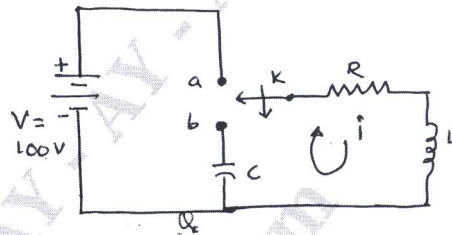


Fig.Q5(a)

- b. Determine the response current  $i(t)$  in the circuit shown in Fig.Q5(b) using Laplace transform. (08 Marks)

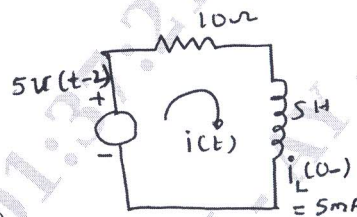


Fig.Q5(b)

OR

- 6 a. Synthesis the waveform shown in Fig.Q6(a) and find the Laplace transform of the periodic waveform. (08 Marks)

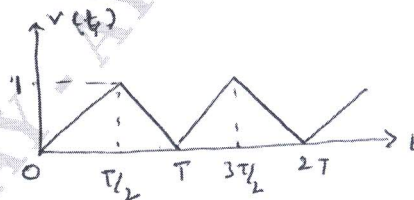


Fig.Q6(a)

- b. Determine  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  at  $t = 0^+$  when the switch k is opened at  $t=0$  in Fig.Q6(b). (08 Marks)

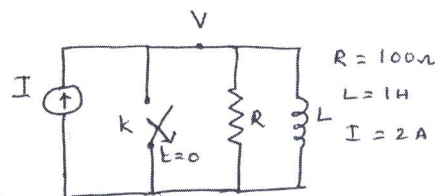


Fig.Q6(b)