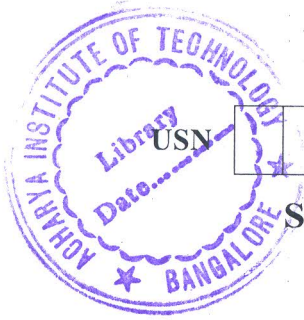


CBCS SCHEME



15EC63

Sixth Semester B.E. Degree Examination, Dec.2019/Jan.2020 VLSI Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Explain the step-by-step CMOS P-Well fabrication process. (08 Marks)
 - With the mathematical equations, explain velocity saturation and mobility degradation effect due to increase in saturation current. (08 Marks)

OR

- With the transfer characteristic of skewed inverter, explain the beta ratio effects. (06 Marks)
 - Compare CMOS and bipolar technologies. (06 Marks)
 - Consider the nMOS transistor in a 180 nm process with a nominal threshold of 0.4V and doping level of $8 \times 10^{17} \text{ cm}^{-3}$. The body is tied to ground with a substrate contact. How much does the threshold change at room temperature if the source is at 1.1V instead of '0'? (04 Marks)

Module-2

- Discuss the λ -based design rules (i) Butting contact (ii) Transistors (nMOS, pMOS and CMOS) (08 Marks)
 - Derive the expression of delay in terms of τ for CMOS inverter pair. (08 Marks)

OR

- Draw the layout for $\bar{Y} = A + BC$ using CMOS. (08 Marks)
 - Find the C_{in} for the layout shown in Fig.Q4(b).

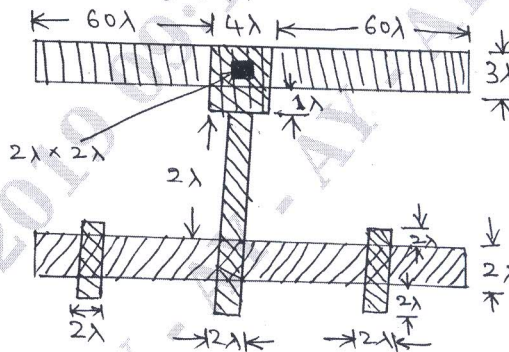


Fig.Q4(b)

(08 Marks)

Module-3

- Define scaling. Explain the scaling factors for device parameters. (08 Marks)
 - What is Manchester Carry Chain? Explain it. (08 Marks)

OR

- What are the problems associated with VLSI design and how to reduce by using standard practice? (06 Marks)
 - Draw the 4×4 cross bar switch using MOS switches and explain it. (06 Marks)
 - Calculate the Regularity for 4×4 bit and 8×8 bit shifter. (04 Marks)

Module-4

- 7 a. Construct a stick diagram for an nMOS parity generator as shown in Fig.Q7(a). The required response is such that $z = 1$ if there is an even number (including zero) of 1s on the input and $z = 0$ if there is an odd number.

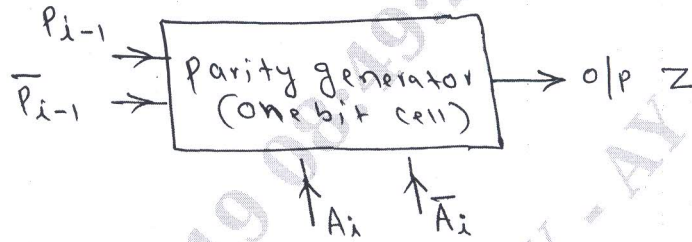


Fig.Q7(a)

(08 Marks)

- b. Draw the block diagram of Generic structure of an FPGA fabric and explain it. (08 Marks)

OR

- 8 a. Construct a stick diagram for an multiplexer shown in Fig.Q8(a) using CMOS.

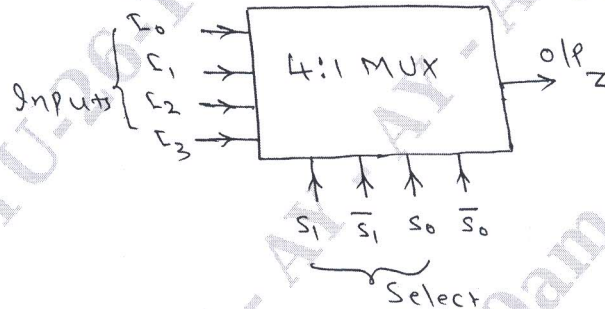


Fig.Q8(a)

(08 Marks)

- b. Explain the goals and techniques of FPGA based system design. (08 Marks)

Module-5

- 9 a. What are the requirements for system timing considerations? (06 Marks)
 b. Explain the operation of a three transistor dynamic RAM cell. (06 Marks)
 c. Write a note on stuck - at faults. (04 Marks)

OR

- 10 a. With the help of block diagram, explain the process of logic verification. (08 Marks)
 b. Explain the operation of CMOS pseudo-static memory cell. (08 Marks)
