

## Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 80


*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Explain the dc analysis of emitter stabilized bias circuit. State its advantages and disadvantages. (06 Marks)
- b. Obtain an expression for  $S_{V_{BE}}$  OR  $S'$  for voltage divider bias circuit. Also express relation between  $S_{I_{CO}}$  (S) and  $S_{V_{BE}}$  (S'). (10 Marks)


OR

- 2 a. For voltage divider bias circuit  $R_1 = 68K\Omega$ ,  $R_2 = 6.8K\Omega$ ,  $R_C = 3.3K\Omega$ ,  $R_E = 1K\Omega$ ,  $V_{CC} = 12V$  and  $\beta = 100$ . Determine the location of Q-point. Draw the circuit diagram. (10 Marks)
- b. For the circuit shown in Fig.Q.2(b), determine  $V_{CE}$ ,  $V_E$  and  $I_E$ . Given that  $R_B = 220K\Omega$ ,  $R_E = 2.2K\Omega$ ,  $V_{BB} = 5V$ ,  $V_{EE} = -5V$ ,  $\beta = 100$ . (06 Marks)

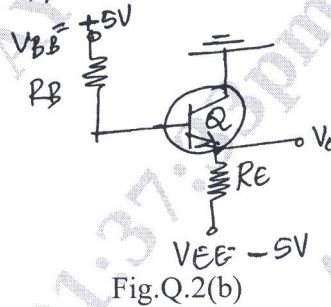
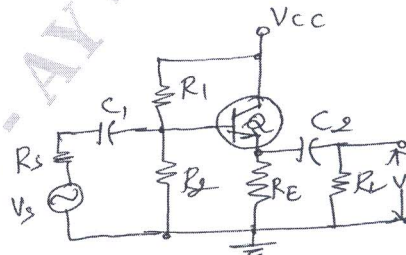
### Module-2

- 3 a. State the conditions to operate transistor in saturation region, just out of saturation region and for active region. (03 Marks)
- b. For the common collector circuit shown in Fig.Q.3(b),  $R_1 = 47K\Omega$ ,  $R_2 = 4.7K\Omega$ ,  $R_E = 3.3K\Omega$ ,  $R_L = 10K\Omega$ ,  $R_S = 1K\Omega$ ,  $h_{ic} = 1.2K\Omega$ ,  $h_{fc} = -101$ ,  $h_{rc} = 1$  and  $h_{oc} = 25\mu A/V$ . Determine  $A_i$ ,  $Z_i$ ,  $A_v$  and  $A_{vs}$ . How do you justify your results? Use exact h-parameter model. (10 Marks)



- c. State and explain the conditions to apply approximate h-parameter model for small signal equivalent circuit. (03 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.


OR

- 4 a. Consider a hybrid II model for CE stage. Explain the variation of current gain vs frequency. Obtain an expression for cut off frequency  $f_{\beta}$ . (10 Marks)
- b. The short circuit CE current gain of transistor is 50 at a frequency of 5MHz, if  $f_{\beta} = 300\text{kHz}$ , determine  $f_T$ ,  $h_{fe}$  and  $|A_i|$  when  $f = 10\text{MHz}$ . (06 Marks)

**Module-3**

- 5 a. For the 2-stage cascade amplifier shown in Fig.Q.5(a), calculate  $A_i$ ,  $A_v$ ,  $Z_i$ ,  $Z_o$ . Given  $h_{ie} = 1.1\text{K}\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = h_{oe} = 0$ . (10 Marks)

Fig.Q.5(a)

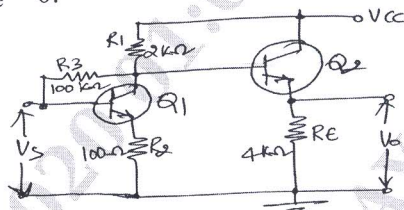


- b. What is a CASCODE amplifier? Draw the circuit of CASCODE amplifier. State its advantage. (06 Marks)

OR

- 6 a. Obtain an expression for transfer gain and stability of gain in negative feedback amplifier. (08 Marks)
- b. For the voltage series feedback amplifier shown in Fig.Q.6(b), calculate  $D$ ,  $A_{vf}$ ,  $Z_{if}$  and  $Z'_{of}$ . (08 Marks)

Fig.Q.6(b)

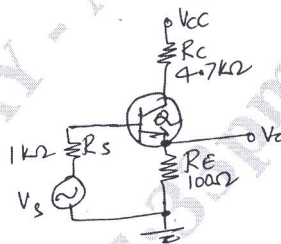**Module-4**

- 7 a. Derive an expression for second harmonic distortion and power output due to distortion in a power amplifier. Use 3-point method. (10 Marks)
- b. A complementary push pull amplifier has capacitive couple load,  $R_L = 8\Omega$ ,  $V_{CC} = \pm 12\text{V}$ , find  $P_{ac\text{max}}$ ,  $P_D$  of each transistor and conversion efficiency. (06 Marks)

OR

- 8 a. Obtain an expression for frequency of oscillations in Hartley oscillator. (10 Marks)
- b. A crystal has  $\alpha = 0.1\text{H}$ ,  $C = 0.01\text{pF}$ ,  $R = 10\text{K}\Omega$ ,  $C_M = 1\text{pF}$ . Find  $f_s$  and  $Q$ -factor. Also state Barkhausen criteria for sustained oscillations. (06 Marks)

**Module-5**

- 9 a. List the important features of FET and state its drawback also. (06 Marks)
- b. For the voltage divider bias circuit of FET,  $R_D = 1.2\text{K}\Omega$ ,  $R_S = 2\text{K}\Omega$ ,  $R_1 = 20\text{K}\Omega$ ,  $R_2 = 10\text{K}\Omega$ ,  $V_{DD} = 12\text{V}$ ,  $I_{DSS} = 12\text{mA}$ ,  $V_P = -4\text{V}$ , determine  $I_D$ ,  $V_{GS}$ ,  $V_G$ ,  $V_{DS}$  and  $V_S$ . Draw the circuit diagram. (10 Marks)

OR

- 10 a. Consider JFET with self bias having unbypassed  $R_S$ . Obtain expression for  $Z_i$ ,  $Z_o$  and  $A_v$ . Draw the circuit diagram and small signal circuit also. (10 Marks)
- b. Explain the differences between depletion type and enhancement type MOSFETS. (06 Marks)

\*\*\*\*\*