

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Derive an expression for $S_{I_{CO}}$ and S_{V_B} of collector to base bias circuit. (08 Marks)
 b. Design a suitable Clipper circuit to the output shown in Fig Q1(b). Assume silicon diode.

 


Fig Q1(b)

(05 Marks)

- c. Find I_C , V_E , V_B , V_C and V_{CE} for the circuit shown in Fig 1(c). Assume silicon transistor with $\beta = 60$.

 


Fig Q1(c)

(07 Marks)

OR

- 2 a. Explain how a transistor can be used as a switch. (07 Marks)
 b. Determine I_E , I_B , V_{CE} , V_{CB} , V_C , and V_E for the network shown in Fig Q2(b). Assume silicon transistor with $\beta = 60$.

 


Fig Q2(b)

(07 Marks)

- c. Determine V_o for the network shown in Fig Q2(c) the frequency of i/p signal is 1KHz. Assume ideal diode.

 


Fig Q2(c)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. For the network shown in Fig Q3(a) determine z_i , z_o , A_v and A_f

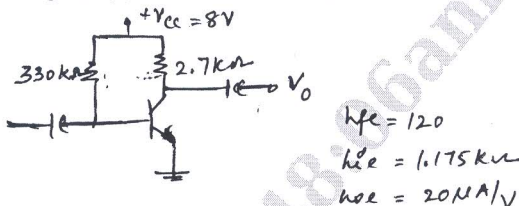


Fig Q3(a)

(08 Marks)

- b. Derive an expression for z_i , z_o , A_v for emitter follower configuration using approximate hybrid model. (08 Marks)
 c. Obtain the expression for Miller i/p capacitance. (04 Marks)

OR

- 4 a. Draw the complete hybrid equivalent model of a transistor. Derive an expression for z_i , z_o , A_f and A_v . (10 Marks)
 b. For the common base amplifier shown in Fig Q4(b), determine: i) z_i ii) A_f iii) A_v . Give $h_{ie} = 1.6k\Omega$, $h_{fe} = 110$, $h_{re} = 2 \times 10^{-4}$, $h_{oe} = 20\mu A/V$.

 


Fig Q4(b)

(10 Marks)

Module-3

- 5 a. For the Darlington emitter, follower shown in Fig Q5(a)
 i) Calculate the dc bias voltages V_B , V_E , V_C and currents I_B and I_C
 ii) Calculate the i/p and o/p impedances
 iii) Determine the voltage and current gains
 iv) The ac o/p voltage for $V_i = 120mV$.

 


Fig Q5(a)

(10 Marks)

- b. For the cascaded arrangement shown in Fig Q5(b), calculate :
 i) The loaded voltage gain of each stage
 ii) The total gain of the system A_v and A_{v1}
 iii) The loaded current gain of each stage
 iv) The total current gain of the system.

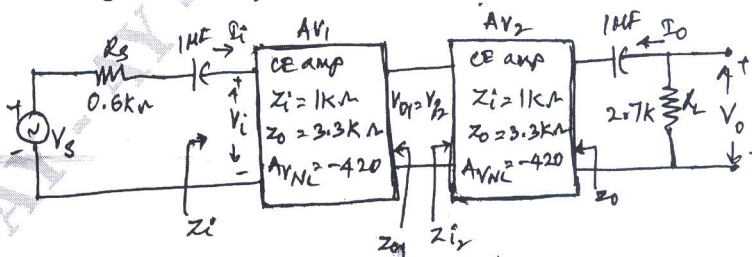


Fig Q5(b)

(10 Marks)

OR

- 6 a. List the advantages of negative feedback. (10 Marks)
 b. Derive an expression for input resistance of current series and current shunt feedback amplifier. (04 Marks)
 c. Negative feedback to be used to reduce noise from an amplifier by 90% i) what must the percentage negative feedback to accomplish this, if the initial voltage gain is 50?
 ii) What will be the voltage gain with feedback. (06 Marks)

Module-4

- 7 a. Derive an expression for frequency of oscillation of RC phase shift oscillator. (10 Marks)
 b. With a neat circuit diagram, explain the working of complementary class B power amplifier. (06 Marks)
 c. The following distortion readings are available for a power amplifier. $D_2 = 0.2$, $D_3 = 0.02$, $D_4 = 0.06$ with $I_1 = 3.3$ A and $R_C = 4\Omega$.
 i) Calculate THD ii) Determine the fundamental power iii) calculate the total power (04 Marks)

OR

- 8 a. With a neat circuit diagram, explain the working of Hartley oscillator. (06 Marks)
 b. For a class B amplifier providing a 20V peak signal to a 16Ω load and a power supply of $V_{CC} = 30V$, determine the i/p power, o/p power and efficiency. (06 Marks)
 c. Explain the classification of power amplifier based on Q- point. (08 Marks)

Module-5

- 9 a. Draw the circuit a fixed bias JFET amplifier and its equivalent circuit. Hence obtain the expression Z_{in} , Z_0 and A_v . (10 Marks)
 b. A JFET has device parameter of $g_{m0} = 10m\Omega$ and $I_{DSS} = 12mA$. When the device is suitably biased, the drain current was found to be 8mA. Determine : i) V_P ii) g_m iii) V_{GS} (06 Marks)
 c. Give the comparison of FET over BJT. (04 Marks)

OR

- 10 a. With a neat sketch, explain the construction and working principle of N-channel enhancement type MOSFET and also explain its static drain characteristics. (10 Marks)
 b. Obtain the expression for trans conductance g_m of JFET. (04 Marks)
 c. For the voltage divider bias configuration shown in Fig Q10(c). Determine the value of R_s , if $V_D = 12V$ and $V_{GSQ} = -2V$.

 


Fig Q10(c)

(06 Marks)
