

CBCS SCHEME



15EE32

Third Semester B.E. Degree Examination, Aug./Sept.2020

Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Reduce the circuit shown in Fig.Q1(a) to a voltage source in series with a resistance between the terminals AB.

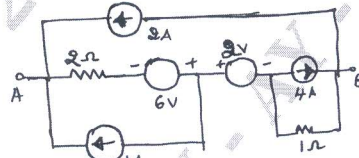


Fig.Q1(a)

(06 Marks)

- b. Find the single delta equivalent circuit of the circuit shown in Fig.Q1(b).

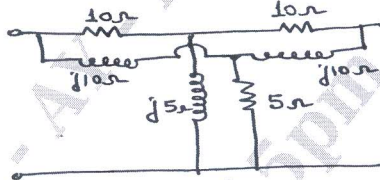


Fig.Q1(b)

(07 Marks)

- c. In Fig.Q1(c), $R = R_L = 1 \Omega$, $L = 1H$ and $C = 0.5F$. Find the resonance frequency and the admittance at the resonant frequency.



Fig.Q1(c)

(03 Marks)

OR

- 2 a. In the circuit shown in Fig.Q2(a), find I_o using mesh analysis method.

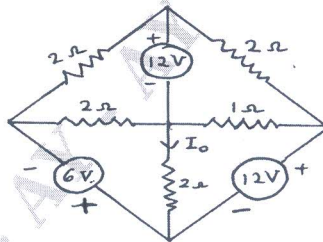


Fig.Q2(a)

(06 Marks)

- b. Using Node-analysis method, find the current through 12Ω resistor in the circuit shown in Fig.Q2(b).

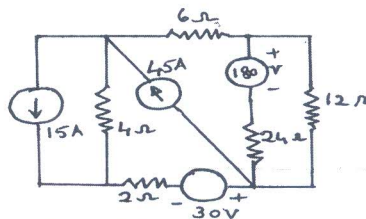


Fig.Q2(b)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. Construct the dual network for the network shown in Fig.Q2(c).

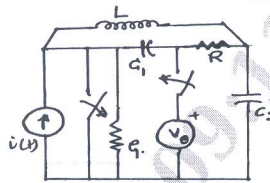


Fig.Q2(c)

(04 Marks)

Module-2

- 3 a. Using superposition theorem find the current I in the circuit shown in Fig.Q3(a).

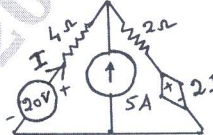


Fig.Q3(a)

(05 Marks)

- b. State and verify the reciprocity theorem for the network shown in Fig.Q3(b).

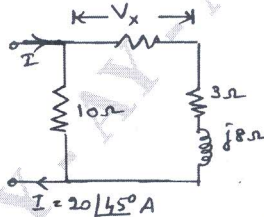


Fig.Q3(b)

(05 Marks)

- c. In the network shown in Fig.Q3(c), find the current I using Thevenin's theorem.

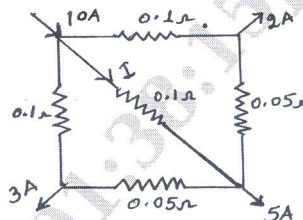


Fig.Q3(c)

(06 Marks)

OR

- 4 a. Find the Norton's equivalent of the circuit shown in Fig.Q4(a).

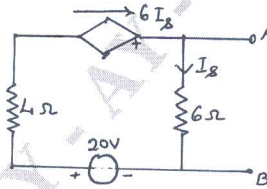


Fig.Q4(a)

(04 Marks)

- b. In the network shown in Fig.Q4(b), find Z_L so that it makes maximum power and determine the maximum power.

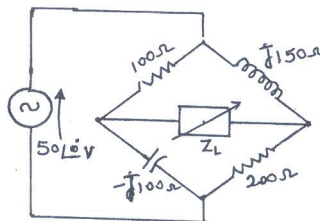


Fig.Q4(b)

(08 Marks)

- c. State and prove Millman's theorem.

(04 Marks)

Module-3

- 5 a. For the network shown in Fig.Q5(a), find the values of nodal voltages, their first and second derivatives at $t = 0_+$. For $t < 0$, all switches are closed. At $t = 0$, they are opened $I_{a(0-)} = 1 \text{ A}$, $V_{2(0-)} = 0 \text{ V}$.

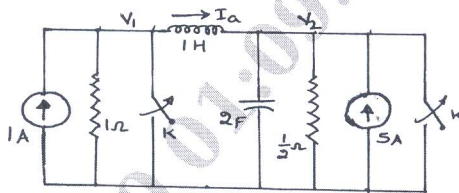


Fig.Q5(a)

(10 Marks)

- b. In the network shown in Fig.Q5(b), switch k is closed at $t = 0$ with zero current in the inductor. Find $i(t)$, $\frac{d}{dt}i(t)$ at $t = 0_+$ and obtain an expression for $i(t)$ at $t \geq 0$ by classical method.

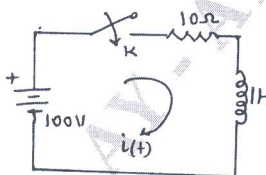


Fig.Q5(b)

(06 Marks)

OR

- 6 a. The switch k in the network of the Fig.Q6(a) is closed at $t = 0$, connecting the battery to an unenergized network. Determine i , V_1 , $\frac{d}{dt}i$, $\frac{d^2}{dt^2}i$ and $\frac{d}{dt}V_1$ at $t = 0_+$.

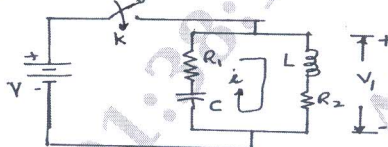


Fig.Q6(a)

(10 Marks)

- b. In the network shown in Fig.Q6(b), the switch k is closed at $t = 0$ a steady-state having previously been attained. Solve for the current in the circuit as a function of time.

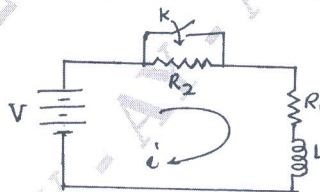


Fig.Q6(b)

(06 Marks)

Module-4

- 7 a. State and prove Initial and Final value theorem. (05 Marks)
 b. At $t = 0$ the switch is closed. Using Laplace transform determine $i_1(t)$ and $i_2(t)$ shown in Fig.Q7(b). The initial currents through the inductors are $i_{1(0)} = 1 \text{ A}$ and $i_{2(0)} = 2 \text{ A}$.

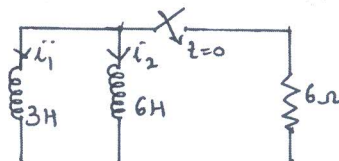


Fig.Q7(b)

(08 Marks)

- c. State and prove Shifting theorem. (03 Marks)

OR

- 8 a. Find the Transform of voltage $V(t)$ of waveform shown in Fig.Q8(a).

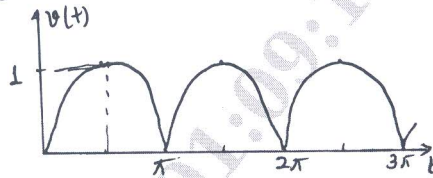


Fig.Q8(a)

(10 Marks)

- b. Find the initial and final values of $i(t)$ using initial and final value theorems:

(i) $I(s) = \frac{(s^2 + 5)}{(s^3 + 2s^2 + 4s)}$

(ii) $I(s) = \frac{8(s^2 + 2s + 1)}{(s + 2)(s^2 + 4)}$

(06 Marks)

Module-5

- 9 a. A star-connected unbalanced system of impedance of 20Ω , $(16 + j12)\Omega$ and $(16 - j12)\Omega$ in the phases R, Y and B is being supplied by a 400V balanced, 3 ϕ generator with phase sequence RYB. Determine the line currents, current in the neutral line and the power supplied to the load, when the neutrals are connected. (06 Marks)
- b. Define Transmission parameters. (04 Marks)
- c. Determine the expression for current $i(t)$ in the circuit shown in Fig.Q9(c), when the applied voltage is given by $e(t) = 10 + 100\sin(100t + 30^\circ) + 50\sin(300t + 60^\circ) + 20\cos(500t + 30^\circ)V$

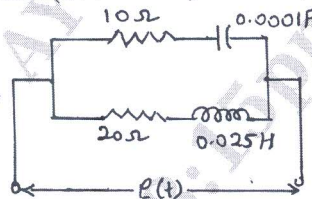


Fig.Q9(c)

(06 Marks)

OR

- 10 a. Find the transmission parameters for the circuit shown in Fig.Q10(a).

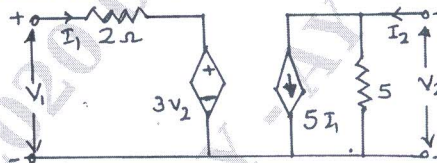


Fig.Q10(a)

(08 Marks)

- b. Determine $G_{21}(s)$ and $Y_{12}(s)$ for the network shown in Fig.Q10(b).

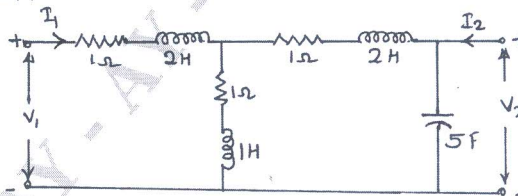


Fig.Q10(b)

(08 Marks)
