

CBCS SCHEME

18EE32

Third Semester B.E. Degree Examination, Aug./Sept.2020

Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Determine voltage V_3 for the circuit shown in Fig.Q1(a), using Mesh analysis method.

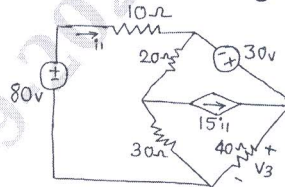


Fig.Q1(a)

(08 Marks)

- b. Apply node analysis method to find node voltages V_1 , V_2 , V_3 for the circuit shown in Fig.Q1(b).

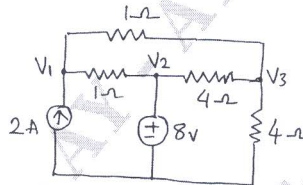


Fig.Q1(b)

(07 Marks)

- c. Determine the equivalent resistance between the terminals AB for circuit shown in Fig.Q1(c).

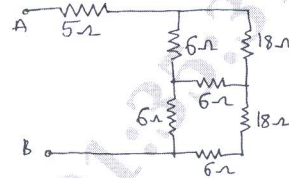


Fig.Q1(c)

(05 Marks)

OR

- 2 a. Apply loop analysis method to find voltage V , such that current through $(2 + j3) \Omega$ resistor is zero. For the circuit shown in Fig.Q2(a).

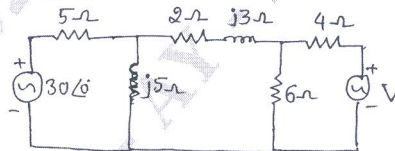


Fig.Q2(a)

(07 Marks)

- b. Determine the voltage V_x in the circuit shown in Fig.Q2(b) using Nodal analysis method.

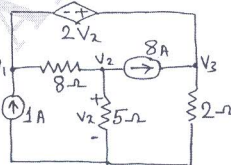


Fig.Q2(b)

(07 Marks)

- c. Apply source transformation and shifting method to reduce the circuit shown in Fig.Q2(c) to a single voltage source in series with resistance.

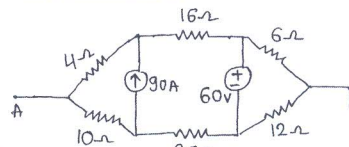


Fig.Q2(c)

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. In the circuit shown in Fig.Q3(a), determine current I_x using super position theorem.

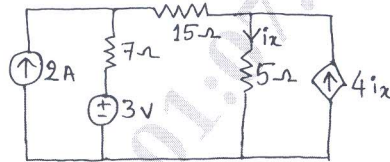


Fig.Q3(a)

(07 Marks)

- b. Determine Thevenin's equivalent of the circuit in Fig.Q3(b).

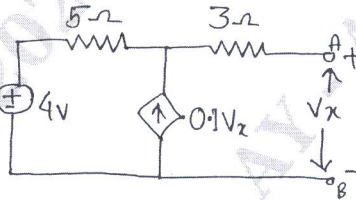


Fig.Q3(b)

(07 Marks)

- c. Use Millman's theorem to find current I , for the circuit shown in Fig.Q3(c).

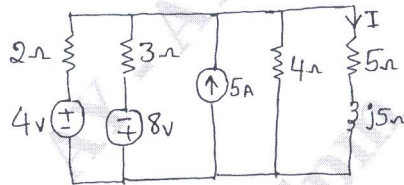


Fig.Q3(c)

(06 Marks)

OR

- 4 a. Determine current through 1Ω resistor. Using Norton's theorem for the circuit shown in Fig.Q4(a).

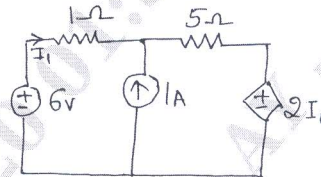


Fig.Q4(a)

(07 Marks)

- b. Determine the load resistance R_L to receive maximum power from the source. Also find maximum power delivered to the load in the circuit shown in Fig.Q4(b).

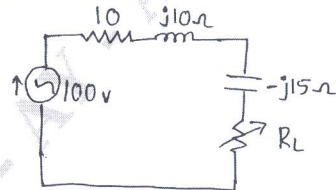


Fig.Q4(b)

(07 Marks)

- c. State and verify reciprocity theorem for the circuit shown in Fig.Q4(c).

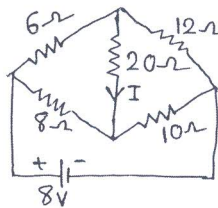


Fig.Q4(c)

(06 Marks)

Module-3

- 5 a. Derive an expression for the resonance frequency of a resonant circuit consisting of R_L , X_L in parallel with RC , X_C . (07 Marks)
- b. An impedance coil having a resistance of 4Ω and an inductance of 1mH connected in series with $10\mu\text{F}$ capacitor. Determine resonant frequency, impedance at resonance, half power frequencies, Q of the circuit and bandwidth. (08 Marks)
- c. For the circuit shown in Fig.Q5(C), the switch is moved from position 1 to 2 at $t = 0$. The steady state has been reached before switching. Determine : i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$.

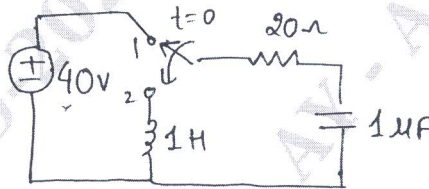


Fig.Q5(c)

(05 Marks)

OR

- 6 a. In circuit shown in Fig.Q6(a), the switch K is closed at $t = 0$. Calculate $\frac{di_1(0^+)}{dt}$ and $\frac{di_2(0^+)}{dt}$. Assume that the circuit was not activated before $t = 0$.

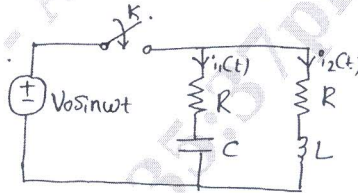


Fig.Q6(a)

(10 Marks)

- b. Determine R_L and R_C for which the circuit shown in Fig.Q6(b), resonances at all frequencies.

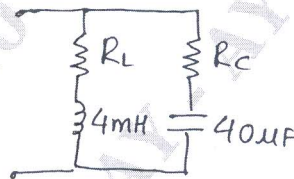


Fig.Q6(b)

(04 Marks)

- c. Show that in series RLC circuit, the resonant frequency $f_0 = \sqrt{f_1 f_2}$.

(06 Marks)

Module-4

- 7 a. State and prove initial and final value theorem in Laplace transformation. (08 Marks)
- b. Find Laplace transform of the signal shown in Fig.Q7(b).

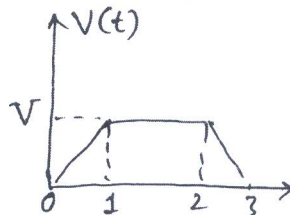


Fig.Q7(b)

(08 Marks)

- c. Find Laplace transform of unit step function.

(04 Marks)

OR

- 8 a. State and prove shifting theorem. (05 Marks)
 b. Verify initial value theorem, given $f(t) = 10e^{5t}$. (05 Marks)
 c. Find Laplace transform of the signal in Fig.Q8(c).

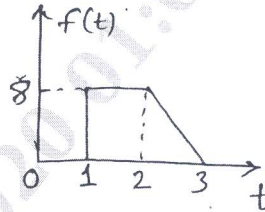


Fig.Q8(c)

(10 Marks)

Module-5

- 9 a. Three impedances $Z_1 = 20 \angle 30^\circ \Omega$, $Z_2 = 40 \angle 60^\circ \Omega$ and $Z_3 = 10 \angle -90^\circ \Omega$ are delta connected to a 400V, 3 – phase system as show in Fig.Q9(a). Determine the :
 i) Phase currents ii) Line currents.

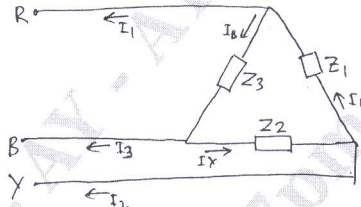


Fig.Q9(a)

(06 Marks)

- b. Determine Y-parameters for the circuit shown in Fig.Q9(b).

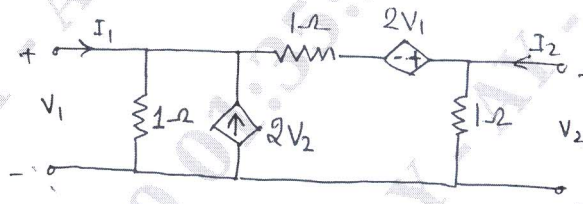


Fig.9(b)

(08 Marks)

- c. Express Y-parameters in terms of Z-parameters. (06 Marks)

OR

- 10 a. An unbalanced four-wire, star connected load has a balanced voltage of 400V, the loads are $Z_1 = (4 + j8)\Omega$, $Z_2 = (3 + j4)\Omega$, $Z_3 = (15 + j20)\Omega$. Calculate the : i) line currents ii) current in the neutral wire. (06 Marks)
 b. Find Z-parameters and T-parameters for the circuit shown in Fig.Q10(b).

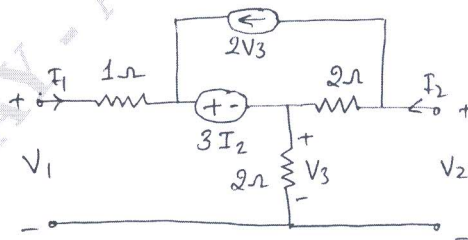


Fig.Q10(b)

(10 Marks)

- c. Define H – parameters with necessary equations. (04 Marks)
