



USN									
-----	--	--	--	--	--	--	--	--	--

10EC63

**Sixth Semester B.E. Degree Examination, Aug./Sept. 2020**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

Note: Answer any **THREE** full questions from Part-A and any **TWO** full questions from Part-B.

**PART - A**

- 1 a. Derive an expression for drain current of a MOSFET in different regions of operation. (05 Marks)
- b. Explain how the MOSFET can be used as an amplifier and as a switch. (05 Marks)
- c. Explain different biasing methods in MOS amplifier circuits. (10 Marks)
- 2 a. Draw the development of the T-equivalent circuit model for the MOSFET. (05 Marks)
- b. The NMOS and PMOS transistors in the circuit shown in Fig. Q2 (b) are matched with  $K'_n \left(\frac{W_n}{L_n}\right) = K'_p \left(\frac{W_p}{L_p}\right) = 1 \frac{\text{mA}}{\text{V}^2}$  and  $V_{in} = -V_{tp} = 1 \text{ V}$ . Assuming  $\lambda = 0$  for both devices, find the drain currents  $i_{DN}$  and  $i_{DP}$  and the voltage  $V_0$  for  $V_1 = 0 \text{ V}, +2.5 \text{ V}$  and  $-2.5 \text{ V}$ . (05 Marks)

 


Fig. Q2 (b)

- c. For a common gate amplifier with  $g_m = 1 \text{ mA/V}$  and  $R_D = 15 \text{ K}\Omega$ . Find  $R_{in}, R_{out}, AV_O, A_V$  and  $G_V$  for  $R_L = 15 \text{ K}\Omega$  and  $R_{sig} = 50 \Omega$ . What will the overall voltage can become for  $R_{sig} = 1 \text{ K}\Omega, 10 \text{ K}\Omega$  and  $100 \text{ K}\Omega$ . (10 Marks)
- 3 a. What is MOSFET scaling? Explain about short channel effect due to scaling. (05 Marks)
- b. Explain with neat diagram of Wilson MOS mirror. (05 Marks)
- c. Given  $V_{DD} = 3 \text{ V}$  and  $I_{REF} = 100 \mu\text{A}$  it is required to design a basic MOSFET constant current source to obtain an output current whose nominal value is  $100 \mu\text{A}$ . Find  $R$  if  $Q_1$  and  $Q_2$  are matched and have channel length's of  $1 \mu\text{m}$ , channel width's of  $10 \mu\text{m}$ ,  $V_t = 0.7 \text{ V}$  and  $K'_n = 200 \mu\text{A/V}^2$ . What is the lowest possible value of  $V_0$ ? Assuming that for this process technology the early voltage  $V'_A = 20 \text{ V}/\mu\text{m}$ , find the output resistance of the current source. Also, find the change in output current resulting from a  $+1 \text{ V}$  change in  $V_0$ . (05 Marks)
- d. Draw the BJT constant current source circuit and explain it. (05 Marks)
- 4 a. In common gate amplifier with active load, obtain 3-dB frequency for using open circuit time constants. Draw the circuit required for determining  $R_{gs}$  and  $R_{gd}$ . (10 Marks)
- b. Consider a source follower circuit, specified as follows :  $W/L = 7.2 \mu\text{m}/0.36 \mu\text{m}$ ,  $I_D = 100 \mu\text{A}$ ,  $g_m = 1.25 \text{ mA/V}$ ,  $\chi = 0.2$ ,  $r_o = 20 \text{ K}\Omega$ ,  $R_{sig} = 20 \text{ K}\Omega$ ,  $R_L = 10 \text{ K}\Omega$ ,  $C_{gs} = 20 \text{ fF}$ ,  $C_{gd} = 5 \text{ fF}$ ,  $C_L = 15 \text{ fF}$ . Find three capacitances  $C_{gd}, C_{gs}$  and  $C_L$ . Find  $\tau_H$  and the percentage contribution to it from each of three capacitances. Find  $f_H$ . (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8=50, will be treated as malpractice.

- 5 a. Draw the two stage Op-Amp CMOS OpAmp configuration and briefly explain obtain overall open loop gain. (08 Marks)
- b. The differential amplifier in figure uses transistors with  $\beta = 100$ . Evaluate the following:
- (i) The input differential resistance  $R_{id}$ .
  - (ii) The overall differential voltage gain  $V_o/V_{sig}$  (Neglect the effect of  $r_o$ ).
  - (iii) The worst case common mode gain if the two collector resistances are accurate to within  $\pm 1\%$ .
  - (iv) The CMRR in dB.
  - (v) The input common mode resistance (assuming that the early voltage  $V_A = 100$  V) (12 Marks)

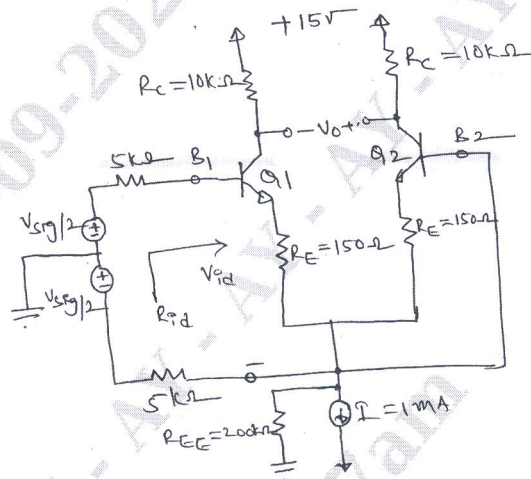


Fig. Q5 (b)

**PART - B**

- 6 a. Explain briefly with expressions the properties of Negative feedback. (10 Marks)
- b. Explain about Shunt-Shunt feedback amplifier with diagram and obtain the expression for input impedance and output impedance. (10 Marks)
- 7 a. Explain instrumentation amplifier with neat circuit diagram. (05 Marks)
- b. Use the superposition principle to find the output voltage of the circuit shown in Fig. Q7 (b). (05 Marks)

 


Fig. Q7 (b)

- c. Explain logarithmic and antilogarithmic amplifiers with neat diagrams. (10 Marks)
- 8 a. Explain the dynamic operation of a CMOS inverter. (10 Marks)
- b. Sketch a CMOS logic circuit that realizes the function  $Y = ABC + DE$ , using AOI gate. (04 Marks)
- c. Explain charge sharing problem in dynamic 3-input NAND circuits. (06 Marks)

\*\*\*\*\*