

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

14ELN15/25

**First/Second Semester B.E. Degree Examination, Aug./Sept.2020**  
**Basic Electronics**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting at least ONE question from each part.**

**Module-1**

- Explain with circuit diagram and waveforms the working of half wave rectifier. (05 Marks)
  - Draw the circuit of a clamper which clamps negative peak of the input square waveform to zero level and explain its operations. (07 Marks)
  - In a Bipolar Junction Transistor circuit, find the relation between  $\alpha_{dc}$  and  $\beta_{dc}$ . If  $\alpha_{dc} = 0.98$   $I_B = 100\mu A$ , compute the value of  $I_C$ ,  $I_E$  and  $\beta_{dc}$ . (08 Marks)
- With a neat circuit diagram, explain the working of a series and a shunt clipper. (08 Marks)
  - In Zener voltage regulator circuit, find the value of resistance R which is connected in series with input  $v_i = 16V$ , when  $I_Z = 20mA$ ,  $V_Z = 10V$  and  $R_L = 1k\Omega$ . (05 Marks)
  - Draw the output characteristics of a transistor in common emitter configuration and explain the various regions. (07 Marks)

**Module-2**

- In a voltage divider bias circuit using NPN transistor  $R_1 = 33k\Omega$ ,  $R_2 = 12k\Omega$ ,  $R_C = 1.2K\Omega$ ,  $R_E = 1K\Omega$ ,  $V_{CC} = 18V$ . Find the emitter voltage, collector voltage and collector to emitter voltage. (07 Marks)
  - What are the ideal characteristics of an op-amp? (05 Marks)
  - With a circuit diagram, explain how an op-amp can be used as a differentiator and integrator. (08 Marks)
- In a base bias circuit using NPN transistor  $R_C = 2.2K\Omega$ ,  $R_B = 470K\Omega$ ,  $V_{CC} = 18V$ ,  $\beta = 100$ . Find  $I_B$ ,  $I_C$  and  $V_{CE}$ . (05 Marks)
  - Draw the block diagram of an op-amp and explain the function of each block. (06 Marks)
  - In the op-amp circuit shown in Fig.Q4(c).

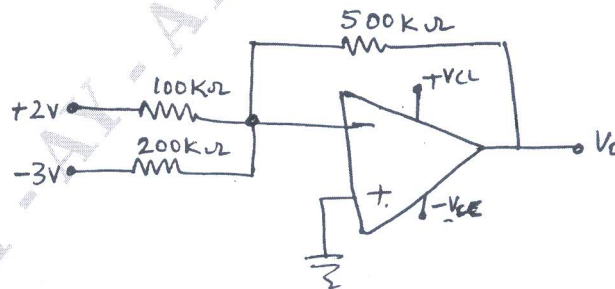


Fig.Q4(c)

- Find the value of  $V_0$ . (04 Marks)
- Explain how an op-amp can be used as an inverting amplifier. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-3**

- 5 a. Simplify the following and realize using basic gates.  
 $Y = \overline{ABC} + \overline{A}BC + \overline{AB}C + \overline{ABC}$ . (05 Marks)
- b. Subtract :  
 i)  $(11010)_2$  from  $(11101)_2$   
 ii)  $(11101)_2$  from  $(11010)_2$  using 2's complement method. (05 Marks)
- c. Realize two input X-OR gate using NOR gates. (05 Marks)
- d. Explain the working of two input AND gate using Diodes. (05 Marks)
- 6 a. Simplify the following and realize using NAND gates :  
 $F = XY + XY\overline{Z} + XYZ + \overline{X}YZ$ . (04 Marks)
- b. Convert :  
 i)  $(1D6.CA8)_{16} = ( )_8$   
 ii)  $(204.2)_8 = ( )_{10}$   
 iii)  $(532.65)_{10} = ( )_2$ . (06 Marks)
- c. Design a logic circuit using basic gates with three inputs A, B, C and one output Y. Output will be high only when A and C are at '1' or B and C are at '1'. (05 Marks)
- d. Design a full adder and implement using gates. (05 Marks)

**Module-4**

- 7 a. Explain the working of RS Latch using NOR gates. (05 Marks)
- b. With a neat block diagram explain the architecture of 8085 microprocessor. (10 Marks)
- c. Write a note on LVDT. (05 Marks)
- 8 a. Draw the circuit of RS flip flop using NAND gates and a clock. Explain its working with truth table. (06 Marks)
- b. What are the difference between microprocessor and microcontroller? (05 Marks)
- c. Explain the flag register of 8085. (04 Marks)
- d. Explain the working of thermister. (05 Marks)

**Module-5**

- 9 a. Draw the basic block diagram of communication system and explain. (05 Marks)
- b. What is amplitude modulation? Explain with the waveforms. (05 Marks)
- c. Explain the principle of operation of mobile phone. (05 Marks)
- d. With the block diagram, explain the optical fibre communication system. (05 Marks)
- 10 a. What is modulation? Explain the need for modulation. (05 Marks)
- b. Compare Amplitude Modulation and Frequency Modulation. (05 Marks)
- c. Draw and explain a typical telephone network. (05 Marks)
- d. Explain the block diagram of ISDN. (05 Marks)

\*\*\*\*\*