

## Third Semester B.E. Degree Examination, July/August 2021 Network Theory

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions.*

- 1 a. Find the equivalent resistance  $R_{ab}$  for circuit in Fig. Q1 (a) and use it to find  $i$ . (06 Marks)

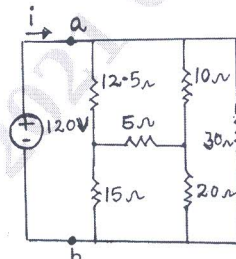


Fig. Q1 (a)

- b. Determine power supplied by the dependent source of Fig. Q1 (b), using nodal analysis. (06 Marks)

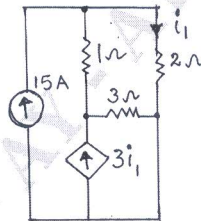


Fig. Q1 (b)

- c. Determine current through  $2 \Omega$  resistor of Fig. Q1 (c) using mesh analysis. (08 Marks)

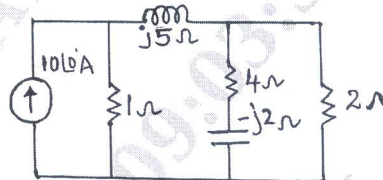


Fig. Q1 (c)

- 2 a. Using source transformation and source shifting techniques, find voltage across  $2 \Omega$  resistor in Fig. Q2 (a). (06 Marks)

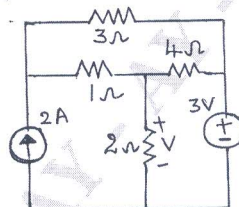


Fig. Q2 (a)

- b. Find  $I_1, I_2, I_3$  in the circuit of Fig. Q2 (b) using mesh analysis. (06 Marks)

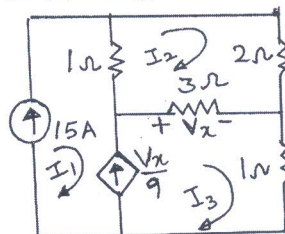


Fig. Q2 (b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- c. Compute  $V_1, V_2$  in the circuit of Fig. Q2 (c) using nodal analysis.

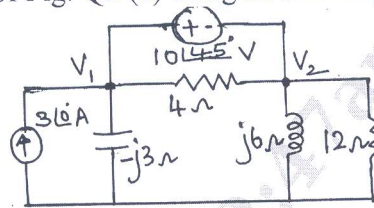


Fig. Q2 (c)

- 3 a. For the circuit in Fig. Q3 (a), use the superposition theorem to find  $I$ .

(06 Marks)

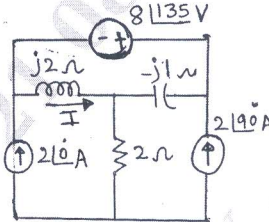


Fig. Q3 (a)

- b. Using Norton's theorem, find current through  $5 \Omega$  resistor in Fig. Q3 (b).

(06 Marks)

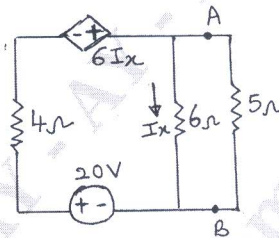


Fig. Q3 (b)

- c. State Millman's theorem, using Millman's theorem find  $I_L$  in Fig. Q3 (c).

(08 Marks)

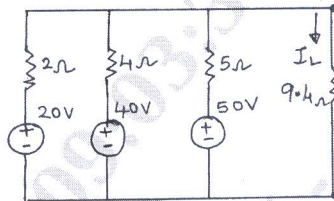


Fig. Q3 (c)

- 4 a. Determine the Thevenin equivalent at terminals A-B of the circuit in Fig. Q4 (a). (06 Marks)

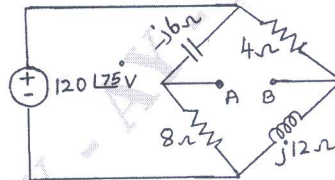


Fig. Q4 (a)

- b. Compute the value of  $R$  that results in maximum power transfer to it in Fig. Q4 (b). Find the maximum power. (06 Marks)

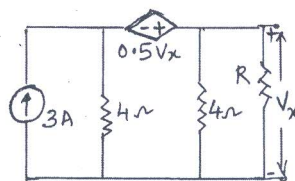


Fig. Q4 (b)

- c. State Reciprocity theorem. Find  $V_x$  and verify Reciprocity theorem for circuit in Fig. Q4 (c). (08 Marks)

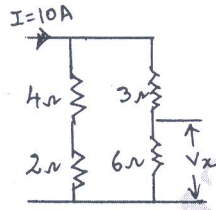


Fig. Q4 (c)

- 5 a. In the network shown in Fig. Q5 (a), the switch K is opened at  $t = 0$ . Solve for the values of  $V$ ,  $\frac{dV}{dt}$  and  $\frac{d^2V}{dt^2}$  at  $t = 0^+$ . (10 Marks)

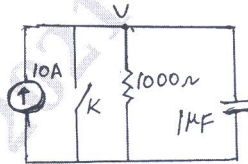


Fig. Q5 (a)

- b. In the network shown in Fig. Q5 (b), a steady state is reached with the switch K open. At  $t = 0$  switch K is closed. Solve for the values of  $I_1$ ,  $I_2$ ,  $V_C$ ,  $\frac{dI_1}{dt}$ ,  $\frac{dI_2}{dt}$  at  $t = 0^+$ . (10 Marks)

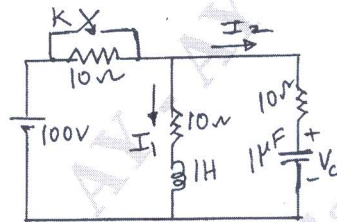


Fig. Q5 (b)

- 6 a. In the network shown in Fig.6(a), K is changed from position a to b at  $t = 0$ . Solve for  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , The steady state having reached before switching. (10 Marks)

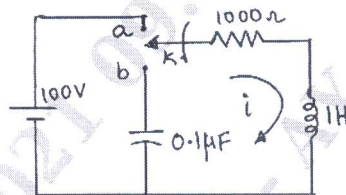


Fig. Q6 (a)

- b. In the network of Fig. Q6(b), the switch K is closed at  $t = 0$  with zero capacitor voltage and zero inductor current. Solve for (a)  $V_1$  and  $V_2$  at  $t = 0^+$  (b)  $V_1$  and  $V_2$  at  $t = \infty$ , (c)  $\frac{dV_1}{dt}$  and  $\frac{dV_2}{dt}$  at  $t = 0^+$ , (d)  $\frac{d^2V_2}{dt^2}$  at  $t = 0^+$ . (10 Marks)

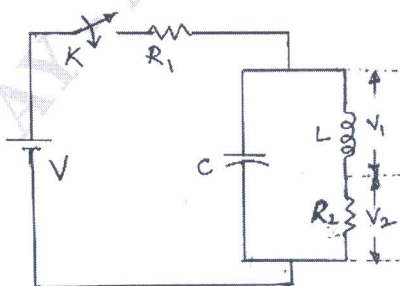


Fig. Q6 (b)



- 7 a. In the circuit given in the Fig. Q7 (a) switch is closed on position 1 at  $t = 0$  and at  $t = 500 \mu\text{s}$ , switch is moved to position 2. Obtain the equation of current in both intervals. Use Laplace transforms. (10 Marks)

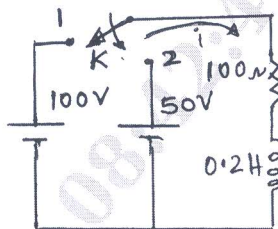


Fig. Q7 (a)

- b. Determine the Laplace transform of the periodic sawtooth waveform, as shown in Fig. Q7 (b). (10 Marks)

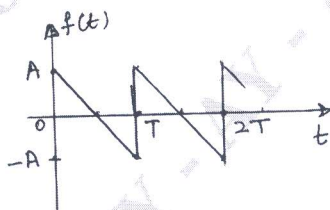


Fig. Q7 (b)

- 8 a. A voltage pulse, of unit height and width T is applied to the circuit in the Fig. Q8 (a) at  $t = 0$ . Determine the voltage across the capacitance C as a function of time. (10 Marks)

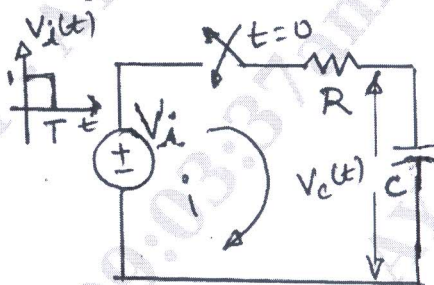


Fig. Q8 (a)

- b. Determine the Laplace transform of waveform given in Fig. Q8 (b). (10 Marks)

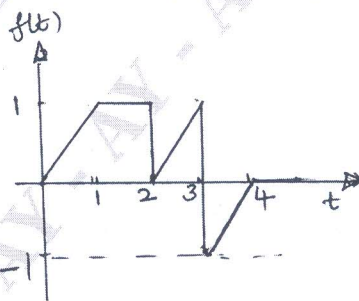


Fig. Q8 (b)

- 9 a. With respect to series resonant circuit, show that resonant frequency is equal to the geometric mean of two half power frequencies. (08 Marks)
- b. A series resonant circuit includes  $1 \mu\text{F}$  capacitor, resistance of  $16 \Omega$  and an inductance of L henry. If the bandwidth is  $500 \text{ rad/sec}$ , determine (i)  $\omega_r$  (ii) Q (iii) L. (06 Marks)

- c. Find the value of  $L$  for which the circuit resonates at a frequency of  $1000 \text{ rad/sec}$  for the circuit in the Fig. Q9 (c). (06 Marks)

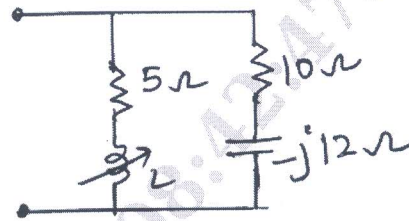


Fig. Q9 (c)

- 10 a. Derive  $Z$ -parameters in terms of hybrid parameters. (08 Marks)  
 b. Determine the  $Z$ -parameters of the network shown in Fig. Q10 (b). (06 Marks)

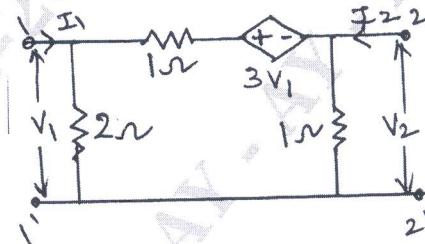


Fig. Q10 (b)

- c. For the network shown in Fig. Q10 (c), find the  $Y$  parameters. (06 Marks)

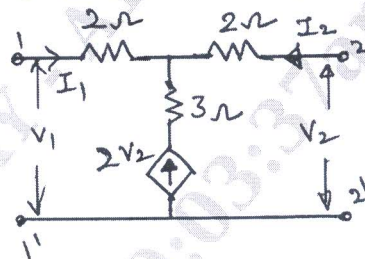


Fig. Q10 (c)

\*\*\*\*\*