

# CBCS SCHEME

15EC34

USN

## Third Semester B.E. Degree Examination, July/August 2021 Network Analysis

Time: 3 hrs.

Max. Marks:80

**Note: Answer any FIVE full questions.**

- 1 a. Calculate the voltage 'V' across  $20\Omega$  resistor for the circuit shown in Fig.Q1(a) using source transformation.

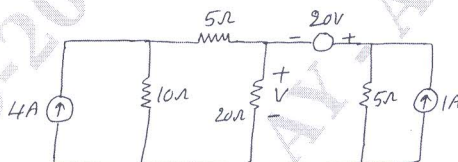


Fig.Q1(a) (08 Marks)

- b. Find the value of a single resistor to replace the network between terminals A and B of the network shown in Fig.Q1(b) using star-delta transformation.

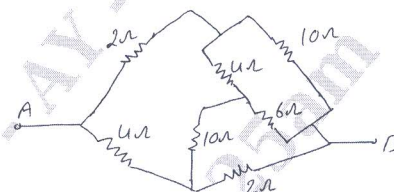


Fig.Q1(b) (08 Marks)

- 2 a. Determine the nodal voltages  $V_1, V_2, V_3$  for the networks shown in Fig.Q2(a).

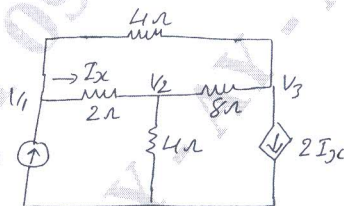


Fig.Q2(a) (08 Marks)

- b. In the circuit shown in Fig.Q2(b), determine  $V_2$ , which results zero current through  $4\Omega$  resistor using Mesh analysis.

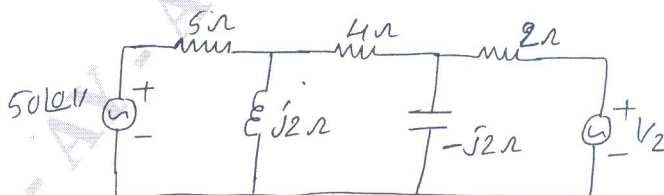


Fig.Q2(b) (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 3 a. Using Millman's theorem find the current through  $(2 + j3)\Omega$  impedance for the circuit shown in Fig.Q3(a).

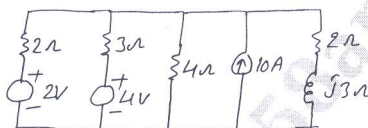


Fig.Q3(a)

(07 Marks)

- b. In the network shown in Fig.Q3(b), determine current in  $5\Omega$  resistor and then verify reciprocity theorem.

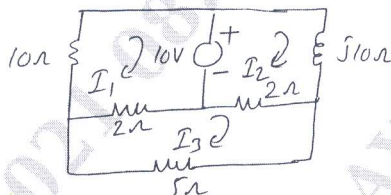


Fig.Q3(b)

(09 Marks)

- 4 a. Find the current following through  $7.5\Omega$  resistor using superposition theorem in the networks shown in Fig.Q4(a).



Fig.Q4(a)

(08 Marks)

- b. State Norton's theorem and find the current flowing through  $Z_L = 10 - j7.5$  connected across AB in the circuit shown in Fig.Q4(b) using North's theorem.

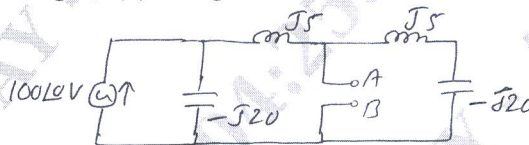


Fig.Q4(b)

(08 Marks)

- 5 a. In the circuit shown in Fig.Q5(a) switch 'K' is changed from position 1 to 2 at  $t = 0$ . Steady state condition having reached before switching. Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ .

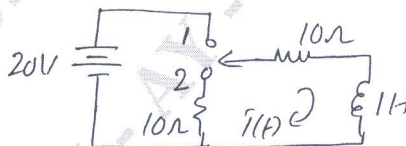


Fig.Q5(a)

(08 Marks)

- b. For the circuit given in Fig.Q5(b) steady state is reached with switch 'K' open and at  $t = 0$  switch is closed. Find the values of  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0^+$ .

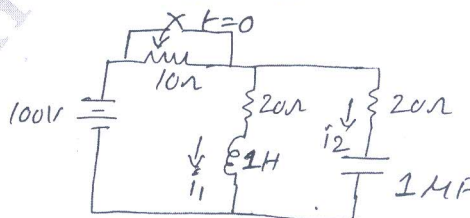


Fig.Q5(b)

(08 Marks)

- 6 a. For the circuit shown in Fig.Q6(a) obtain the equation for  $i_1(t)$  and  $i_2(t)$  when the switch is closed at  $t = 0$ . Use Laplace transforms.

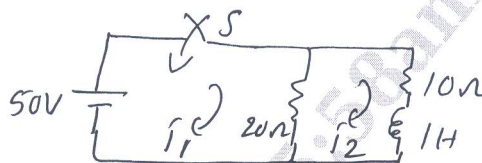


Fig.Q6(a)

(08 Marks)

- b. Obtain the Laplace transform of the function shown in Fig.Q6(b).

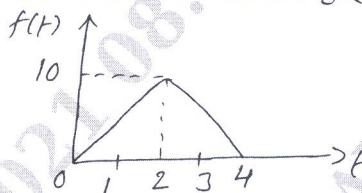


Fig.Q6(b)

(08 Marks)

- 7 a. Define the following terms : i) Resonance ii) Q – Factor  
 iii) Selectivity of series RLC circuit iv) Band width. (08 Marks)  
 b. A series RLC circuit consists of a  $50\Omega$  resistance,  $0.2H$  inductance and  $10\mu F$  capacitor with an applied voltage of  $20V$ . Determine the resonant frequencies. Find the Q – factor of the circuit. Compute the lower and upper frequencies limit and also the Band width of the circuit. (08 Marks)

- 8 a. For the circuit shown in Fig.Q8(a). Find the two values of capacitor for the resonance. Derive the formula used consider  $f = 50Hz$ .



Fig.Q8(a)

(08 Marks)

- b. Determine the value of RC in the network shown in Fig.Q8(b).

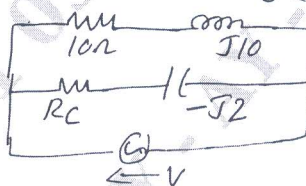


Fig.Q8(b)

(08 Marks)

- 9 a. Derive the Y-parameters in terms Z – parameters. (08 Marks)  
 b. Determine the admittance parameters of the 'T' networks shown in Fig.Q9(b).

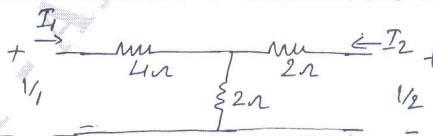


Fig.Q9(b)

(08 Marks)

- 10 a. Obtain the expression of Z-parameters in terms of transmission parameters. (08 Marks)  
 b. Determine T – parameters interms of Z – parameters and hence show that  $AD - BC = 1$ . (08 Marks)

\*\*\*\*\*