

# CBCS SCHEME

USN: 

--	--	--	--	--	--	--	--	--	--

17EE34

## Third Semester B.E. Degree Examination, Feb./Mar. 2022 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Explain the working of series positive clipper circuit which clips off positive part of the input above  $V_R$ . Draw the waveforms and transfer characteristics. Neglect  $V_f$ . (05 Marks)
- b. For the collector to base bias circuit  $V_{CC} = 10\text{ V}$ ,  $R_C = 4.7\text{ K}\Omega$ ,  $R_B = 220\text{ K}\Omega$  and  $\beta = 100$ . Calculate the location of Q-point. (05 Marks)
- c. For the fixed bias circuit, derive expressions for  $S_{I_{CO}}$ ,  $S_{V_{BE}}$  and  $S_{\beta}$ . Also obtain the relations between  $S_{I_{CO}}$  and  $S_{V_{BE}}$  and  $S_{I_{CO}}$  and  $S_{\beta}$ . (10 Marks)

### OR

- 2 a. Calculate the output voltage  $V_0$  for the clamper circuit as shown in Fig.Q2(a). The input voltage  $V_i$  is also shown. Frequency  $V_i = 1\text{ kHz}$ .

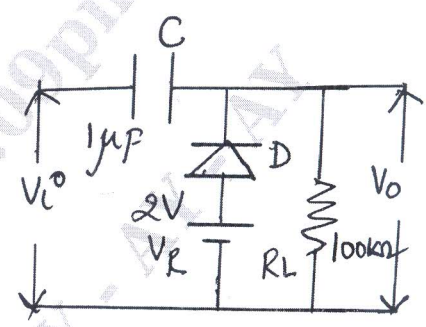
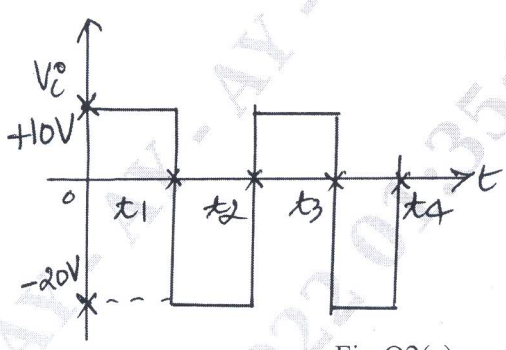


Fig.Q2(a)

- b. For the voltage divider bias circuit, derive expressions for  $S_{V_{BE}}$ . Also obtain the relation between  $S_{V_{BE}}$  and  $S_{I_{CO}}$ . (10 Marks)

### Module-2

- 3 a. For the transistor amplifier in general form, derive expressions for  $A_i$ ,  $Z_i$ ,  $A_v$ ,  $A_{vS}$ ,  $A_{iS}$  and  $Z_o$ . Use h-parameter model. (10 Marks)
- b. A single stage common emitter amplifier has  $R_S = 1\text{ K}\Omega$ ,  $R_L = 2\text{ K}\Omega$ ,  $R_1 = 50\text{ K}\Omega$ ,  $R_2 = 2\text{ K}\Omega$ ,  $R_C = 2\text{ K}\Omega$ ,  $h_{fe} = 50$ ,  $h_{ie} = 1.1\text{ K}\Omega$ ,  $h_{oe} = h_{re} = 0$ ,  $V_{CC} = 10\text{ V}$ ,  $R_E = 470\ \Omega$ ,  $C_E = 47\ \mu\text{F}$ ,  $C_1 = C_2 = 0.01\ \mu\text{F}$ . Draw the circuit diagram and determine  $A_i$ ,  $Z_i$ ,  $A_v$ ,  $A_{iS}$  and  $A_{vS}$  and  $Z'_o$ . (10 Marks)

### OR

- 4 a. Explain the working of common collector or emitter follower configuration. Develop expressions for  $A_i$ ,  $Z_i$ ,  $A_v$  and  $Y_o$  using approximate and exact hybrid model. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. For the amplifier circuit as shown in Fig.Q4(b),  $h_{fe} = 100$ ,  $h_{ie} = 3.37 \text{ K}\Omega$ ,  $h_{re} = h_{oc} = 0$ . Determine  $A_i$ ,  $Z_i$ ,  $A_v$ ,  $A_{is}$ .

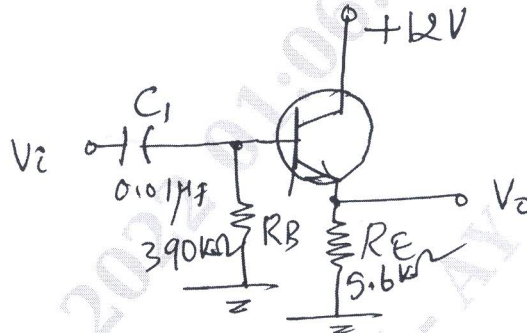


Fig.Q4(b)

(10 Marks)

**Module-3**

- 5 a. Draw the circuit of cascode amplifier. State its merits. Develop h-parameter model using approximate model. (08 Marks)
- b. Consider a 2-stage RC coupled CE-CE amplifier. The component values are  $R_S = 1 \text{ K}\Omega$ ,  $R_{C_1} = 15 \text{ K}\Omega$ ,  $R_{E_1} = 100 \Omega$ ,  $R_1 = 200 \text{ K}\Omega$ ,  $R_2 = 20 \text{ K}\Omega$ ,  $C_{E_1} = 47 \mu\text{F}$ ,  $C_1 = C_2 = 0.1 \mu\text{F}$  and for II stage  $R_{C_2} = 4 \text{ K}\Omega$ ,  $R_{E_2} = 330 \Omega$ ,  $C_{E_2} = 47 \mu\text{F}$ ,  $C'_1 = C'_2 = 0.1 \mu\text{F}$ , biasing resistors of II stage,  $R_3 = 47 \text{ K}\Omega$  and  $R_4 = 4.7 \text{ K}\Omega$ ,  $h_{ie} = 1.2 \text{ K}\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oc} = 25 \mu\text{A/V}$ . Determine the overall  $A_v$ ,  $A_{VS}$  and  $Z_o$ . Draw the circuit diagram and small signal circuit. (12 Marks)

OR

- 6 a. For the current series feedback topology, obtain expressions for  $R_{if}$  and  $R'_{of}$ . (10 Marks)
- b. For the voltage series feedback circuit of Fig.Q6(b), calculate  $A_v$ ,  $\beta$ ,  $D$ ,  $R_i$ ,  $R_{if}$ ,  $R_{of}$  and  $R'_{of}$ ,  $h_{fe} = 50$ . Draw the small signal model.

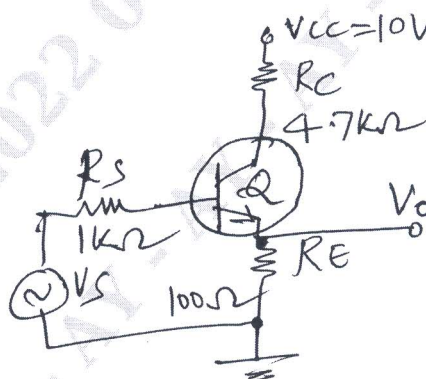


Fig.Q6(b)

(10 Marks)

**Module-4**

- 7 a. For the transformer coupled class-A amplifier, explain DC and AC operations, AC and DC, output and input power efficiency, maximum efficiency and power dissipation. (10 Marks)
- b. The input signal  $V_s$  is given by  $V_s = 1.75\sin(600t)$  is fed to a power amplifier and regulating o/p current is  $i_o = 15\sin 600t + 1.5\sin 1200t + 1.2\sin 1800t + 0.5\sin 2400t$ . Determine percentage increase in power due to distortion. (05 Marks)
- c. Explain cross-over distortion in class-B push pull amplifier. (05 Marks)

OR

- 8 a. Explain the expression for gain with feedback in oscillators. What is the value of  $A\beta$  to generate oscillations? Thus, explain principle of oscillations. (06 Marks)
- b. State Barkhausen criteria for sustained oscillations. (04 Marks)
- c. Derive an expression for frequency of oscillations in Colpitt's oscillator and  $h_{fe}$  min required for transistor. (10 Marks)

Module-5

- 9 a. Explain construction of n-channel D-MOSFET. Draw and explain transfer characteristics and drain characteristics. (10 Marks)
- b. Explain biasing for zero current drift and derive condition for zero drift. (10 Marks)

OR

- 10 a. For the JFET with fixed bias circuit, obtain expressions for  $Z_i$ ,  $Z_o$ ,  $A_v$ . Compare the result for exact analysis and when  $r_d \gg R_D$ . (10 Marks)
- b. For the JFET amplifier as in Fig.Q10(b), determine  $A_v$ ,  $Z_i$ ,  $Z_o$  and  $Z'_o$ . For FET,  $g_m = 2 \text{ mA/V}$ ,  $r_d = 10 \text{ K}\Omega$ .

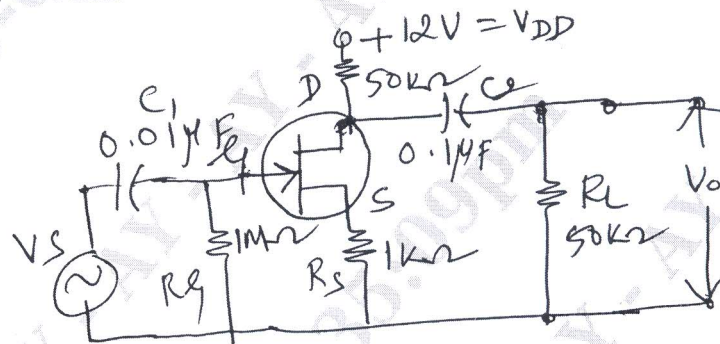


Fig.Q10(b)

(10 Marks)

\*\*\*\*\*