

USN

--	--	--	--	--	--	--	--	--	--

18EC34

**Third Semester B.E. Degree Examination, Feb./Mar. 2022**  
**Digital System Design**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Define and explain the combinational logic circuit along with block diagram. (06 Marks)  
b. Develop the canonical minterm and maxterm forms in decimal notation for the following Boolean functions:  
i)  $X = f(a, b, c, d) = \bar{a}b + c\bar{d}$   
ii)  $Y = f(a, b, c) = (\bar{a} + b)(b + \bar{c})$  (08 Marks)  
c. Simplify the following function using K-map method and also construct logic circuit for the simplified equation (function).  
 $Y = f(a, b, c, d) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13, 14)$ . (06 Marks)

**OR**

- 2 a. Simplify the following Boolean function by using Q-M method:  
 $X = f(a, b, c) = \sum(0, 1, 2, 3, 4, 5, 6)$ . (10 Marks)  
b. Design a combinational logic circuit for valid single digit BCD data, the output is 1 whenever a number is greater than 5 appears at the input. (05 Marks)  
c. Identify the PI and EPI for the following function:  
 $M = f(a, b, c, d) = \sum(1, 2, 3, 5, 7, 11, 12, 13, 14, 15)$ . (05 Marks)

**Module-2**

- 3 a. Draw and explain the circuit for 3 to 8 decoder. (06 Marks)  
b. Design and implement a full adder circuit using logic gates. (08 Marks)  
c. Write a short notes on PLD's and FPGA. (06 Marks)

**OR**

- 4 a. Define MUX and explain 4:1 MUX with the help of logic diagram using gates. (06 Marks)  
b. Explain 4-bit carry look-ahead adder with diagram. (08 Marks)  
c. Design and implement 1-bit comparator circuit. (06 Marks)

**Module-3**

- 5 a. Compare sequential circuit and combinational circuits. (06 Marks)  
b. Write a short notes on SR-latch. (06 Marks)  
c. Illustrate master-slave J-K flip-flop using NAND Gates. (08 Marks)

**OR**

- 6 a. Distinguish between synchronous and asynchronous counter. (06 Marks)  
b. Explain 4-bit universal shift register along with diagram. (08 Marks)  
c. Explain the working of clocked SR-FF using NAND Gates. (06 Marks)

**Module-4**

- 7 a. Explain Mealy and Moore model with diagrams. (10 Marks)  
 b. Design and develop Mod-6 synchronous counter using T-FF. (10 Marks)

**OR**

- 8 a. Construct the excitation table, transition table, state table and state diagram for the following sequential circuit. (Refer Fig.Q.8(a)). (14 Marks)

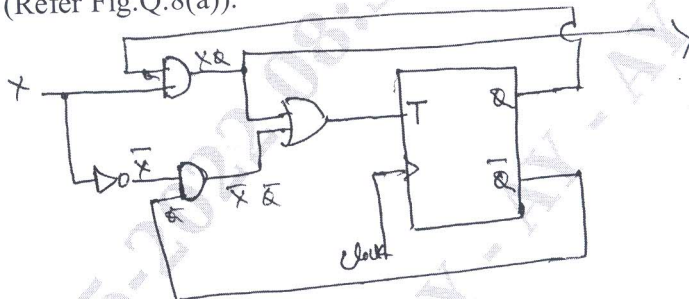


Fig.Q.8(a)

- b. List out the applications of shift registers along with brief explanation. (06 Marks)

**Module-5**

- 9 a. Explain the operation of serial adder with accumulator. (12 Marks)  
 b. Illustrate state assignment rules. (08 Marks)

**OR**

- 10 a. Write a short notes on:  
 i) Sequential circuit design steps (10 Marks)  
 ii) BCD to Ex-3 code convertor. (10 Marks)  
 b. Explain 4-bit Ring and Johnson counter along with diagram.

\*\*\*\*\*