

USN

--	--	--	--	--	--	--	--	--	--

17EC33

Third Semester B.E. Degree Examination, Feb./Mar. 2022
Analog Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Obtain the expressions for Z_i , Z_o and A_v for fixed bias transistor circuit using r_e model. (10 Marks)
- b. What is Darlington Connection? Calculate the DC bias voltage and currents in the Darlington emitter follower circuit given.

 


Fig.Q1(b)

- c. For a fixed bias circuit with $R_B = 330K\Omega$, $R_C = 2.7K\Omega$ and $V_{CC} = 8V$. Find Z_i , Z_o and A_v if transistor used has $h_{fe} = 120$, $h_{ie} = 1.175K\Omega$ and $h_{oe} = 20\mu A/v$. (05 Marks)

OR

- 2 a. Obtain expression for Z_i , Z_o and A_v for Emitter follower circuit (CC – configuration of transistor) with $r_o = \infty$. (10 Marks)
- b. For the voltage divider bias circuit with $R_1 = 56K\Omega$, $R_2 = 8.2K\Omega$, $R_C = 6.8K\Omega$, $R_E = 1.5K\Omega$. Find : Z_i , Z_o and A_v if transistor used has $h_{fe} = 120$, $h_{ie} = 1.175K\Omega$ and $h_{oe} = 20\mu A/v$. (06 Marks)
- c. Draw and explain Hybrid – II model of transistor in CE configuration. (04 Marks)

Module-2

- 3 a. Explain the construction and working of N-channel JFET. Also explain the drain the transfer characteristics of JFET with neat diagrams. (10 Marks)
- b. The fixed bias configuration shown in Fig.Q3(b), has $V_{GSQ} = -2V$, $I_{DSS} = 10mA$, $I_{DQ} = 5.6mA$, $V_P = -8V$, $Y_{os} = 40\mu s$. Find Q_m , r_d , Z_i , Z_o and A_v .

 


Fig.Q3(b)

- c. With necessary equivalent circuit obtain the expression for Z_i , Z_o and A_v for self Bias configuration with Bypass capacitor of JFET. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 4 a. With necessary equivalent circuit obtain the expression for Z_i , Z_o and A_v for a JFET common gate configuration. (10 Marks)
- b. Find Z_i , Z_o and output voltage if $g_m = 2.6\text{mS}$ of both stages.

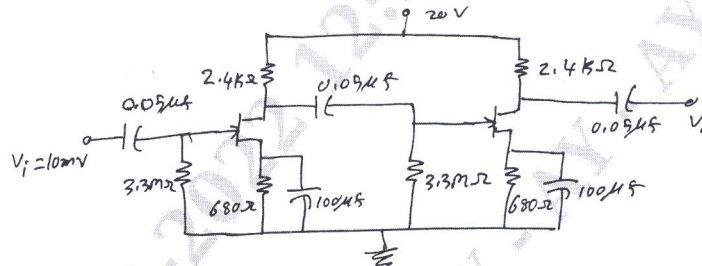


Fig.Q4(b)

(06 Marks)

- c. Identify the differences between enhancement and depletion MOSFET (any two). (04 Marks)

Module-3

- 5 a. What is Miller effect? Derive expression for Miller capacitance for an amplifier. (08 Marks)
- b. Determine f_{L_G} , f_{L_C} , f_{L_S} , f_{H_i} and f_{H_o} for the given FET amplifier circuit with $C_{w_i} = 5\text{pf}$, $C_{w_o} = 6\text{pf}$, $C_G = 0.01\mu\text{f}$, $C_C = 0.5\mu\text{f}$, $C_S = 2\mu\text{f}$, $I_{DSS} = 8\text{mA}$, $V_P = -4\text{V}$, $r_d = \infty$, $V_{DD} = 20\text{V}$, $V_{GS} = -2\text{V}$, $C_{gd} = 2\text{pf}$, $C_{gs} = 4\text{pf}$, $C_{ds} = 0.5\text{pf}$.

 


Fig.Q5(b)

(12 Marks)

OR

- 6 a. Derive the expressions for low frequency cut-offs for a voltage divider transistor with R_S and R_L . (08 Marks)
- b. The input power to a device is 10000W at a voltage of 1000V. The output power is 500W and the output impedance is 20Ω . Find : i) power gain in dB ii) voltage gain in dB. (04 Marks)
- c. For the given circuit of transistor amplifier find f_{β_1} , f_{H_i} and f_{H_o} . Given $r_0 = \infty$, $C_{be} = 36\text{pf}$, $C_{bc} = 4\text{pf}$, $C_{ce} = 1\text{pf}$, $C_{w_i} = 6\text{p}$, $C_{w_o} = 8\text{pf}$, and $r_c = 15.76\Omega$.

 


Fig.Q6(c)

(08 Marks)

Module-4

- 7 a. Derive expressions for voltage gain, Z_{if} and Z_{of} of voltage series feedback amplifier with necessary feedback connections. (08 Marks)
- b. With neat diagram and necessary expressions explain tuned Hartely Oscillators. Using transistor. (06 Marks)
- c. Describe the working of series crystal oscillator. (06 Marks)

OR

- 8 a. For a practical current series feedback circuit drive expression for A_{Vf} , Z_{if} and Z_{of} . (08 Marks)
- b. With neat diagram and necessary expressions explain : (12 Marks)
- Wien bridge Oscillator
 - UJT Oscillator.

Module-5

- 9 a. Calculate the efficiency of a transformer coupled class A amplifier for supply of 12V and output of $V_p = 6V$. (05 Marks)
- b. With neat diagram explain the working of transformer – coupled push – pull amplifier. (08 Marks)
- c. Describe with block diagram the series type of voltage regulator. (07 Marks)

OR

- 10 a. Calculate the output voltage and the Zener current in the regulator circuit given for $R_L = 1k\Omega$, $R = 220\Omega$, $V_z = 12V$, $\beta = 50$.

 


Fig.Q10(a)

- (05 Marks)
- b. Explain the working of class D amplifier with block diagram and necessary waveforms. (07 Marks)
- c. With necessary circuit diagram and characteristics curve, show that the maximum efficiency of a series fed class A amplifier is 25%. (08 Marks)
