

USN

--	--	--	--	--	--	--	--	--	--

17MT35

Third Semester B.E. Degree Examination, Feb./Mar.2022 Analog & Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define filter. List and explain the classification of filters. Also mention the advantages of active filter over passive filter. (10 Marks)
- b. With a neat sketch derive the expression for gain of a first order Butterworth high pass filter. Also draw the frequency response curve. (10 Marks)

OR

- 2 a. With a neat sketch demonstrate the operation of a narrow band reject filter and also write necessary equations with frequency response curve. (10 Marks)
- b. Design a wide band pass filter with outoff frequencies 200 Hz and 1 kHz and a pass band gain of 4. Also plot frequency response curve and calculate Q factor. (10 Marks)

Module-2

- 3 a. Derive the condition for oscillation with a block diagram. Also define oscillator. (10 Marks)
- b. With a neat circuit, illustrate the working of RC-phase shift oscillator with relevant equations. (10 Marks)

OR

- 4 a. With a neat circuit and input output waveform illustrate the working inverting comparator circuit. (10 Marks)
- b. Demonstrate the working of Schmitt Trigger. With neat circuit diagram and input output waveform. (10 Marks)

Module-3

- 5 a. With a neat sketch, explain the block diagram of 555 Timer. (10 Marks)
- b. With a neat sketch, explain the working of monostable multivibrator as frequency divider. (10 Marks)

OR

- 6 a. With a neat sketch, explain the working of 555 timer as Astable multivibrator. With relevant equations and waveforms. (10 Marks)
- b. Explain the working of Astable multivibrator as Free running ramp generator. (10 Marks)

Module-4

- 7 a. Simplify the following Boolean function $F = \overline{AC} + \overline{AB} + A\overline{BC} + BC$ using K map and also illustrate NAND and NOR gate realization of it. (10 Marks)
- b. Design a BCD to decimal decoder. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 8 a. Define MUX, Design a 4×1 multiplexer. Also implement the Boolean function $F(A,B,C) = \sum(1, 3, 5, 6)$ with a multiplexer. (10 Marks)
- b. With a neat circuit, illustrate the working of 2 to 4 line decoder. Also design a 4×16 decoder using 3×8 decoder. (10 Marks)

Module-5

- 9 a. Derive the characteristic equation for the following. Also write circuit and characteristic table:
(i) SR flip flop. (12 Marks)
(ii) D flip flop. (08 Marks)
- b. Design a 3 bit synchronous binary us counter..

OR

- 10 a. Design a BCD ripple counter. (12 Marks)
- b. Design a 3 bit binary ripple down counter. (08 Marks)

* * * * *