

# CBCS SCHEME

Library  
Learning Resource Centre  
AICTE Institute & Technology

USN

--	--	--	--	--	--	--	--	--	--

18ELN14/24

## First/Second Semester B.E. Degree Examination, July/August 2021 Basic Electronics

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions.**

- 1 a. Explain the operation of p-n junction Diode under unbiased condition with a neat diagram. (08 Marks)
- b. In a full wave rectifier, input is from  $30 - 0 - 30V$ . The load and  $R_f$  are  $100\Omega$  and  $10\Omega$  respectively. Calculate area voltage, efficiency, percentage regulation. (06 Marks)
- c. Determine  $I_D$ ,  $V_1$ ,  $V_2$  and  $V_0$  for the given circuit.

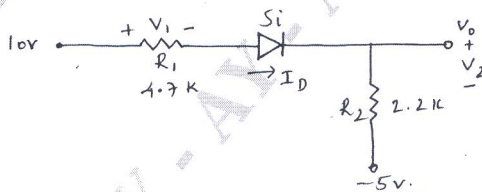


Fig.Q1(c)

(06 Marks)

- 2 a. With a neat diagram and waveforms explain the working of a bridge rectifier. (08 Marks)
- b. Explain the operation of a zener diode with line regulation and load regulation. (08 Marks)
- c. For a zener regulator shown in Fig.Q2(c), calculate the range of input voltage for which output remain constant.  $V_Z = 6.1V$ ,  $I_{Zmin} = 2.5mA$ ,  $I_{Zmax} = 25mA$ ,  $r_Z = 0\Omega$ .

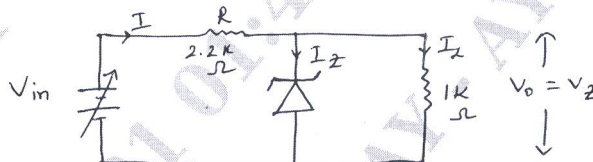


Fig.Q2(c)

(04 Marks)

- 3 a. Explain the characteristics of N-channel JFET (Drawn and transfer characteristics). (12 Marks)
- b. For a N-channel JFET,  $I_{DSS} = 8mA$ ,  $V_P = -5V$ . Find :
  - i)  $I_D$  @  $V_{GS} = -2V$  and  $-3V$
  - ii)  $V_{GS}$  @  $I_D = 3mA$  and  $5mA$ . (06 Marks)
- c. List out classification of FET with symbols. (02 Marks)

- 4 a. Draw and explain forward and reverse characteristics of an SCR. (07 Marks)
- b. Sketch the transfer and drain characteristics for an n-channel depletion - type MOSFET for the range of values of  $V_{GS} = -6V$  to  $+1V$  with  $I_{DSS} = 8mA$ ,  $V_P = V_{GS(off)} = -6V$ . (08 Marks)
- c. With a neat diagram, explain the 2 transistor model of SCR. (05 Marks)

- 5 a. Explain following with respect to OP-Amp.
  - i) Virtual ground      ii) CMRR      iii) Slew rate
  - iv) Offset voltage      v) Matched transistors. (10 Marks)
- b. Derive the expression for output voltage of an
  - i) integrator      ii) inverting summing amplifier. With a neat circuit diagram. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 6 a. Explain the ideal characteristics of an op-Amp. (08 Marks)  
 b. Derive the expression for output voltage of a non-inverting amplifier with a neat circuit and waveform. (08 Marks)  
 c. Design an adder circuit using an op-Amp to obtain output expression.  
 $V_0 = -2(0.1V_1 + 0.5V_2 + 20V_3)$ . (04 Marks)
- 7 a. Explain the operation of BJT as an amplifier and as a switch. (10 Marks)  
 b. Draw and explain the operation of a voltage series -ve feedback amplifier and derive an expression for its input impedance. (10 Marks)
- 8 a. Define an oscillator. Explain Barkhausen's criteria for oscillations with block diagram. (06 Marks)  
 b. Derive the expression for frequency of oscillations of Wien bridge oscillator. (08 Marks)  
 c. With a neat diagram, explain the working of RC phase shift oscillator. (06 Marks)
- 9 a. Subtract  $(111001)_2$  from  $(101011)_2$  using 2's complement method. (04 Marks)  
 b. State and prove De Morgan's theorem for 3 variables. (04 Marks)  
 c. Simplify the following Boolean expression :
- $A + \overline{AB} = A + B$
  - $\overline{XYZ} + \overline{XYZ} + \overline{XY} + \overline{XY}$
  - $\overline{\overline{XY} + \overline{XYZ} + X(Y + \overline{XY})}$
  - $ABC + A\overline{BC} + A\overline{BC} + \overline{ABC}$
  - $\overline{\overline{AB} + ABC} + A(B + \overline{AB})$
  - $AB + \overline{AC} + \overline{AB}C(AB + C)$ . (12 Marks)
- 10 a. With block diagram and truth table, explain the operation of full adder using 2 half adder. (08 Marks)  
 b. Explain the operation NOT, AND and OR gates using analogous switch equivalent circuit. (09 Marks)  
 c. Implement Ex - OR gate using only NOR gate. (03 Marks)

\*\*\*\*\*