

CBCS SCHEME

15ELN15/25

USN
 Learning Resource Centre
 Acharya Institute & Technology

First/Second Semester B.E. Degree Examination, Feb./Mar. 2022 Basic Electronics

Time: 3 hrs.

Max. Marks: 80


Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Draw and explain V-I characteristics of a Diode. (05 Marks)
- b. With a neat circuit diagram and waveforms, explain the working of Half-wave rectifier with capacitor filter. (05 Marks)
- c. Draw the Common – Emitter (CE) circuit and sketch the input and output characteristics and explain the different regions of operation of NPN transistor. (06 Marks)

OR

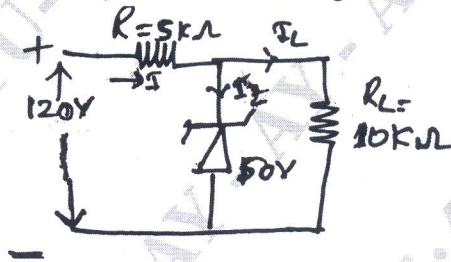- 2 a. Explain Zener diode voltage regulator with and without load. (08 Marks)
- b. For the circuit shown in Fig Q2(b), find : i) the output voltage ii) the voltage drop across series resistance iii) the current through the zener diode.



Given : input voltage : 120V
 $R = 5K\Omega$, $R_L = 10K\Omega$

I_L = load current
 I_z = zener current
 I = Total current.

Fig Q2(b)


(08 Marks)

Module-2

- 3 a. What is a DC-load line and explain with respect to NPN transistor. (04 Marks)
- b. Explain voltage – divider bias method with neat circuit and analysis. (08 Marks)
- c. Explain the practical characteristics of an opamp? (04 Marks)

OR

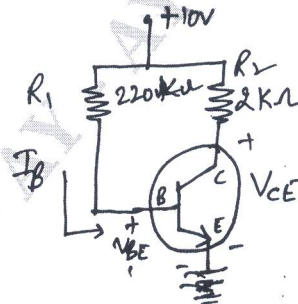- 4 a. Explain 3-input inverting summing amplifier and also derive the output voltage equation. (08 Marks)
- b. For the bias circuit shown in Fig Q4(b), find : i) I_{BQ} and I_{CQ} ii) V_{CEQ} iii) V_B , V_C iv) V_{BC} .



Given : $V_{BE} = 0.7V$
 $\beta = 60$
 $R_1 = 220K\Omega = R_B$
 $R_2 = 2K\Omega = R_C$

Fig Q4(b)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Convert the following :
- (i) $(3A.2F)_{16} = ()_{10} = ()_2$ (06 Marks)
- (ii) $(0.BF85)_{16} = ()_2 = ()_8$
- b. Perform the following using 1's and 2's complement techniques.
- (i) $(22)_{10} - (7)_{10}$ (ii) $(112)_{10} - (65)_{10}$ (06 Marks)
- c. State and prove De-Morgan's theorem using suitable truth table. (04 Marks)

OR

- 6 a. Design and Realize the Half – adder using NAND gates. (06 Marks)
- b. Simplify the following expressions :
- (i) $Y = \overline{(A+B)} (\overline{A+C}) (\overline{B+C})$ (08 Marks)
- (ii) $Y = ABC + A\overline{B}C + AB\overline{C} + \overline{A}BC$ (02 Marks)
- c. Draw Universal symbols of Basic and Universal gates.

Module-4

- 7 a. Differentiate latch and Flip-Flop. (02 Marks)
- b. Explain the operation of NAND – latch with symbol, circuit and truth table. (06 Marks)
- c. Explain the architecture of 8051 microcontroller. (08 Marks)

OR

- 8 a. Explain clocked RS-Flip-flop with symbol, circuit and truth table. (08 Marks)
- b. With neat block diagram, explain the working and operation of 8051 microcontroller based stepper motor. (08 Marks)

Module-5

- 9 a. What is Modulation? Why we need it? (04 Marks)
- b. Differentiate AM and FM. (04 Marks)
- c. Explain the working principle and operation of LVDT with suitable diagram. (08 Marks)

OR

- 10 a. Explain Frequency Modulation (FM) with help of neat waveforms. (06 Marks)
- b. Prove that $P_{\text{total}} = \left[\left(1 + \frac{m_a^2}{2} \right) P_C \right]$
- Where P_C = average carrier power
 m_a = modulation index (08 Marks)
- c. What are the applications of Thermistors. (02 Marks)

* * * * *