

**Sixth Semester B.E. Degree Examination, July/August 2022**

**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting atleast THREE questions from Part-A and any TWO questions from Part-B.**

**PART - A**

- 1 a. Mention the voltage requirements of an enhancement NMOSFET to work in different regions of operation. Derive an expression for current  $I_{ds}$  in linear region of operation with necessary diagrams. (10 Marks)
- b. Design the circuit of Fig.Q1(b) so that the FET operates at  $I_{ds} = 0.4 \text{ mA}$  and  $V_d = 0.5 \text{ V}$ . The NMOSFET has  $V_{tn} = 0.7 \text{ V}$ ,  $\mu_n CO_x = 100 \text{ } \mu\text{A/V}^2$ ,  $L = 1 \text{ } \mu\text{m}$ ,  $W = 32 \text{ } \mu\text{m}$  and  $V_{DD} = 2.5\text{V}$ .

 


Fig.Q1(b)

(10 Marks)

- 2 a. Explain the graphical derivation of CS MOSFET amplifier transfer characteristics with suitable diagrams. (10 Marks)
- b. Explain the working of single stage common gate MOSFET amplifier circuit. Define  $R_{in}$ ,  $V_o$ ,  $A_{V_o}$ ,  $A_V$  and  $G_V$  for the same circuit. (10 Marks)
- 3 a. Compare NMOSFET and BJT with respect to the following parameters:
  - (i) Active region voltage values
  - (ii) Current expression in the active region
  - (iii) Low frequency T-model
  - (iv) Transconductance  $g_m$(08 Marks)
- b. Explain with suitable diagram current mirror and current steering circuits. (08 Marks)
- c. Explain briefly cascade amplifiers. (04 Marks)
- 4 a. Design the current of Fig.Q2(a) to obtain an output current whose nominal value is  $100 \text{ } \mu\text{A}$ . Find  $R$  if  $Q_1$  and  $Q_2$  are matched and have channel lengths of  $1 \text{ } \mu\text{m}$ , channel widths of  $10 \text{ } \mu\text{m}$ ,  $V_t = 0.7 \text{ V}$  and  $k'_n = 200 \text{ } \mu\text{A/V}^2$ , what is the lowest possible value of  $V_0$ ? Assume  $V'_A = 20\text{V}/\mu\text{m}$ . Find the out resistance of the current source. Also find the change in output current resulting from a  $+1\text{V}$  change in  $V_0$ .

 


Fig.Q2(a)

(10 Marks)

- b. Explain the working of CMOS implementation of common source amplifier and define the voltage gain. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 5 a. Explain the operation of BJT differential pair configuration. (10 Marks)  
b. Explain the frequency response of current mirror loaded MOS differential pair circuit. (10 Marks)

**PART – B**

- 6 a. Explain how noise reduction and band-width extension can be achieved using negative feedback with necessary diagrams and expressions. (10 Marks)  
b. Explain the ideal structure of a series-series feedback amplifier with figures and expressions. (10 Marks)
- 7 a. Design an inverting op-amp circuit to form the weighted sum  $V_0$  of two inputs  $V_1$  and  $V_2$ . It is required that  $V_0 = -(V_1 + 5V_2)$ . Select values for  $R_1$ ,  $R_2$  and  $R_f$  so that for a maximum o/p voltage of 10V, the current in the f/b resistor will not exceed 1 mA. (06 Marks)  
b. Explain different amplifiers with neat diagrams. (08 Marks)  
c. Explain briefly Sample and Hold circuits. (06 Marks)
- 8 a. Explain the following characteristics of a logic family. (06 Marks)  
b. Write about the dynamic operation of CMOS inverter with necessary diagrams and expressions. (10 Marks)  
c. Draw the CMOS schematic and AOI implementation for  
$$Y = \overline{AB + CD}$$
 (04 Marks)

\* \* \* \* \*