Librarian Learning Resource Centre Acharya Institutes

GBGS SCHEME

USN							18EE36
		1	1			1	

Third Semester B.E. Degree Examination, July/August 2022 **Electrical and Electronic Measurements**

Time: 3 hrs. Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define sensitivity of galvanometer. Draw Wheatstone's bridge and derive balance equation.

 (08 Marks)
 - b. A Wheatstone Bridge has $P = 1K\Omega$, $Q = 100\Omega$, $R = 2005\Omega$ and S = 200. Find ΔR if bridge is not balanced. If the galvanometer sensitivity is (S_i) 10mm/ μA , applied voltage is 5V and internal resistance of galvanometer is 100Ω . Find the deflection of the galvanometer.

(12 Marks)

OR

- 2 a. Draw a neat circuit diagram and explain Desauty's modified bridge and derive relevant equation. (08 Marks)
 - b. Explain how Schering bridge can be used to measure relative permittivity of dielectric material. (08 Marks)
 - c. Explain fall of potential method of measuring earth resistance.

(04 Marks)

Module-2

- 3 a. Derive the torque equation of a dynamometer type of wattmeter. List the errors that occur in it. (08 Marks)
 - b. Explain:
 - i) Weston frequency meter
 - ii) Phase sequence indicators.

(12 Marks)

OF

- 4 a. Explain the construction and working of a single phase power factor meter. (08 Marks)
 - b. A 230V energy meter disc makes 10 revolutions when connected to a resistive load of 600W in 10 mins. Calculate the meter constant. (06 Marks)
 - c. Discuss the various adjustment required in energy meters for accurate reading. (06 Marks)

Module-3

- 5 a. What are shunts and multipliers and explain how they are used to extend instrument range derive relevant expressions. (08 Marks)
 - b. A moving coil meter gives full scale deflection with a current of 5mA. If the coil of the instrument has a resistance of 10Ω how can it be adopted to work as:
 - i) Ammeter of range (0 10A)
 - ii) Voltmeter of range (0 10V).

(08 Marks)

c. Explain turns compensation used instrument transformers.

(04 Marks)

OR

- 6 a. Draw a neat circuit diagram and explain Silbee's method of testing Current Transform (CT).
 - b. With the help of a neat circuit diagram explain how flux density can be measured in a ring specimen. (08 Marks)

Module-4

7 a. List the advantage of electronic instruments.

(04 Marks)

- b. Explain construction and working of:
 - i) True RMS reading voltmeter
 - ii) RAMP type digital voltmeter.

(16 Marks)

OR

- 8 a. Draw the block diagram of a electronic energy meter and explain its working. List its advantages. (12 Marks)
 - b. Explain the construction and working of a successive approximation type DVMS. (08 Marks)

Module-5

- 9 a. With relevant diagrams explain:
 - i) Seven segment displays
 - ii)Liquid crystal displays.

(08 Marks)

b. Explain the working of Cathode Ray Tube (CRT) with a neat diagram.

(08 Marks)

c. What are Bar graph displays and where are they used?

(04 Marks)

OR

10 a. List the different types of recording devices and explain LVDT and strip chart types.

(10 Marks)

- b. Explain the following:
 - i) Nixie tubes
 - ii) ECG.

(10 Marks)