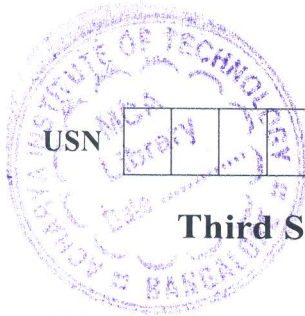


CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

15MT35

Third Semester B.E. Degree Examination, July/August 2022 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks:80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the V-I characteristics of an Ideal diode, silicon diode, Germanium diode and zener diode. (08 Marks)
- b. Explain junction diode models with necessary equivalent circuits. (08 Marks)

OR

- 2 a. Explain, with diagrams, how a pn-junction diode can be used as a switch. (06 Marks)
- b. Explain how the capacitor filter reduces the ripple in rectifier circuit. (06 Marks)
- c. The input voltage of centre tapped full wave rectifier is 10 V (rms). The sum of the dc resistance of the transformer winding and forward dc resistance of the diode is $R_s = 0.2\Omega$, the load resistance $R_L = 10\Omega$ and forward diode drop $V_D = 0.7$ V, Find :
 - i) Peak load current
 - ii) DC load current.
 - iii) Individual diode dc current.
 - iv) DC output voltage.
 - v) PIV. (04 Marks)

Module-2

- 3 a. Explain first order low pass Butterworth filter and derive the gain and phase angle equations. (08 Marks)
- b. Design a wide band pass filter with $f_L = 200\text{Hz}$, $f_H = 1\text{KHz}$
 - i) passband gain = 4
 - ii) draw the frequency response of the filter
 - iii) calculate the value of Q for the filter. (08 Marks)

OR

- 4 a. Explain second order high pass Butterworth filter with necessary circuit diagram and equations. (04 Marks)
- b. Design Wein bridge oscillator for the Fig.Q4(b) below so that $f_0 = 965\text{Hz}$. (04 Marks)

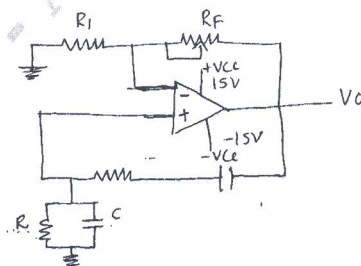


Fig.Q4(b)

- c. State Backhausen criterion for sustained oscillations and explain phase shift oscillator with necessary circuit and equations. (08 Marks)

Module-3

- 5 a. With the help of circuit diagram explain op-amp as a basic comparator and zero crossing detector. (08 Marks)
b. Explain the operation of a inverting Schmitt trigger. Draw its input and output waveforms. (08 Marks)

OR

- 6 a. Explain the operation of a monostable multivibrator and its applications. Draw its input output waveforms. (08 Marks)
b. Explain the operation of 555 timer as a Astable multivibrator with circuit diagram and its applications. (08 Marks)

Module-4

- 7 a. Draw Rs latch with NAND and NOR gate circuit. (04 Marks)
b. Explain clocked master/slave JK flip-flop with necessary logic circuit. (06 Marks)
c. Explain bi – directional shift register with parallel load. (06 Marks)

OR

- 8 Explain 3 – bit synchronous – Binary up-down counter. (08 Marks)
Explain how read and write information transfer takes place in magnetic core-memory. (08 Marks)

Module-5

- 9 a. What is multiplexer? Realize 4 : 1 multiplexer using basic gates and write its truth table. (08 Marks)
b. Explain the operation of R-2R DAC. And also derive the expression of output voltage. (08 Marks)

OR

- 10 a. What is decoder? Realize 2 to 4 line decoder using basic gates and write its truth table. (08 Marks)
b. Explain the operation of a successive approximation ADC. (08 Marks)

* * * * *