

OR

- 6 a. Write short notes on three state buffers. (06 Marks)
b. Design 7-segment decoder using PLA. (06 Marks)
c. Construct 8 : 1 mux using only 2 : 1 mux. (08 Marks)

Module-4

- 7 a. Given that $A = "00101101"$ and $B = "10011"$. Determine the value of F
 $F \leq \text{not } B \& "0111" \text{ or } A \& "1" \text{ and } "1" \& A$ (04 Marks)
b. Write the complete VHDL code for 4 bit binary adder. (08 Marks)
c. Explain how the VHDL code can be compiled simulated and synthesized with example. (08 Marks)

OR

- 8 a. Explain T Flip Flop with truth table. (07 Marks)
b. Explain Master-Slave JK flip flop with neat diagram. (08 Marks)
c. Write short notes on switch debouncing with an SR Latch. (05 Marks)

Module-5

- 9 a. Explain 8 bit serial in serial out shift register. (10 Marks)
b. Explain n bit parallel adder with accumulator. (10 Marks)

OR

- 10 a. Design and explain mod 8 synchronous counter using JK flip flop. (10 Marks)
b. Explain how moore transition and states can be constructed with examples. (10 Marks)
