 


# CBCS SCHEME

15EE34



## Third Semester B.E. Degree Examination, Jan./Feb. 2023 Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Define clipping and clamping circuits. Explain type of clamping circuits. (08 Marks)
- b. What is biasing of a transistor? Explain the factors that affect selection of Q-pt anywhere in the active region for the transistor to operate as an amplifier. (08 Marks)

OR

- 2 a. Derive the expression for stability factors for fixed bias circuit with respect to  $I_{CO}$ ,  $V_{BE}$  and  $\beta$ . (08 Marks)
- b. Define fixed bias circuit and explain with neat diagram. (08 Marks)

### Module-2

- 3 a. State and prove Miller's theorem. (04 Marks)
- b. Calculate the overall lower 3db and upper 3db frequency for a 3 stage amplifier having an individual frequency  $f_1 = 40\text{hz}$  and  $f_2 = 2\text{MHz}$ . (04 Marks)
- c. Derive the expression for Miller's effect capacitances. (08 Marks)

OR

- 4 a. Define h-parameters and hence derive h-parameter model of a CE-BJT. (08 Marks)
- b. A voltage source of negligible internal resistance drives a common collector transistor amplifier. The load resistance is  $2500\Omega$ . The transistor h-parameters are  $h_{ie} = 1000\Omega$ ,  $h_{re} = 1$ ,  $h_{fe} = -50$  and  $h_{oe} = 25\mu\text{A/V}$ , compute  $A_i$ ,  $A_v$ ,  $Z_i$  and  $Z_o$ . (08 Marks)

### Module-3

- 5 a. Explain the need of cascading amplifier, 'Draw and explain the Block diagram of two stage cascade amplifier. (08 Marks)
- b. With block diagram, explain the concept of feedback amplifier. (08 Marks)

OR

- 6 a. List general characteristics of negative feedback amplifier. (04 Marks)
- b. Determine the voltage gain input and output independence with feedback for voltage series having  $A = -100$ ,  $R_i = 10\text{K}\Omega$  and  $R_o = 20\text{K}\Omega$  for feedback  $\beta = -0.1$ . (06 Marks)
- c. A 2-stage cascade amplifier system is built with stage voltage gains 25 and 40. Both stages have the same bandwidth of  $220\text{KHz}$  with identical lower cutoff frequency of  $500\text{Hz}$ . Find the overall gain bandwidth product. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-4**

- 7 a. With a neat diagram, explain the working of a complementary symmetry class-B amplifier. (08 Marks)
- b. A class – B push pull amplifier operating with  $V_{CC} = 25V$  provides a 22V peak signal to an  $8\Omega$  load. Find peak load current, dc current drawn from the supply, input power, output power, circuit efficiency, power dissipation. (08 Marks)

OR

- 8 a. A crystal has the following parameter  $L = 0.3344$ ,  $CM = 1pF$ ,  $C = 0.065pF$  and  $R = 5.5k\Omega$ . Calculate the series Resonant frequency, parallel resonant frequency and find the Q- of the crystal. (08 Marks)
- b. With a neat diagram, explain RC phase shift oscillator and write differentiate between RC phase shift oscillator and wein bridge oscillator. (08 Marks)

**Module-5**

- 9 a. Draw the JFET amplifier using fixed bias configuration. Derive  $Z_i$ ,  $Z_o$   $A_v$  using small signal model. (08 Marks)
- b. Determine  $V_{GSQ}$ ,  $I_{DQ}$  and  $V_{DS}$ ,  $V_D$  for circuit shown in Fig. Q9(b).


 


Fig. Q9(b)

(08 Marks)

OR

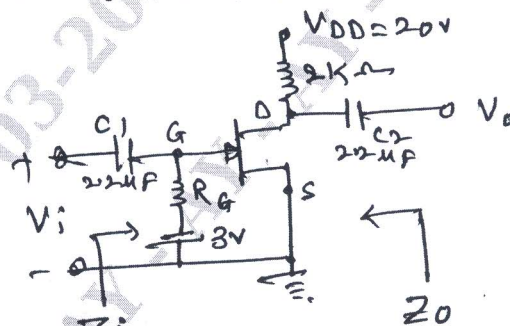- 10 a. Compare FET over BJT. (04 Marks)
- b. With necessary equivalent circuit obtain the expression for  $Z_i$  and  $A_v$  for a JFET. Common gate configuration. (06 Marks)
- c. For the JFET amplifier shown in below Fig Q10(c). Calculate:  
 i)  $g_m$  ii)  $r_d$  iii)  $Z_i$  iv)  $Z_o$  v)  $A_v$ .



$I_{DSS} = 5mA$   
 $V_P = -6V$   
 $Y_{DS} = 40\mu S$   
 $V_{GSQ} = -3V$   
 $R_G = 2m\Omega$

Fig Q10(c)

(06 Marks)

\*\*\*\*\*