

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EE35

Third Semester B.E. Degree Examination, Jan./Feb. 2023

Digital System Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Show that $a'c + b'c' + ab = a'b' + bc + ac'$. (06 Marks)
- b. The 4 inputs to a circuit (A, B, C, D) represent an 8 4 2 1 binary coded decimal digit. Design the circuit so that the output (z) is 1 if the decimal number represented by the inputs is exactly divisible by 3. Assume that only valid BCD digits occur as inputs. (10 Marks)

OR

- 2 a. Simplify the following expression using K-Map.
- i) $f(A, B, C, D) = \pi M(0, 2, 3, 8, 9, 12, 13, 15)$
- ii) $f(w, x, y, z) = \Sigma m(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$. (08 Marks)
- b. Use Quine-McCluskey method and simplify the following function :
 $f(a, b, c, d) = \Sigma m(0, 1, 2, 3, 8, 9)$. (08 Marks)

Module-2

- 3 a. Implement full subtractor using a decoder and write a truth table. (06 Marks)
- b. Explain the design procedure for combinational circuits. (06 Marks)
- c. Write short notes on Encoder. (04 Marks)

OR

- 4 a. Explain look ahead carry adder. (10 Marks)
- b. Design 16 : 1 MUX using 8 : 1 MUX. (06 Marks)

Module-3

- 5 a. With a neat logic diagram explain working of a master slave JK flip-flop along with waveform. Also brief about race around condition. (08 Marks)
- b. What is the difference between a flip-flop and a latch? With logic diagram and truth table, explain the operation of gated SR latch. (08 Marks)

OR

- 6 a. Convert D flip-flop to SR flip-flop. (08 Marks)
- b. Design mod 6 ripple counter using T flip-flops. (08 Marks)

Module-4

- 7 a. With a suitable example, explain Mealy and Moore model in a sequential circuit analysis. (08 Marks)
- b. Construct transition table, state table and state diagram for the given sequential circuit.

 


Fig.Q7(b)

(08 Marks)

OR

- 8 a. Design synchronous mod 6 counter using D flip-flop to generate the sequence : (0, 2, 3, 6, 5, 1, 0 ---). (08 Marks)
- b. Describe the following terms with respect to sequential machines :
- State
 - Present state
 - Next state
 - State diagram.

(08 Marks)

Module-5

- 9 a. Write the comparison between VHDL and verilog. (08 Marks)
- b. Explain various data types available in VHDL.s (08 Marks)

OR

- 10 a. Explain the following :
- Signal declaration and assignment statements
 - Concurrent signal assignment statements.
- b. Explain shift and rotate operator in HDL with an example. (08 Marks)

(08 Marks)
