

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC33

Third Semester B.E. Degree Examination, Dec.2023/Jan.2024 Analog Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. For a common Emitter with voltage divider bias, derive the expression for voltage gain, input impedance and output impedance sign re model. (10 Marks)
- b. For the networks shown in Fig.Q1(b).
 - i) Determine
 - ii) Find Z_i (with $r_0 = \infty$)
 - iii) Calculate Z_0 (with $r_0 = \infty$)
 - iv) Determine A_V (with $r_0 = \infty$)

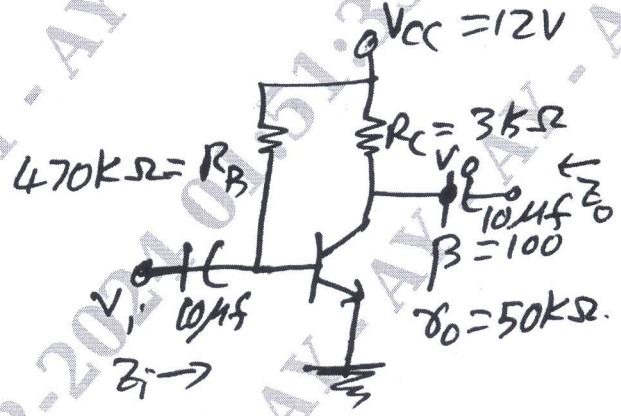


Fig.Q1(b)

(10 Marks)

OR

- 2 a. Draw the complete hybrid equivalent (h-parameters model) circuit of two part networks for BJT and obtain equation for voltage gain and current gain. (10 Marks)
- b. Draw circuit of Hybrid π -model of transistor and mention various parameters. (10 Marks)

Module-2

- 3 a. Explain construction and characteristics of n-channel JFET. (08 Marks)
- b. Explain transfer characteristics of FET and mention the required equation. (08 Marks)
- c. Mention differences between depletion type and enhancement type MOSFET. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 4 a. Draw the circuit of common source voltage divider using JFET and derive the expression for Z_i , Z_o and A_v . (10 Marks)
- b. The self-bias configuration has operating point at $V_{GS} = -2.6V$, $I_{Dn} = 2.6mA$. The circuit is a shown in Fig.Q4(b). Determine : i) g_m ii) r_d iii) Z_i iv) Z_o v) A_v without r_d .

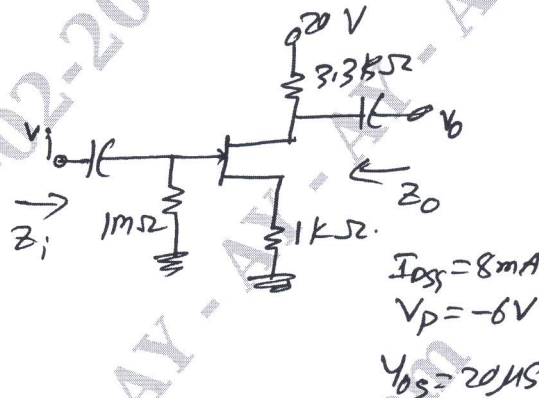


Fig.Q4(b)

(10 Marks)

Module-3

- 5 a. Derive expression for lower cut-off frequency w.r.t C_g and mention the effect of C_C and C_E frequency. (08 Marks)
- b. For FET amplifier circuit determine lower cut off frequency and sketch frequency response curve using the following parameters :
- | | | | |
|---------------------|----------------------|------------------------|-------------------------|
| $C_Q = 0.01\mu f$, | $C_C = 0.5\mu f$, | $C_S = 2\mu f$, | $R_{Sig} = 10K\Omega$, |
| $R_G = 1m\Omega$, | $R_D = 4.7K\Omega$, | $R_S = 1K\Omega$, | $R_L = 2.2K\Omega$, |
| $I_{DSS} = 8mA$, | $V_P = -4V$, | $r_d = \infty\Omega$, | $V_{DD} = 20V$. |
- (12 Marks)

OR

- 6 a. Draw high frequency ac equivalent circuit of FET amplifier and obtain higher cut off frequency for i/p and o/p. (12 Marks)
- b. With the help of suitable equations and neat diagram, explain the multistage frequency effect. (08 Marks)

Module-4

- 7 a. Draw the block diagram of voltage series feedback amplifier and derive the expression for gain with feedback, i/p and o/p impedances. (10 Marks)
- b. Determine the voltage gain, i/p and o/p impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10K\Omega$, $R_o = 20K\Omega$, for feedback factor of $B = -0.1$. (06 Marks)
- c. State the merits of -ve feed back in amplifier. (04 Marks)

OR

- 8 a. Draw the circuit of phase shift oscillator using JFET and explain its operation. Also mention the equation of for frequency of oscillations. (10 Marks)
- b. Draw the circuit of Wien Bridge oscillator and derive the expression for frequency of oscillation. Also explain the circuit connection and working. (10 Marks)

Module-5

- 9 a. Draw the circuit of series fed class-A amplifier and derive the expression for maximum efficiency with operation. (10 Marks)
- b. Define harmonic distortion and calculate the harmonic distortion components for an o/p signal having the fundamental amplitude of 2.5V, second harmonic amplitude of 0.25V, third harmonic of 0.1V and fourth harmonic amplitude of 0.05V, also find total harmonic distortion. (10 Marks)

OR

- 10 a. With the help of a block diagram, explain short voltage regulation and also explain how the same can be implemented using BJT. (12 Marks)
- b. Calculate the output voltage and the zener current in the regulator circuit. Refer Fig.Q10(b).

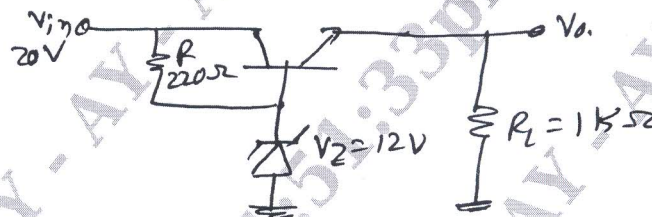


Fig.Q10(b)

(08 Marks)
