

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--	--

18EE62

Sixth Semester B.E. Degree Examination, Dec.2023/Jan.2024 Power System Analysis – I

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Show that the per unit impedance of a transformer is the same irrespective of the side on which it is calculated. (04 Marks)
- b. A 300 mVA, 20 kV, 3 ϕ generator has a reactance of 20%. The generator supplies two motors m_1 and m_2 over a transmission line of 64 km having transformers at both ends as shown in Fig. Q1 (b). The transformer T_1 is a 3-phase transformer and T_2 is composed of 3 single phase transformers of rating 100 mVA each, 127 KV/13 KV, 10% reactance. The series reactance of transmission line is 0.5 ohm/km. Draw the reactance diagram with all reactances marked in per unit. Select the generator rating as base values.

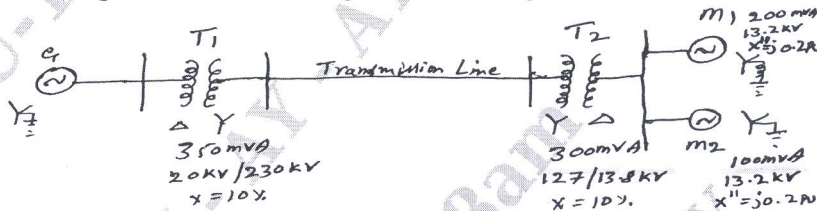


Fig. Q1 (b)

(10 Marks)

- c. How is the per unit impedance value in a given base are changed to per unit impedance value on new base? (06 Marks)

OR

- 2 a. Draw the equivalent circuit models of synchronous generator, transmission line and two winding transformer. (06 Marks)
- b. What is per unit quantity and mention the advantages of per unit quantities? (04 Marks)
- c. The one-line diagram of an unloaded generator is as shown in Fig. Q2 (c). Choose a base of 50 mA, 13.8 kV in the circuit of generator G_1 . The ratings are as follows :

- G_1 : 20 mVA, 13.8 KV, $X'' = 0.2 P.U$
 G_2 : 30 mVA, 18 KV, $X'' = 0.2 P.U$
 G_3 : 30 mVA, 20 KV, $X'' = 0.2 P.U$
 T_1 : 25 mVA, 220 KV Y/13.8 kV Δ , $X = 10 \%$.
 T_2 : 30 mVA, 220 KV Y/18 kV Δ , $X = 10 \%$.
 T_3 : 35 mVA, 220 KV Y/22 kV Y, $X = 10 \%$.

Draw the per unit reactance diagram.

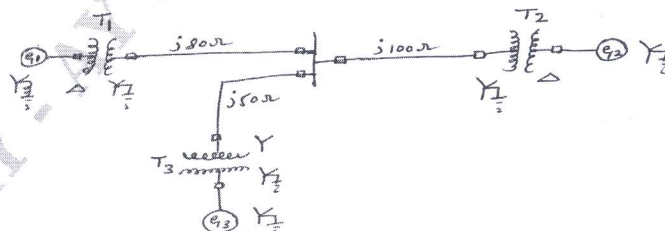


Fig. Q2 (c)

(10 Marks)

1 of 4

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. Explain clearly, how the circuit breakers are rated. (08 Marks)
 b. A three phase, 5 mVA, 6.6 kV alternator with reactance of 8% is connected to a feeder of series impedance of $(0.12+j0.48)$ ohm/phase/km. The transformer is rated at 3 mVA, 6.6 KV/33KV and has a series reactance of 5%. Determine the fault current supplied by the generator operating under no load with a voltage of 6.9 kV, when a three-phase symmetrical fault occurs at a point 15 km along the feeder. Choose base mVA as 5 mVA,

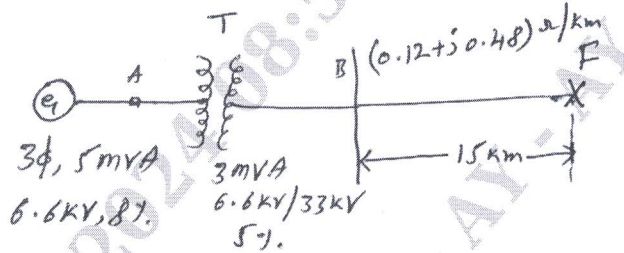


Fig. Q3 (b)

(12 Marks)

OR

- 4 a. With the oscillogram of the short circuit current of a synchronous machine, distinguish between subtransient, transient and steady state reactances. Also, show that $X''_d < X'_d < X_d$ with equivalent circuit diagram. (08 Marks)
 b. For the radial network shown in Fig. Q4 (b), a three phase fault occurs at F. Determine the fault current under fault conditions. Choose the base of 100 mVA and base kV of 33 kV in the overhead line.

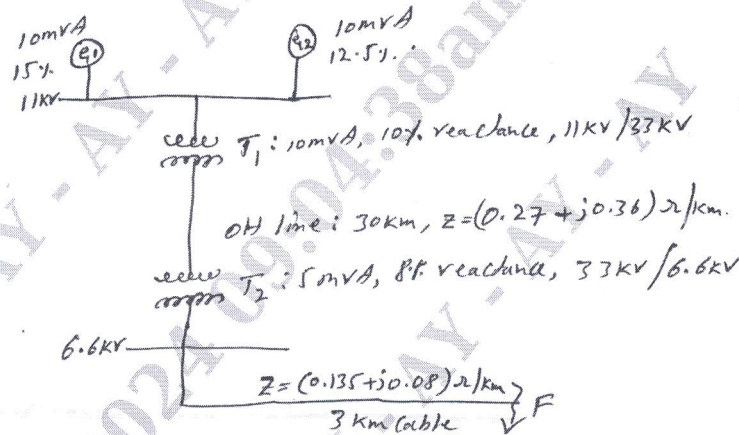


Fig. Q4 (b)

(12 Marks)

Module-3

- 5 a. Derive the expression for symmetrical components of voltages in terms of phase voltages. (08 Marks)
 b. Draw the zero sequence impedance networks of a transformer for the following connections:
 (i) $\Delta - \Delta$
 (ii) $Y - Y$
 (iii) $Y - \Delta$ (06 Marks)
 c. A balanced delta connected load is connected to a three phase symmetrical supply. The line currents are each 10 A. If fuse in one of the line is blown out, determine the sequence components of line current. (06 Marks)

