

CBCS SCHEME

BCS302



Third Semester B.E./B.Tech. Degree Examination, June/July 2024 Digital Design and Computer Organization

Time: 3 hrs.

Max. Marks: 100

- Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M : Marks, L: Bloom's level, C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Reduce the following Boolean expressions to the minimum number of literals. i) $x(x' + y)$ ii) $x + x'y$ iii) $(x + y)(x + y')$ iv) $xy + x'z + yz$ v) $(x + y)(x' + z)(y + z)$	10	L3	CO1
	b.	Determine the minimum SOP form using Karnaugh Map $F = A'B'C' + B'CD' + A'BCD' + AB'C'$.	10	L3	CO1
OR					
Q.2	a.	Simplify the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ which has the don't care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$	10	L3	CO1
	b.	Simplify and implement the following Boolean function using NAND gates $F(x, y, z) = (1, 2, 3, 4, 5, 7)$.	10	L3	CO1
Module – 2					
Q.3	a.	Implement the design of combinational circuit BCD and excess 3 code converter.	10	L2	CO2
	b.	Implement full adder circuit using 3:8 decoders.	10	L2	CO2
OR					
Q.4	a.	With Truth table and K-map simplification, implement the full adder with basic gates and using two half adders an OR gate.	10	L2	CO2
	b.	Realize the Boolean function using 8:1 multiplexer $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$.	10	L2	CO2
Module – 3					
Q.5	a.	Explain Bus structure with diagram, explain how different peripherals connected to the bus.	10	L2	CO3
	b.	Explain in detail about the word alignment of a machine (microprocessor based systems) what is the consecutive addresses of aligned words for 16, 32 and 64 bit word length of the machine? Give consecutive address for each of the following specified above.	10	L2	CO3
OR					
Q.6	a.	Write a note on : i) Register Transfer Notation (RTN)	10	L2	CO3

	b.	Illustrate an indexed addressing mode with a assembly language program to find the sum of the Test 1, Test 2 and Test 3 scores of the N number of students.	10	L2	CO3
Module – 4					
Q.7	a.	Explain Hardware interrupt, enabling/disabling of interrupts and sequence of events in handling interrupt request from a single device.	10	L2	CO4
	b.	Explain memory mapped I/O and I/O interface for an input device with a diagram.	10	L2	CO4
OR					
Q.8	a.	Describe DMA with its register and controllers.	10	L2	CO4
	b.	Explain the effect of size, cost and speed in memory Hierarchy.	10	L2	CO4
Module – 5					
Q.9	a.	Explain the process of Fetching word from memory in processor.	10	L2	CO5
	b.	With a diagram, explain the single bus organization of the data path inside a processor.	10	L2	CO5
OR					
Q.10	a.	Describe how an ALU perform on arithmetic and logic operation along with input gating diagrams.	10	L2	CO5
	b.	Explain the complete set of operations involved in executing the instruction Add (R ₃) R ¹ along with control sequence.	10	L2	CO5
