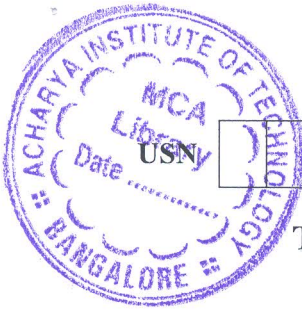


# CBCS SCHEME



--	--	--	--	--	--	--	--

21EE33

## Third Semester B.E. Degree Examination, June/July 2024 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Define the following networks with example :
  - i) Linear and Nonlinear Network
  - ii) Bilateral and Unilateral Network
  - iii) Active and Passive network. (06 Marks)
- b. Using source transformation, determine the power delivered by 50 V source in given network Fig.Q1(b) below.

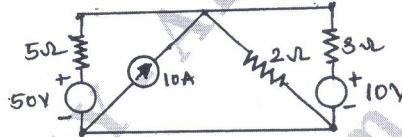


Fig.Q1(b)

(07 Marks)

- c. Determine  $I_x$  and  $V_x$  for the circuit shown in Fig.Q1(c) below, using mesh analysis.

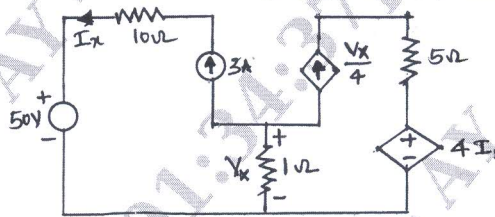


Fig.Q1(c)

(07 Marks)

### OR

- 2 a. Obtain expressions to convert star connected impedances into equivalent delta connected impedances. (06 Marks)
- b. Explain the concept of supermesh using network and also mention steps to apply Mesh analysis. (07 Marks)
- c. Determine the power dissipation in 10 ohm resistor using nodal analysis, shown in Fig.Q2(c).

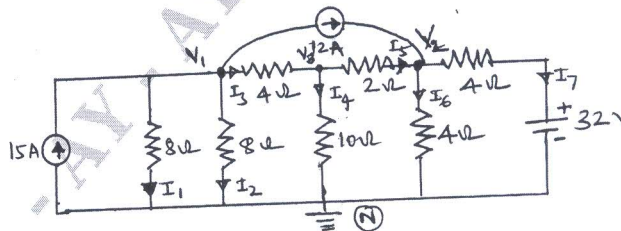


Fig.Q2(c)

(07 Marks)

### Module-2

- 3 a. State Thevenin's theorem. Explain it with the help of networks. Mention the steps to apply Thevenin's theorem and also limitations of Thevenin's theorem. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. State Norton's theorem and determine the Norton's equivalent circuit across AB terminals in Network shown in Fig.Q3(b). Also draw Thevenin's equivalent across AB.

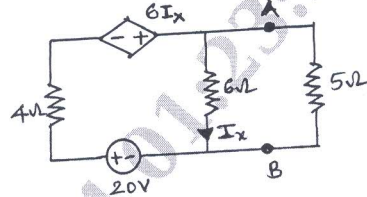


Fig.Q3(b)

(10 Marks)

OR

- 4 a. State and explain maximum power transfer theorem using suitable networks and also prove the maximum power transfer theorem. (10 Marks)  
 b. By using superposition theorem, determine the current through the  $(4 + j3)$  impedance shown in Fig.Q4(b) Network.

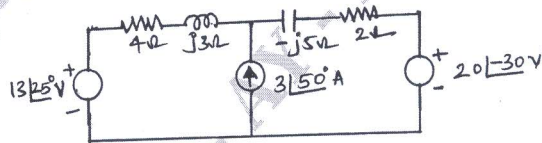


Fig.Q4(b)

(10 Marks)

**Module-3**

- 5 a. Define the following :  
 i) Resonance    ii) Q-factor    iii) Selectivity    iv) Bandwidth (04 Marks)  
 b. Explain the behaviour of R, L, C elements for transients. Mention their representation at the time of switching. (06 Marks)  
 c. The network shown in Fig.Q5(c) below is under steady state condition with switch K is at position 1. Determine expression for  $i(t)$  if switch K is moved to position 2. Draw variation of  $i(t)$ .

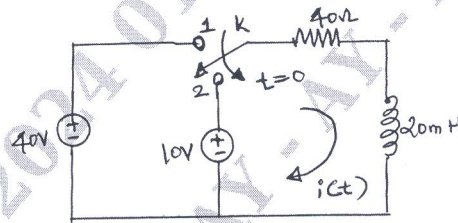


Fig.Q5(c)

(10 Marks)

OR

- 6 a. Show that Resonant frequency is geometric mean of two half power frequencies. (04 Marks)  
 b. It is required that a series RLC circuit should resonate at 1 MHz. Determine values of R, L and C if bandwidth of circuit is 5 kHz and its impedance is  $50 \Omega$  at resonance. (06 Marks)  
 c. In circuit shown in Fig.Q6(c), determine complete solution for current, when switch K is closed at  $t = 0$ . Applied voltage is  $V(t)$  which is given,  $100\cos(10^3t + \pi/2)$ .

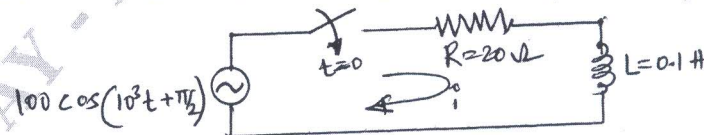


Fig.Q6(c)

(10 Marks)

**Module-4**

- 7 a. Mention advantages and disadvantages of Laplace transform. (04 Marks)  
 b. State and prove Final Value theorem as applied to Laplace transform. (06 Marks)  
 c. Synthesis the waveform shown in Fig.Q7(c). Determine Laplace transform of periodic waveform.

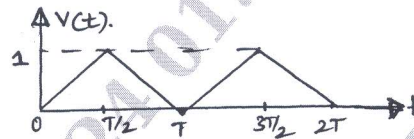


Fig.Q7(c)

(10 Marks)

OR

- 8 a. Obtain Laplace transform of a Ramp function. (04 Marks)  
 b. Determine Laplace transform of a following :  
 i)  $\sin^2 t$     ii)  $\cos^2 t$  (06 Marks)  
 c. Calculate the voltage  $V_c(t)$  for  $t \geq 0$  for the circuit shown below using Laplace transform method. In the circuit shown Fig.Q8(c) switch is opened at  $t = 0$ .

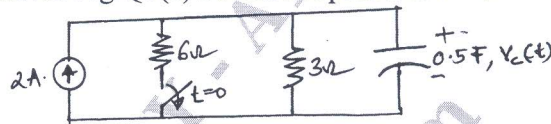


Fig.Q8(c)

(10 Marks)

**Module-5**

- 9 a. Define port of network and write assumptions to be made to find network and also obtain Z-parameters. (10 Marks)  
 b. An unbalanced 3-phase load is supplied by symmetrical 3 phase, 440V, 3 wire system. The star connected load branch are  $Z_R = 5\angle 30^\circ$ ,  $Z_Y = 10\angle 45^\circ$ ,  $Z_B = 10\angle 60^\circ$ . Determine line currents. (10 Marks)

OR

- 10 a. Discuss the method of analyzing 3-phase star connected unbalanced load using mesh method. (10 Marks)  
 b. Determine h-parameter of network shown in Fig.Q10(b) and give its equivalent circuit.

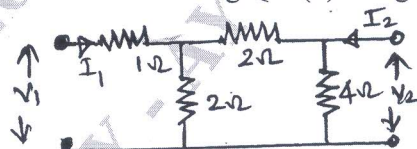


Fig.Q10(b)

(10 Marks)

\*\*\*\*\*