



Second Semester B.E./B.Tech. Degree Examination, June/July 2024
Introduction to Electronics and Communication

Time: 3 hrs.

Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. M : Marks , L: Bloom's level , C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Draw the block diagram of Regulated power supply and mention the function of each block.	8	L2	CO1
	b.	With the use of circuit diagram and waveforms, explain the working of Half wave rectifier with capacitor filter.	8	L2	CO1
	c.	Mention advantages of –ve feedback.	4	L1	CO1
OR					
Q.2	a.	List out and explain the various types of amplifiers.	8	L1	CO1
	b.	With neat diagram, explain the concept of negative feedback amplifier.	7	L2	CO1
	c.	Write a note on Multistage amplifiers.	5	L1	CO1
Module – 2					
Q.3	a.	Explain the working of RC – ladder network oscillator.	6	L2	CO2
	b.	Define Multivibrators. Explain the working of single stage astable multivibrator with diagram.	8	L1	CO2
	c.	Explain its working of Weinbridge Oscillator with diagram.	6	L2	CO2
OR					
Q.4	a.	Define the following terms with respect to the Op_Amp : i) CMRR ii) Slew rate iii) Supply voltage rejection ratio iv) Input offset voltage v) Input offset current.	10	L1	CO2
	b.	Explain how Op_Amp can be used as i) Voltage follower ii) Integrator.	10	L2	CO2
Module – 3					
Q.5	a.	Convert i) $(3568)_{10} = (?)_2$ ii) $(3FD)_{16} = (?)_2$ iii) $(110111)_2 = (?)_{10}$ iv) $(1234)_{10} = (?)_8$ v) $(5678)_{10} = (?)_{16}$.	10	L2	CO3
	b.	Write any four Boolean theorems and Identities.	10	L1	CO3
OR					
Q.6	a.	Simplify the following Boolean functions : i) $Y = A\bar{B} + AB$ ii) $F = B[(A + \bar{B})(B + C)]$ iii) $Z = B(A + C) + C$.	8	L3	CO3

	b.	Explain Half adder circuit with truth table, Realize the circuit for sum and carry using basic gates.	8	L2	CO3
	c.	Write the Symbol and Truth Table of AND and OR – Gate.	4	L1	CO3
Module – 4					
Q.7	a.	Define Embedded system and explain the classification of Embedded system based on Complexity and Deterministic behavior.	10	L2	CO4
	b.	Compare Embedded system and General computing system.	6	L1	CO4
	c.	List out the major applications areas of Embedded system.	4	L1	CO4
OR					
Q.8	a.	With the use of diagram, explain the core of an Embedded system.	8	L2	CO4
	b.	Compare RISC and CISC.	6	L1	CO4
	c.	Write a short notes on Sensors and 7 – segment LED displays.	6	L2	CO4
Module – 5					
Q.9	a.	With the help of block diagram, explain the basic Communication system.	10	L2	CO5
	b.	Define Noise and explain the various kinds of noises.	10	L2	CO5
OR					
Q.10	a.	Define Multiplexing and explain types of Communication systems.	8	L2	CO5
	b.	Classify and explain the Multiple Access Techniques.	8	L2	CO5
	c.	Mention the Need for Modulation.	4	L1	CO5
