

## Third Semester B.E. Degree Examination, June/July 2025 Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Use Mesh analysis to find  $I_1$ ,  $I_2$ ,  $I_3$  in the circuit of Fig.Q1(a).

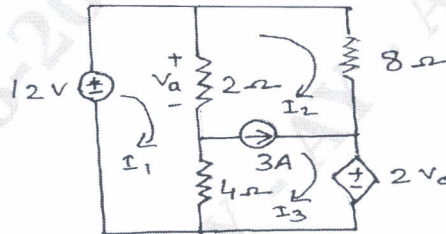


Fig.Q1(a)

(10 Marks)

- b. Find  $R_{eq}$  and  $i$ , for the circuit shown in Fig.Q1(b).

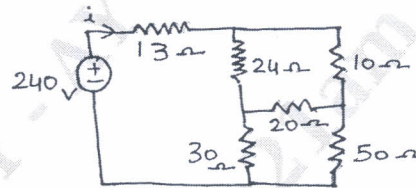


Fig.Q1(b)

(06 Marks)

- c. Construct the dual of the circuit in Fig.Q1(c).

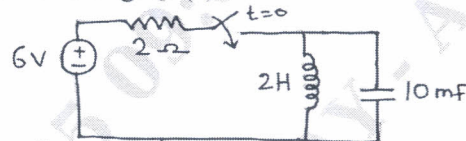


Fig.Q1(c)

(04 Marks)

OR

- 2 a. Determine the power supplied by the dependent source in Fig.Q2(a), using Node analysis.

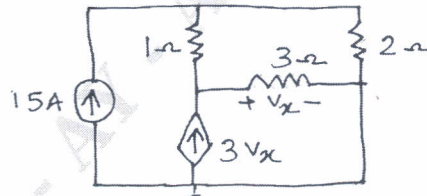


Fig.Q2(a)

(10 Marks)

- b. Reduce the network in Fig.Q2(b) to a single voltage source using source shifting and transformation.

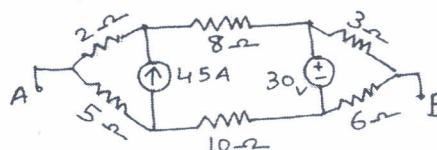


Fig.Q2(b)

(10 Marks)

**Module-2**

- 3 a. Using superposition theorem, find  $V_x$  in the circuit of Fig.Q3(a).

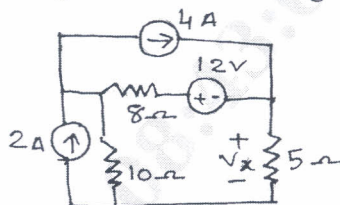


Fig.Q3(a)

(10 Marks)

- b. Find the current  $I$  in the circuit Fig.Q3(b) and verify reciprocity theorem.

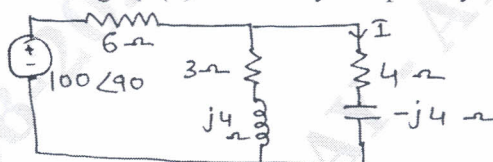


Fig.Q3(b)

(10 Marks)

**OR**

- 4 a. Obtain the Thevenin's equivalent across AB for the network shown in Fig.Q4(a).

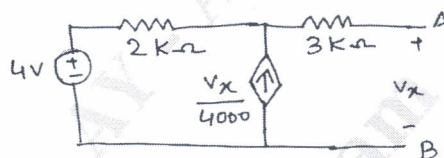


Fig.Q4(a)

(08 Marks)

- b. Obtain the Norton equivalent across AB for the network shown in Fig.Q4(b).

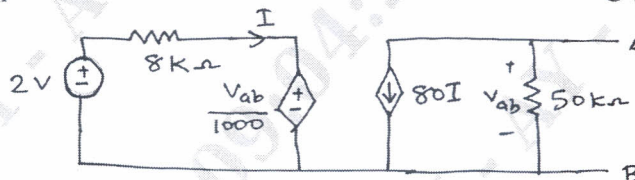


Fig.Q4(b)

(06 Marks)

- c. In the circuit shown in Fig.Q4(c), find the load connected at AB for which the power transferred will be maximum. Also find the maximum power.

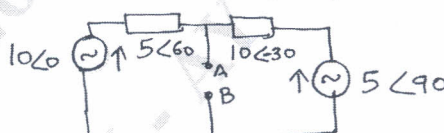


Fig.Q4(c)

(06 Marks)

**Module-3**

- 5 a. Determine the RLC parallel circuit parameters whose response curve is as shown in Fig.Q5(a). What are the new values of  $\omega_r$  and bandwidth if  $C$  is increased by four times.

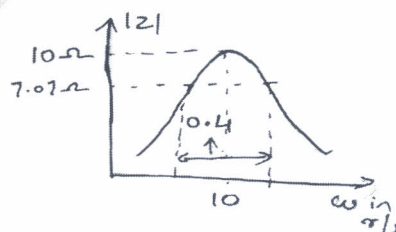


Fig.Q5(a)

(08 Marks)

- b. In the circuit shown in Fig.Q5(b), the switch K is opened at  $t = 0$ . Find at  $t = 0^+$  the voltage across the switch, its first and second derivatives.

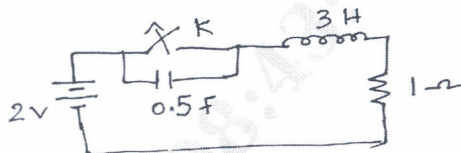


Fig.Q5(b)

(12 Marks)

OR

- 6 a. In the circuit shown in Fig.Q6(a), the switch K is closed at  $t = 0$ . Solve for the currents in L and C and their derivatives at  $t = 0^+$ .

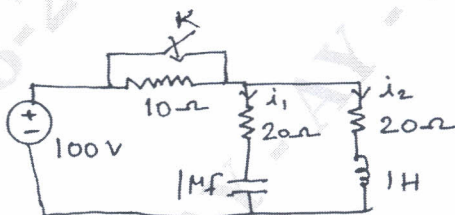


Fig.Q6(a)

(12 Marks)

- b. Find the value of L for which the given circuit in Fig.Q6(b) resonates at 1000 Hz.

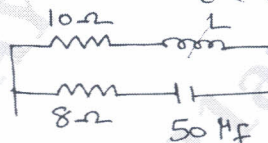


Fig.Q6(b)

(08 Marks)

**Module-4**

- 7 a. Find the final value and the initial value for the given functions:

i)  $f(t) = 5 + 4e^{-2t}$

ii)  $f(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)}$

(06 Marks)

- b. Find the Laplace transform of the given waveform in Fig.Q7(b).

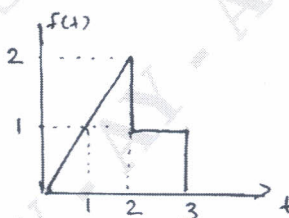


Fig.Q7(b)

(06 Marks)

- c. Obtain the Laplace transform for the given waveform in Fig.Q7(c).

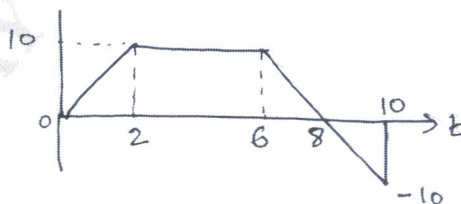


Fig.Q7(c)

(08 Marks)



OR

- 8 a. State and prove initial value and final value theorem.  
b. Obtain the Laplace transform of the periodic function in Fig.Q8(b).

(10 Marks)

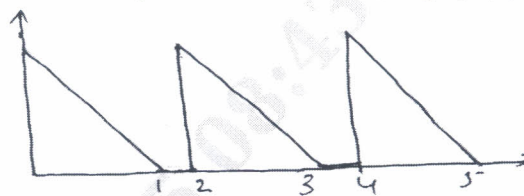


Fig.Q8(b)

(10 Marks)

**Module-5**

- 9 a. For the unbalanced delta connected load in Fig.Q9(a), find the phase currents, line currents and total power consumed by load when the phase sequence ACB.

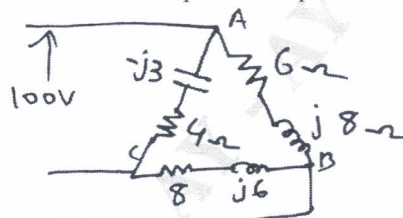


Fig.Q9(a)

(10 Marks)

- b. Obtain the Y parameter for the network shown in Fig.Q9(b).

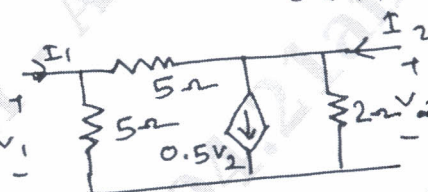


Fig.Q9(b)

(10 Marks)

OR

- 10 a. Find the Z – parameters for the network shown in Fig.Q10(a).

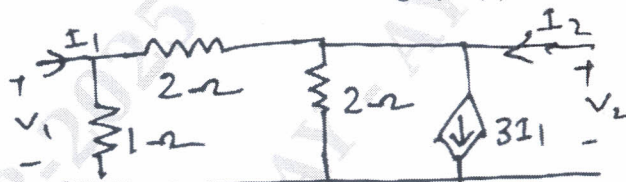


Fig.Q10(a)

(10 Marks)

- b. Obtain the T parameter, for the network shown in Fig.Q10(b), give the result in S domain.

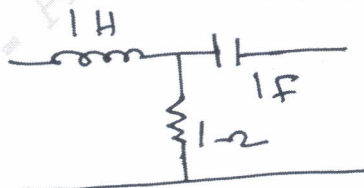


Fig.Q10(b)

(10 Marks)

\*\*\*\*\*