

CBCS SCHEME - Make-Up Exam





BEE302

Third Semester B.E/B.Tech. Degree Examination, June/July 2025

Electric Circuit Analysis

Max. Marks:100

- Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M : Marks , L: Bloom's level , C: Course outcomes.

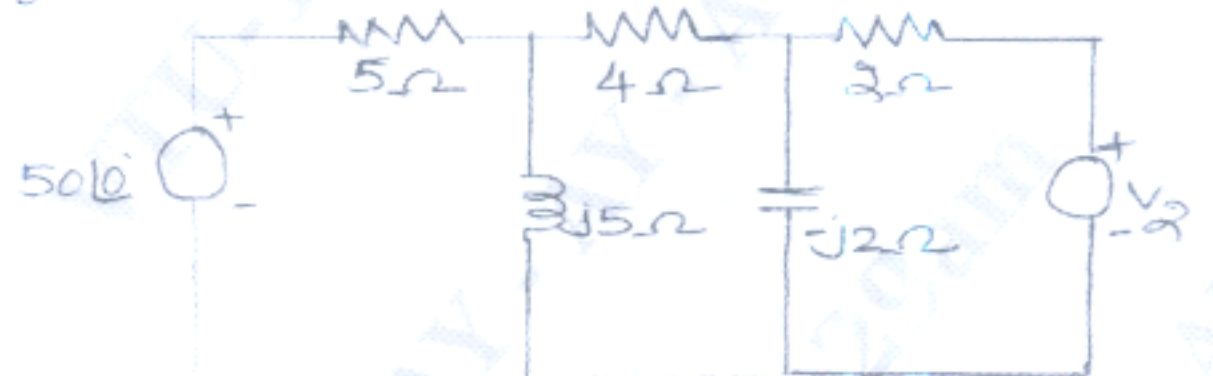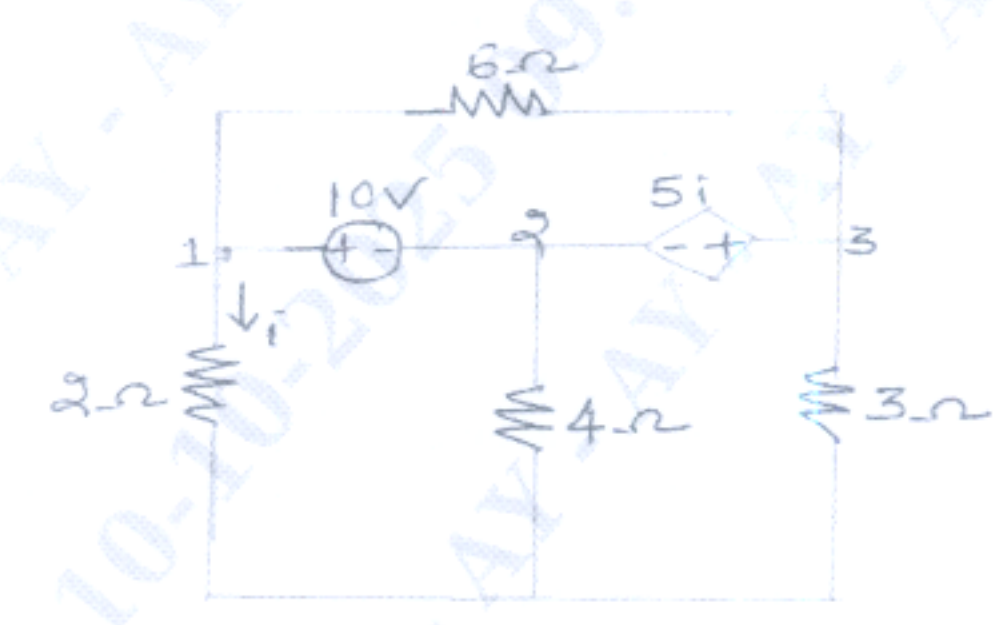Module – 1		M	L	C
1	a. Explain source shifting and source transformation of voltage and current sources with an example for each.	8	L1	CO1
	b. Using the mesh current method, determine V_2 that results in zero current through 4Ω resistor.	6	L3	CO1
	 Fig. Q. 1(b)			
	c. Find the voltages at nodes 1, 2, 3 for the n/w shown in fig1. (c) using nodal Analysis.	6	L3	CO1
	 Fig. Q 1 (c)			

OR

- 2 a. Distinguish between :
i) Active and Passive elements
ii) Ideal and Practical sources.

6

L1

CO1

- b. Find the currents i_1 , i_2 and i_3 in the network given in Fig. Q. 2 (b) using mesh analysis.

6

L3

CO1

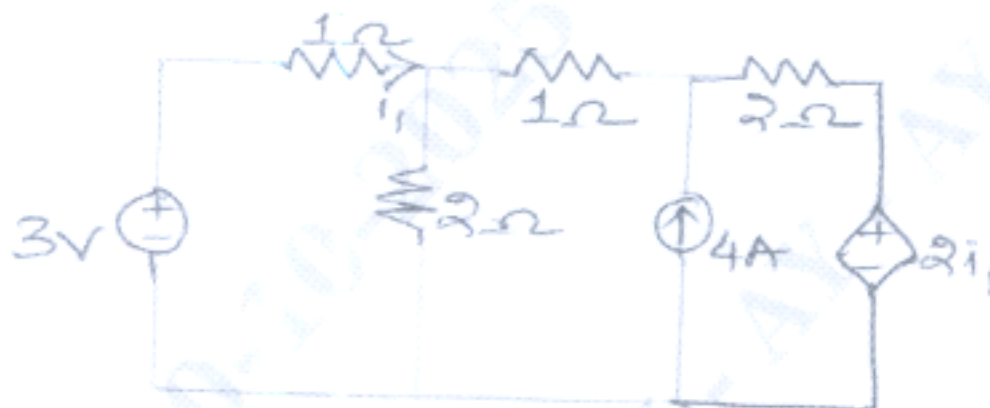


Fig. Q 2 (b)

- c. Explain the concept of supermesh analysis with a suitable circuit diagram.

8

L3

CO1

Module – 2

- 3 a. State and explain Superposition Theorem.

6

L1

CO2

- b. Using the Superposition Theorem, obtain the response I for the network shown in Fig. 3 (b).

8

L3

CO2

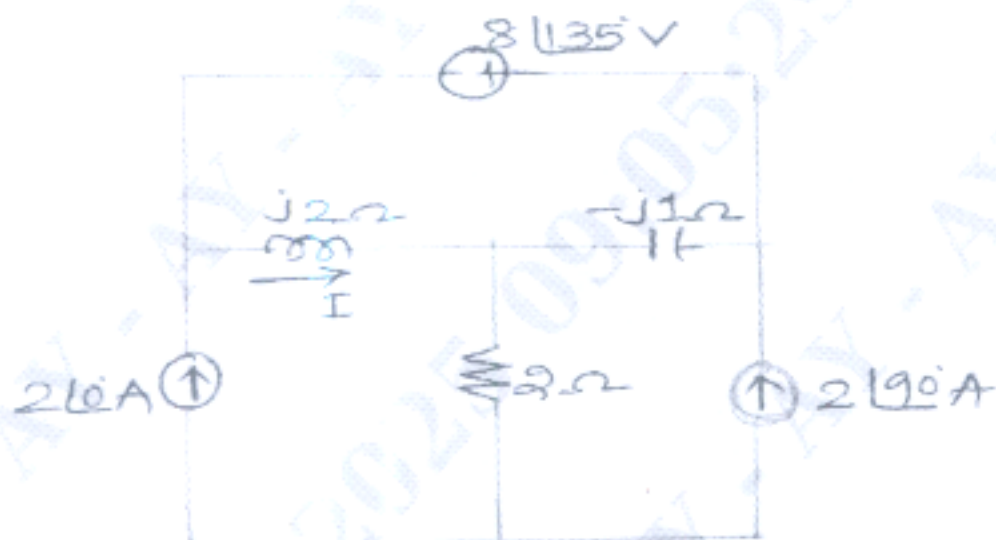


Fig. Q 3 (b)

- c. Find the Thevenin's Voltage short circuit current and determine the actual current flowing through the 6Ω resistor in the network given in Fig. Q. 3 (c).

6

L3

CO2

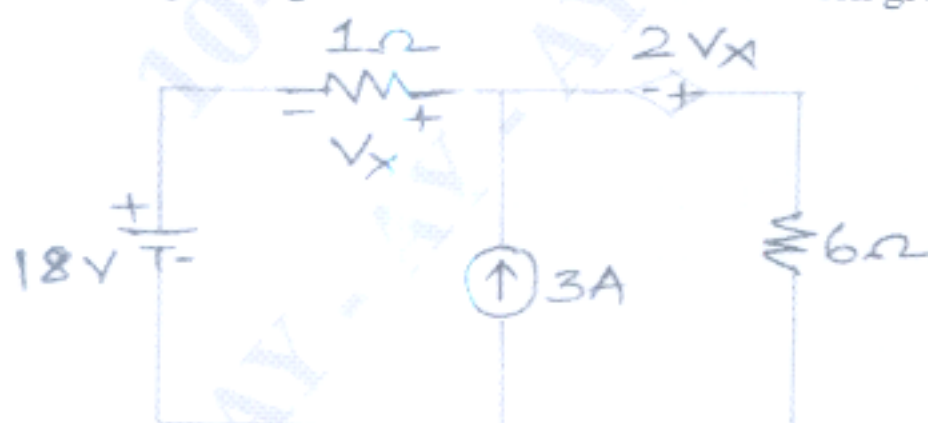
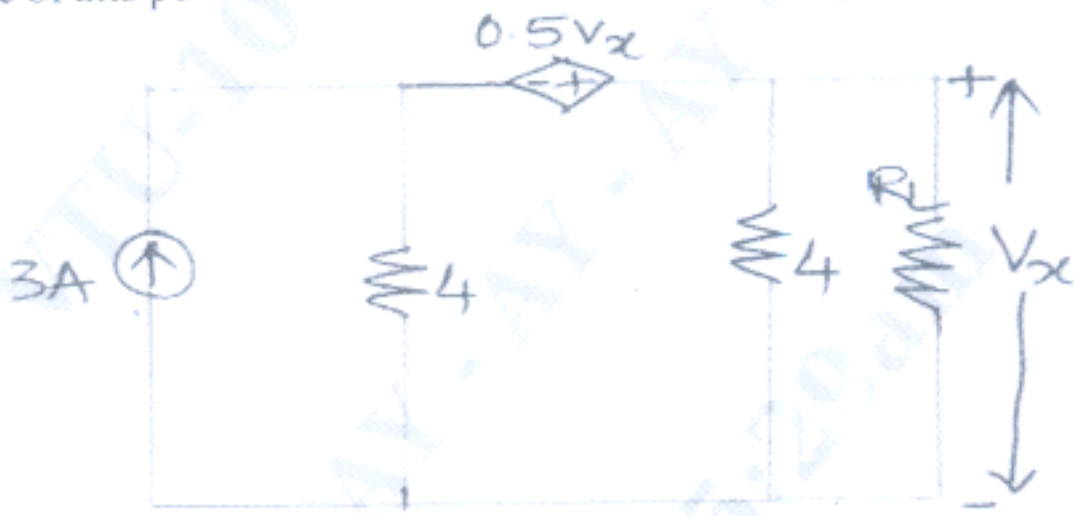
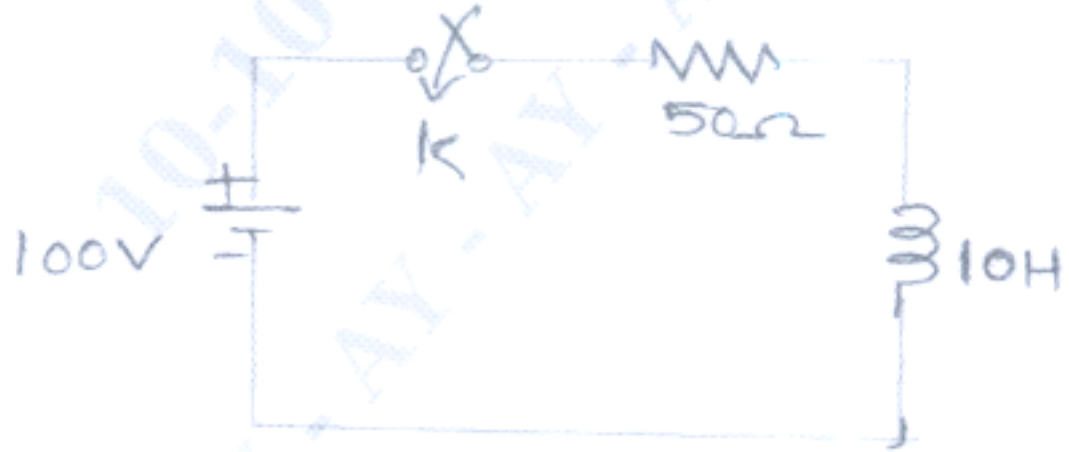


Fig. Q. 3 (c)

OR

4	a.	State and prove Thevenin's Theorem.	6	L1	CO2
	b.	Find the Thevenin's equivalent of the network shown in Fig. Q. 4 (b).	8	L3	CO2
 Fig. Q. 4 (b)					
	c.	What will be the value of R_L to get maximum power delivered to it? What is the value of this power? Refer the network shown in Fig. Q. 4 (c).	6	L3	CO2
 Fig. Q. 4 (c)					

Module - 3

5	a.	Derive expressions for resonant frequency in series RLC circuit.	6	L3	CO2
	b.	A series RLC circuit has $R = 4\Omega$, $L = 1 \text{ mH}$, $C = 10 \mu\text{F}$. Calculate Q Factor, bandwidth, resonant frequency and half power frequencies.	8	L3	CO2
	c.	Find the equation of current if the switch is closed at $t = 0$. Find also the voltage across L and R, the current at $t = 0.1 \text{ sec}$. and the time at which the voltage across L and R are equal in Fig. Q 5 (c).	6	L3	CO2
 Fig. Q. 5 (c)					

OR

- 6 a. Find I_0 , I_c , I_L , Q factor, resonant frequency and parallel resonance for the parallel resonant circuit shown in Fig. Q 6 (a).

8

L3

CO3

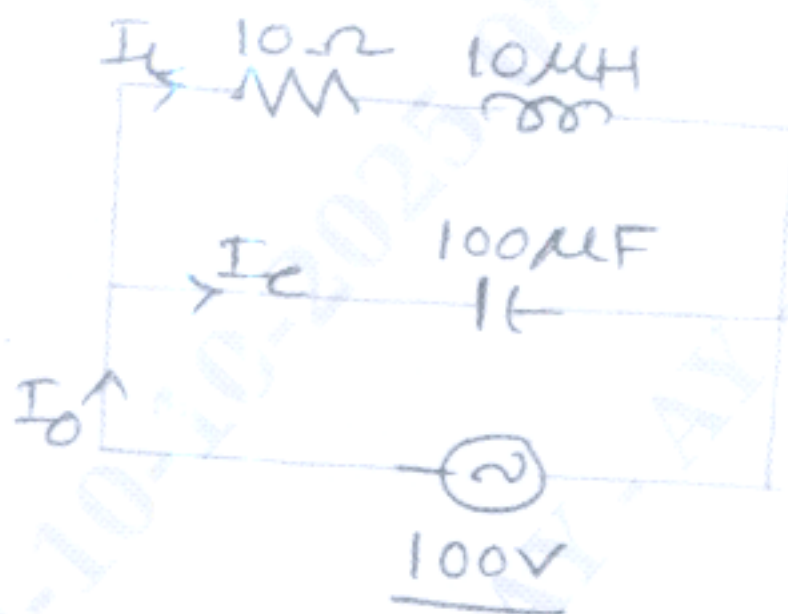


Fig. Q. 6 (a)

- b. In the Fig. Q. 6 (b), the switch S is closed at $t = 0$, find the time when the current from the battery reaches to 500 mA.

8

L3

CO3

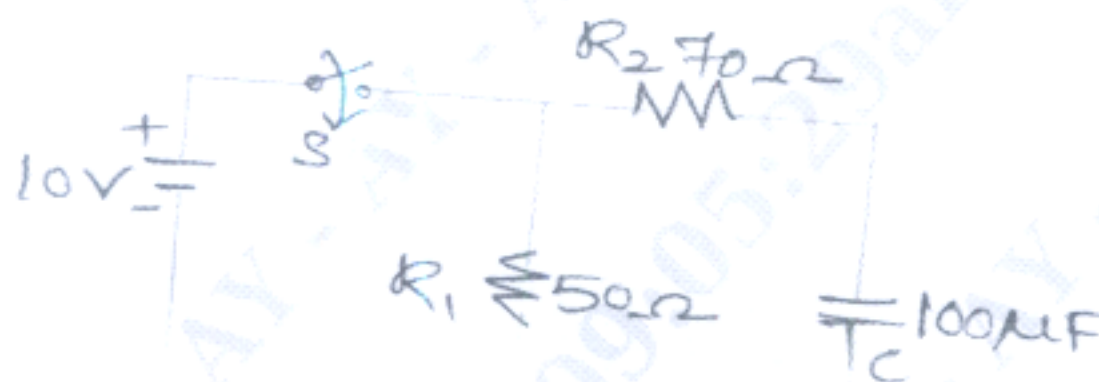


Fig. Q. 6 (b)

- c. What are the Initial conditions and their use in network analysis.

4

L1

CO2

Module - 4

- 7 a. State and explain the initial value theorem and final value theorem.
- b. Obtain the Laplace transform of a periodic function with a suitable example. Also find the Laplace transform of the following waveform shown in Fig. Q. 7 (b).

10

L3

CO4

10

L3

CO4

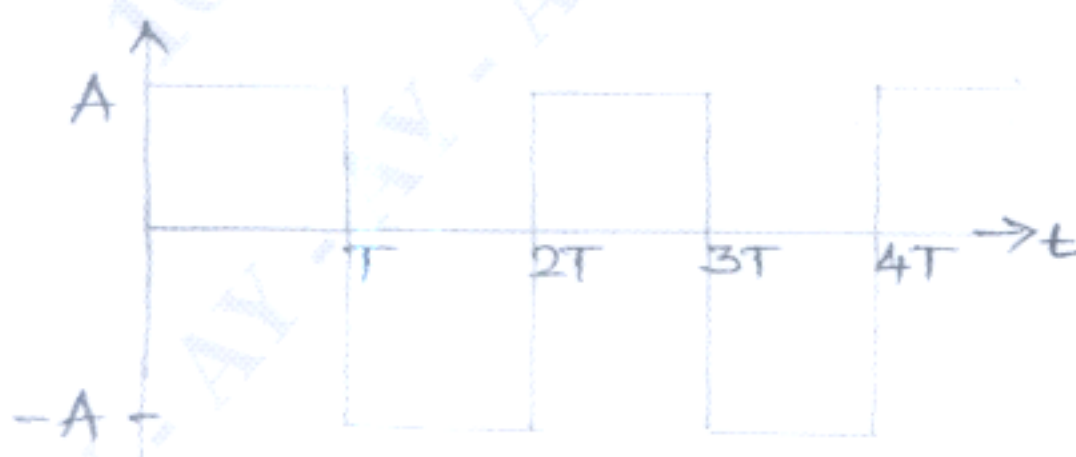


Fig. Q. 7 (b)

OR

8	a.	Find the Laplace transform of the following. i) $\sin^2 t$ ii) $\cos^2 t$ iii) $\sin \omega t$ iv) $\int_0^t i(t) dt$	10	L4	CO4
	b.	Find the inverse Laplace transform. i) $\frac{s^2 + 5}{s(s^2 + 2s + 4)}$ ii) $\frac{2s + 6}{s^2 + 6s + 25}$	10	L4	CO4

Module – 5

9	a.	Derive Y – parameters and transmission parameters in terms of z – parameters.	10	L4	CO5
	b.	Find the transmission parameters for the given R – C network shown in Fig. Q. 9 (b).	10	L3	CO5

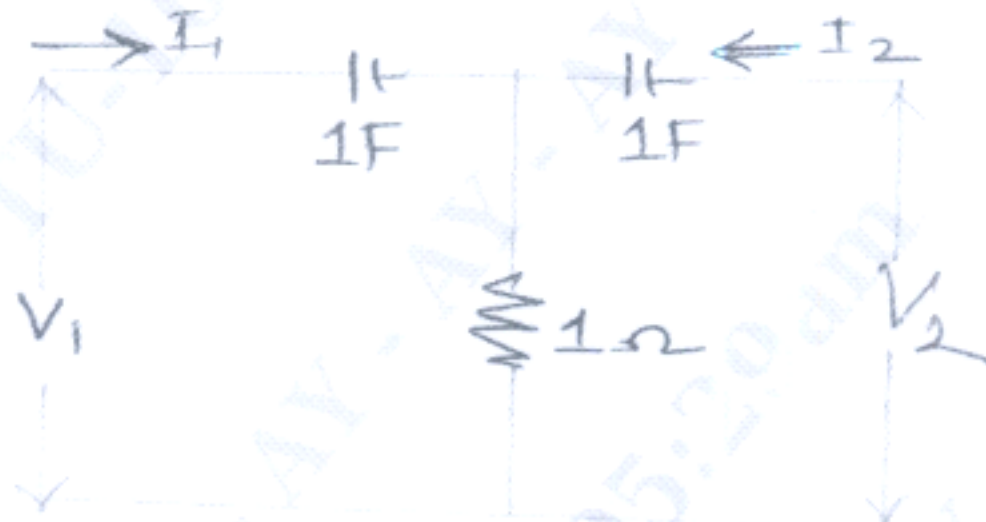


Fig. Q. 9 (b)

OR

10	a.	Express z parameters in terms of h – parameters.	10	L3	CO5
	b.	For the network shown, find Z and Y parameters.	10	L3	CO5

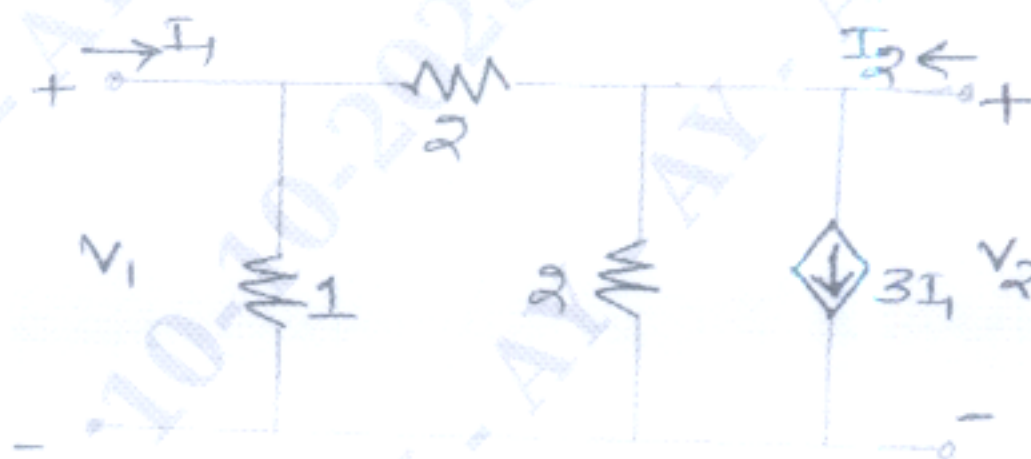


Fig. Q. 10(b)
