





Third Semester B.E./B.Tech. Degree Examination, June/July 2025

Analog Electronic Circuits

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks, L: Bloom's level, C: Course outcomes.

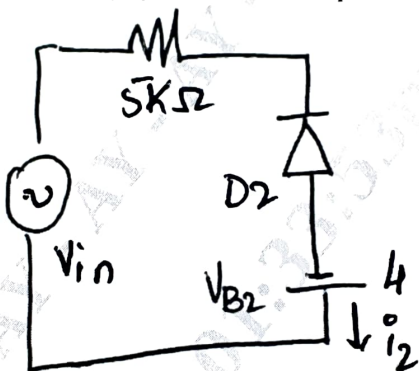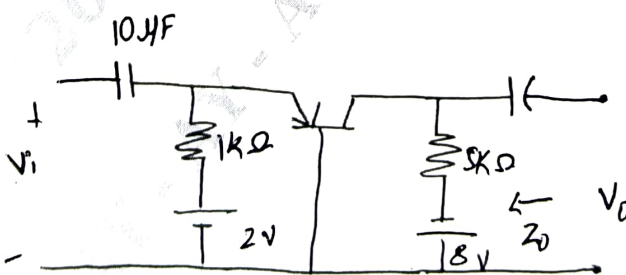Module – 1			M	L	C
Q.1	a.	How can a diode circuit be implemented to represent parallel independent clipper, illustrate with circuit equations and waveforms.	10	L2	CO1
	b.	The emitter bias circuit has the following specifications : $I_{CQ} = \frac{1}{2} I_{sat}$, $I_{sat} = 8 \text{ mA}$, $V_C = 18 \text{ V}$, $V_{CC} = 18 \text{ V}$, $\beta = 110$. Determine R_C , R_E and R_B .	10	L3	CO1
OR					
Q.2	a.	Find the output voltage V out of the clipper circuit shown assuming. i) Diode are ideal ii) $V_{on} = 0.7 \text{ V}$. For both cases, $R_f = 0$. Sketch the output waveforms.	10	L3	CO1
 <p>Fig.Q2(a)</p>					
	b.	Explain the voltage divider bias circuit and derive I_c and V_{CE} and terminal voltages.	10	L2	CO2
Module – 2					
Q.3	a.	With the help of small signal low frequency transistor model, draw generalized model of the amplifier.	10	L2	CO3
	b.	For the networks shown in below, find – I_E , r_e , Z_i , Z_o , A_v , A_i .	10	L3	CO3
 <p>Fig.Q3(b)</p>					
OR					
Q.4	a.	Explain miller effect capacitance. Derive C_{mi} .	10	L2	CO3
	b.	Enumerate on general frequency consideration for a Transistors.	10	L2	CO3

1 of 2

Module – 3

Q.5	a.	Derive Z_{in} and Z_o of darlington amplifier also derive A_i and A_v .	10	L4	CO3
	b.	Explain cascade amplifier and explain the overall gain equation.	10	L2	CO3

OR

Q.6	a.	For a transformer coupled amplifier with $V_{CC} = 12V$, $C_{in} \rightarrow \infty$, $\beta = 100$, $V_{BE} = 0.7V$, $A_i = 0$. Find power supplied to load and power required from supply.	10	L3	CO3
	b.	Write important characteristics of: i) Darlington emitter follower ii) Feedback amplifier.	10	L2	CO3

Module – 4

Q.7	a.	Explain push-pull circuit with a circuit and derive A_v .	10	L2	CO3
	b.	Draw DC equivalent circuit for class C amplifier and explain.	10	L2	CO3

OR

Q.8	a.	With a neat circuit diagram explain RC phase shift oscillator and derive equation for frequency.	10	L2	CO3
	b.	The tuned collector oscillator circuit used in the local oscillator of radio makes use of LC tuned circuit with $L_1 = 58.6\mu H$, $C_1 = 300$ pf calculate oscillation frequencies.	5	L3	CO3
	c.	What are the advantages and disadvantages of using crystal oscillator?	5	L2	CO3

Module – 5

Q.9	a.	Explain the operation of JFET.	10	L2	CO3
	b.	Derive g_m for n-channel JFET and draw its characteristic curve.	6	L4	CO3
	c.	What are the advantages of FET over BJT?	4	L2	CO3

OR

Q.10	a.	With a neat circuit diagram for FET – voltage divider bias – derive I_D and $V_{GS(min)}$, $V_{GS(max)}$.	10	L3	CO3
	b.	Derive i_d , μ , g_m for FET amplifier.	10	L3	CO3
