

Third Semester B.E./B.Tech. Degree Examination, June/July 2025

Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define diode clippers. With circuit diagram and waveforms explain negative shunt clipper. (06 Marks)
- b. What is transistor biasing? Analyse fixed bias circuit. (07 Marks)
- c. For the Emitter-bias network of Fig.Q1(c), determine :
 i) I_B ii) I_C iii) V_{CE} iv) V_C v) V_E vi) V_B vii) V_{BC} .

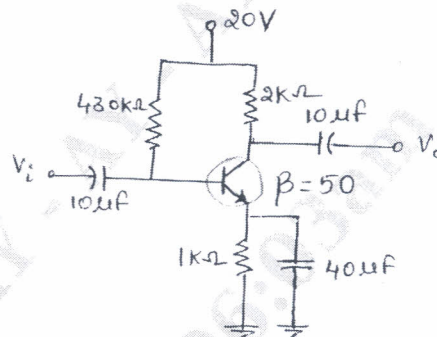


Fig.Q1(c)

(07 Marks)

OR

- 2 a. Explain transistor switching action and switching characteristics. (07 Marks)
- b. State the significance of stability factor and define each. (05 Marks)
- c. Determine the output voltage for the clamper circuit shown in Fig.Q2(c).

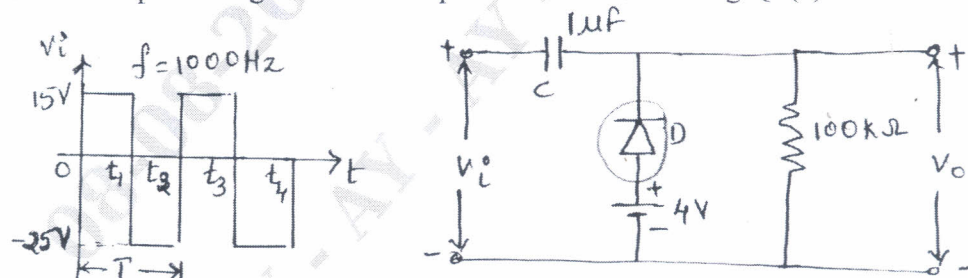


Fig.Q2(c)

(08 Marks)

Module-2

- 3 a. For the transistor connected in CE configuration, with voltage divider biasing, determine voltage gain, current gain, input and output resistances using h-parameter model. (09 Marks)
- b. Explain Miller's theorem. (05 Marks)
- c. Draw the h-parameter models for all transistor configurations. (06 Marks)

OR

- 4 a. Derive the expression for A_i , A_v and Z_i for an emitter follower circuit using hybrid model. (10 Marks)
- b. For the network of Fig.Q4(b), determine :
i) Z_i ii) Z_o iii) A_v iv) A_i .

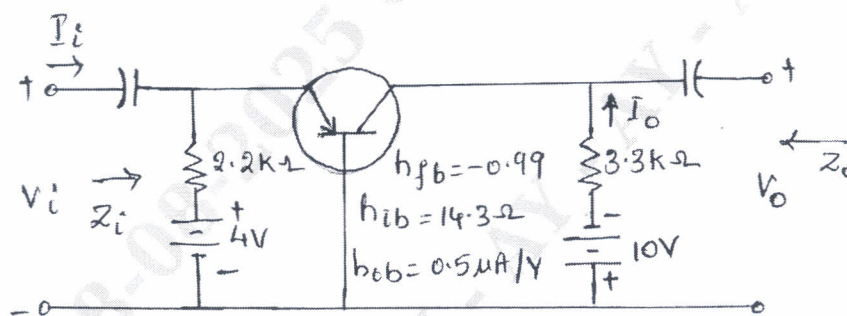


Fig.Q4(b)

(10 Marks)

Module-3

- 5 a. State the need for cascading amplifiers. With the block diagram explain two-stage cascaded amplifier. (10 Marks)
- b. Derive the expression for output resistance for a voltage series feedback amplifier. (06 Marks)
- c. State the advantages of negative feedback. (04 Marks)

OR

- 6 a. For the Darlington emitter follower circuit, obtain expression for voltage gain, current gain and input impedance. (10 Marks)
- b. Calculate the voltage gain of the circuit Fig.Q6(b).

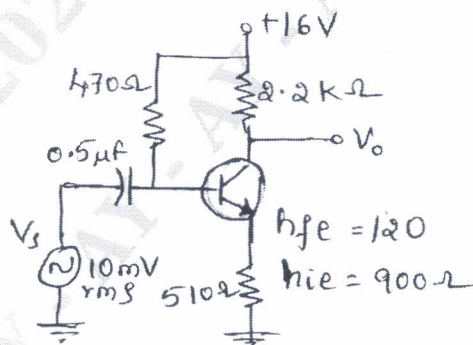


Fig.Q6(b)

(10 Marks)

Module-4

- 7 a. Explain the operation of transformer coupled class A power amplifier. Also show that the amplifier has a maximum efficiency of 50%. (10 Marks)
- b. With the help of neat circuit diagram explain the operation of transistor RC phase shift oscillator. Write the expression for frequency of oscillation. (10 Marks)

OR

- 8 a. With a neat circuit diagram explain the operation of Wein Bridge oscillator. Also derive for frequency of oscillation. (10 Marks)
- b. How crystal oscillators provide good frequency stability. (03 Marks)
- c. For a class B amplifier using a supply of $V_{CC} = 30V$ and driving a load of 16Ω , determine the maximum input power, output power and transistor dissipation. (07 Marks)

Module-5

- 9 a. Draw the experimental setup and explain drain characteristics of n-channel JFET with schematic graph. (10 Marks)
- b. Explain the depletion and enhancement type MOSFETs characteristics. (10 Marks)

OR

- 10 a. Define transconductance g_m and drain resistance r_d of field effect transistor. Explain the procedure to determine them graphically. (10 Marks)
- b. The fixed bias configuration shown in Fig.Q10(b) with an applied signal V_i had an operating point defined by $V_{GSQ} = -2V$ and $I_{DQ} = 5.625$ mA with $I_{DSS} = 10$ mA and $V_P = -8$ V. The value of Y_{OS} is provided as $40 \mu S$.
- Determine g_m
 - Find r_d
 - Determine Z_i
 - Calculate Z_o
 - Determine the voltage gain A_v
 - Determine A_v ignoring the effects of r_d .

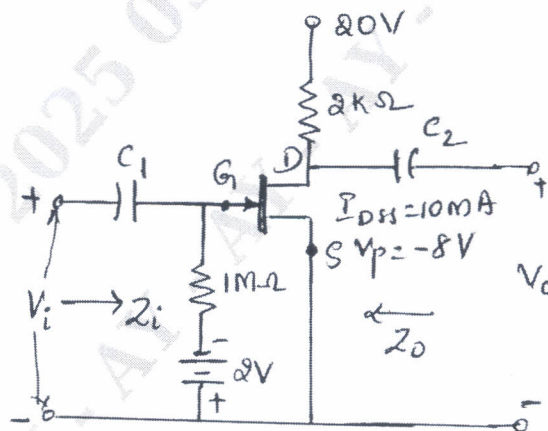


Fig.Q10(b)

(10 Marks)
