



## Fourth Semester B.E. Degree Examination, June/July 2025

### Operational Amplifiers and Linear IC's

Date .....

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

#### Module-1

1 a. With a neat block diagram, explain the internal structure and characteristics of a typical operational amplifiers. (10 Marks)  
b. Explain the working of inverting and non-inverting amplifiers using ideal Op-Amp. (10 Marks)

**OR**

2 a. Describe the open loop configuration of an Op-Amp with relevant examples. (10 Marks)  
b. Explain the working of an instrumentation amplifier and its advantages. (10 Marks)

#### Module-2

3 a. Explain and design the frequency response of a second order Butterworth low pass filter. (10 Marks)  
b. Explain the working of an all pass filter and mention its applications. (10 Marks)

**OR**

4 a. With a neat diagram, explain the working of LM317 adjustable voltage regulator. (10 Marks)  
b. Compare LM317 and LM337 regulators and describe voltage follower regulator. (10 Marks)

#### Module-3

5 a. Draw the circuit of a triangular wave generator and explain its operation. (10 Marks)  
b. Explain the working of a phase shift oscillator using Op-Amp. (10 Marks)

**OR**

6 a. Describe the working of an inverting and non-inverting Schmitt trigger using Op-Amp. (10 Marks)  
b. With a circuit diagram, explain the operation of voltage to frequency converter. (10 Marks)

#### Module-4

7 a. Draw and explain the working of a precision full wave rectifier. (10 Marks)  
b. Explain the working of a voltage-current converter with a grounded load. (10 Marks)

**OR**

8 a. Explain the operation of an R – 2R ladder D/A converter with a neat diagram. (10 Marks)  
b. Discuss the principle and working of a successive approximation ADC. (10 Marks)

#### Module-5

9 a. Explain the basic building blocks and working principle of phase locked loop. (10 Marks)  
b. Define and explain capture range, lock range, and loop gain in PLL systems. (10 Marks)

**OR**

10 a. Draw and explain the internal architecture of 555 timer IC. (10 Marks)  
b. Describe the working of a Monostable Multivibrator using a 555 timer and mention two applications. (10 Marks)

\* \* \* \* \*