

USN

Fifth Semester B.E./B.Tech. Degree Examination, June/July 2025
Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain five different types of power electronic converter circuits with neat circuit diagram, input and output waveforms. (10 Marks)
- b. With neat figure, explain the V-I characteristics of diode. (05 Marks)
- c. Explain peripheral effects of power electronics equipments with block diagram. (05 Marks)

OR

- 2 a. With neat circuit diagram and waveforms explain single phase full wave rectifier with R load. And also derive the expression for average output voltage. (10 Marks)
- b. Explain reverse recovery characteristics of a diode with waveforms. (06 Marks)
- c. Explain the significance of free-wheeling diode. (04 Marks)

Module-2

- 3 a. Explain steady state and switching characteristics of BJT. (10 Marks)
- b. Explain the switching limits of BJT. (04 Marks)
- c. The bipolar transistor in Fig.Q.3(c) is specified to have β_F in the range of 8 to 40. The load resistance is $R_C = 11\Omega$. The dc supply voltage is $V_{CC} = 200$ V and the input voltage to the base circuit is $V_B = 10$ V. If $V_{CE(sat)} = 1.0$ V and $V_{BE(sat)} = 1.5$ V. Find : i) The value of R_B that results in saturation with an ODF of 5 ; ii) The B_{forced} ; iii) The power loss P_T in the transistor.

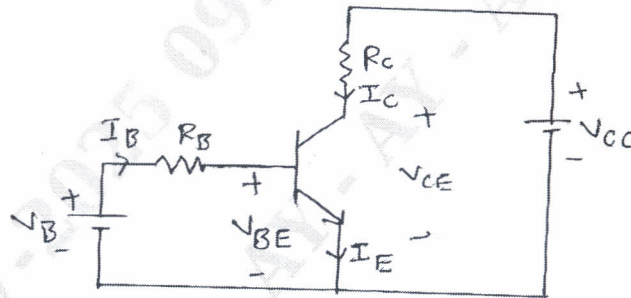


Fig.Q.3(c)

(06 Marks)

OR

- 4 a. With the help of neat figures, explain steady state and switching characteristics of MOSFET. (10 Marks)
- b. With neat circuit diagram, explain pulse transformer and opto coupler. (06 Marks)
- c. The maximum junction temperature of a transistor is $T_J = 150^\circ\text{C}$ and the ambient temperature is $T_A = 25^\circ\text{C}$. If the thermal impedances are $R_{JC} = 0.4^\circ\text{C/W}$, $R_{CS} = 0.1^\circ\text{C/W}$ and $R_{SA} = 0.5^\circ\text{C/W}$, calculate
 - i) The maximum power dissipation
 - ii) The case temperature.

(04 Marks)

Module-3

- 5 a. Explain V – I characteristics of SCR. And also define i) Latching current ii) Holding current. (12 Marks)
- b. Ten thyristors are used in a string to withstand a dc voltage of $V_S = 15 \text{ kV}$. The maximum leakage current and recovery charge differences of thyristors are 10 mA and 150 μC , respectively. Each thyristor has voltage sharing difference of $R = 56 \text{ K}\Omega$ and capacitance of $C_1 = 0.5 \text{ }\mu\text{F}$. Determine : i) The maximum steady state voltage sharing ii) The steady-state voltage derating factor iii) The maximum transient voltage sharing $V_{DT(\text{max})}$ iv) The transient voltage derating factor. (08 Marks)

OR

- 6 a. Explain with neat figure two-transistor model of thyristor and also write relevant equations. (08 Marks)
- b. Explain briefly different thyristor turn-on methods. (06 Marks)
- c. Explain $\frac{di}{dt}$ protection and $\frac{dv}{dt}$ protection. (06 Marks)

Module-4

- 7 a. With circuit diagram and waveforms explain single phase half wave controlled rectifier with R-L load. (08 Marks)
- b. A single phase full converter bridge is connected to RLE load. The source voltage is 230 V, 50Hz. The average load current of 10 A is continuous over the working range. For $R = 0.4\Omega$ and $L = 2 \text{ mH}$, compute i) Firing angle for $E = 120 \text{ V}$ ii) Firing angle for $E = -120 \text{ V}$. (06 Marks)
- c. With neat circuit diagram and waveforms explain J- ϕ dual converter. (06 Marks)

OR

- 8 a. With circuit diagram and waveforms explain phase control in ac voltage controller and also derive expression for RMS output voltage. (08 Marks)
- b. An ac voltage controller has a resistive load of $R = 10\Omega$ and rms input voltage is $V_s = 120 \text{ V}$, 60 Hz. The thyristor switch is on for $n = 25$ cycles and is off for $m = 75$ cycles. Find : i) rms output voltage V_o ii) The input power factor iii) The average and rms current of thyristors. (06 Marks)
- c. With circuit diagram and waveform explain single phase bidirectional controllers with resistive loads. (06 Marks)

Module-5

- 9 a. Explain the principle operation of step down converter with RL load and also draw the waveforms. (10 Marks)
- b. For the stepdown chopper consisting of a resistive load of $R = 10\Omega$ and the input voltage is $V_s = 220 \text{ V}$. When the converter switch remains on, its voltage drop is $V_{ch} = 2 \text{ V}$ and chopping frequency is $f = 1 \text{ kHz}$. If the duty cycle is 50%, determine: i) average output voltage V_a ii) rms output voltage V_o iii) The converter efficiency iv) effective input resistance R_i of the converter v) rms value of the fundamental component of output harmonic voltage. (10 Marks)

OR

- 10 a. Explain :
i) Single pulse – width modulation
ii) Multiple – pulse – width modulation techniques used for voltage control of single phase inverters. (10 Marks)
- b. Describe 180 – degree conduction operation of three phase bridge inverter with circuit diagram and waveforms of line voltages and phase voltages. (10 Marks)

* * * * *