

USN

--	--	--	--	--	--	--	--	--	--

BEC304

Third Semester B.E./B.Tech. Degree Examination, June/July 2025

Network Analysis

Max. Marks: 100



Time: 3 hrs.

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

Module - 1

Use source transformation to convert the circuit in Fig.Q1(a) to a single current source in parallel with a single resistor.

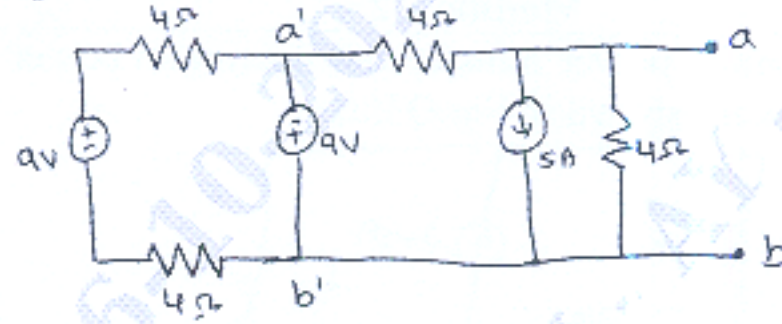


Fig.Q1(a)

b. Find the currents in various branches in the circuit shown in Fig.Q1(b) using mesh current analysis.

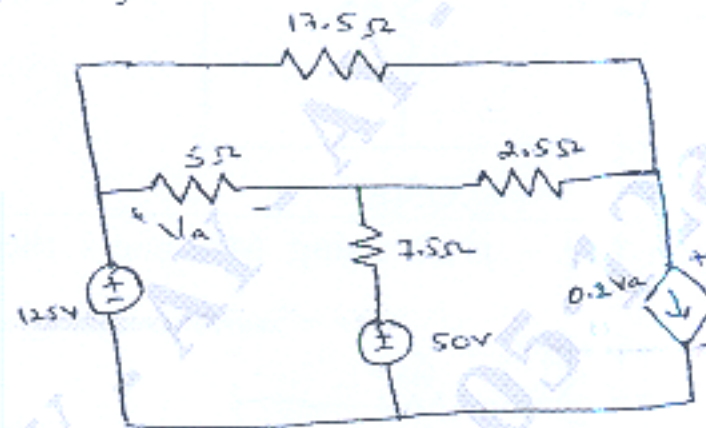


Fig.Q1(b)

c. Use nodal analysis to find V_0 in the circuit Fig.Q1(c).

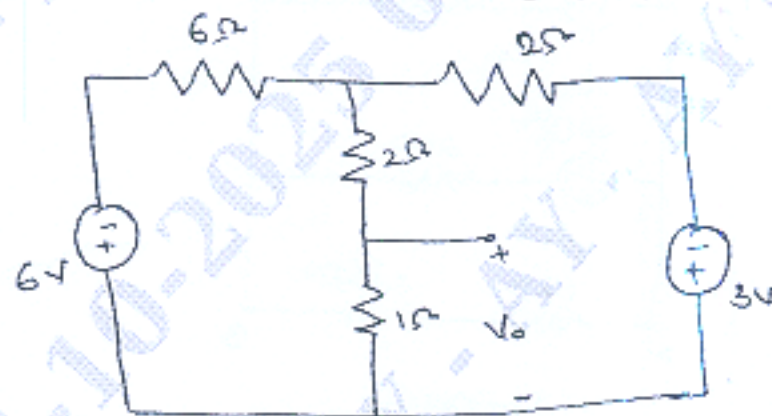


Fig.Q1(c)

OR

Q.2 a. Refer the circuit shown in Fig.Q2(a). Find the power dissipated in the 70 Ω register.

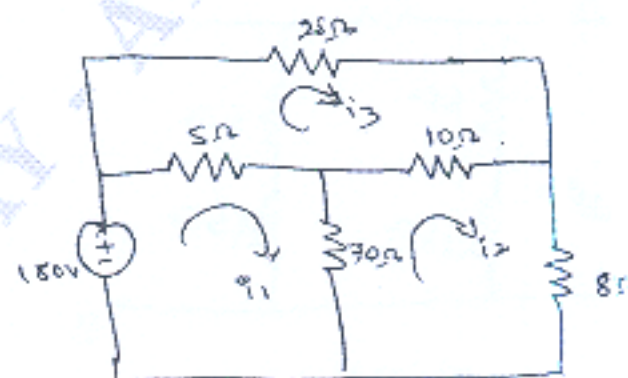


Fig.Q2(a)

- b. Find the value of resistance between the terminals a – b of the network shown in Fig.Q2(b).

10

L2
L3

CO1

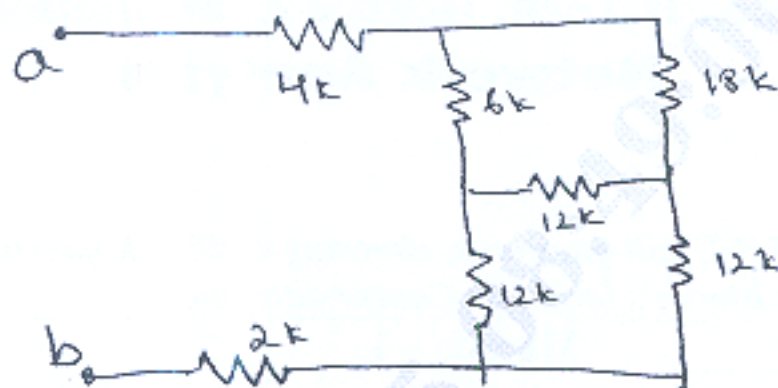


Fig.Q2(b)

Module – 2

- Q.3 a. Find the R_L for maximum power transfer and maximum power that can be transferred in the network shown in Fig.Q3(a).

10

L2
L3

CO2

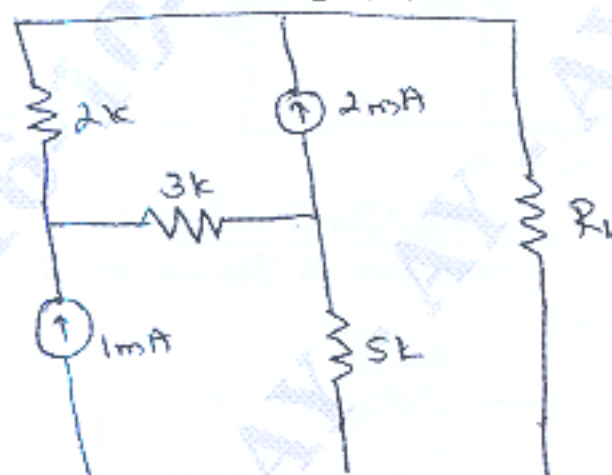


Fig.Q3(a)

- b. Find the current through $(10 - j3)\Omega$ using Millman's theorem. [Refer Fig.Q3(b)]

10

L2
L3

CO2

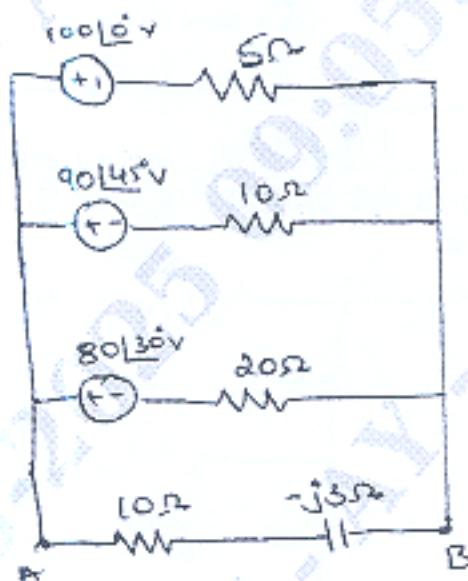


Fig.Q3(b)

OR

- Q.4 a. Obtain Thevenin's and Norton's equivalent circuit at the terminals AB for the network shown in Fig.Q4(a).

10

L2
L3

CO2

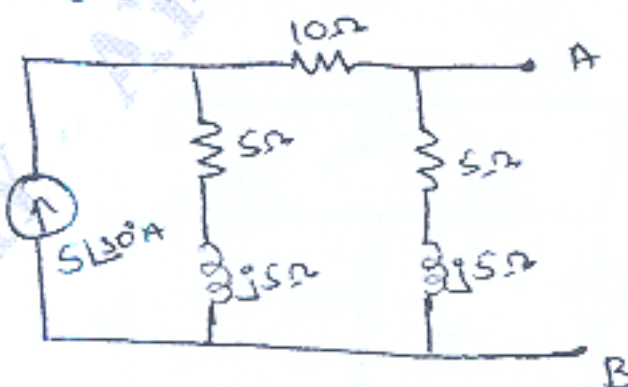


Fig.Q4(a)

- b. Find the value of R_L in the network shown in Fig.Q4(b) that will achieve max power transfer and determine the value of the maximum power.

10

L2
L3

CO2

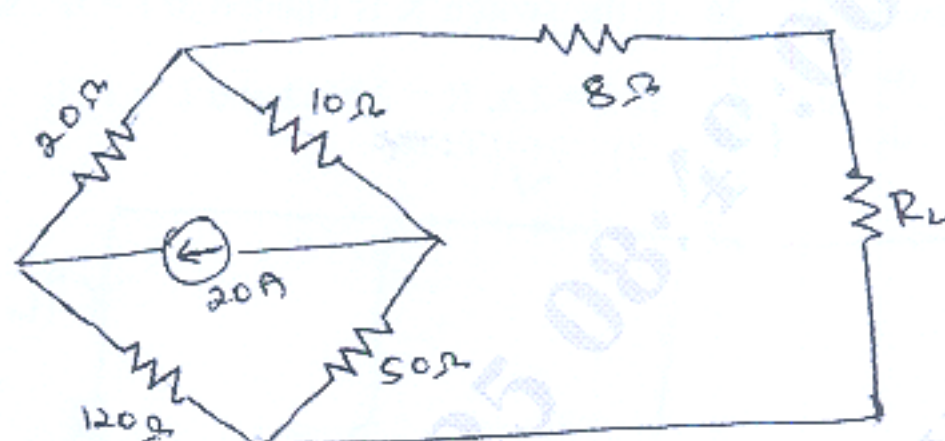


Fig.Q4(b)

Module – 3

- Q.5 a. In the network of Fig.Q5(a) the switch is moved from position (1) to position (2) at $t = 0$. The steady state having reached before switching. Calculate i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$

10

L2
L3

CO2

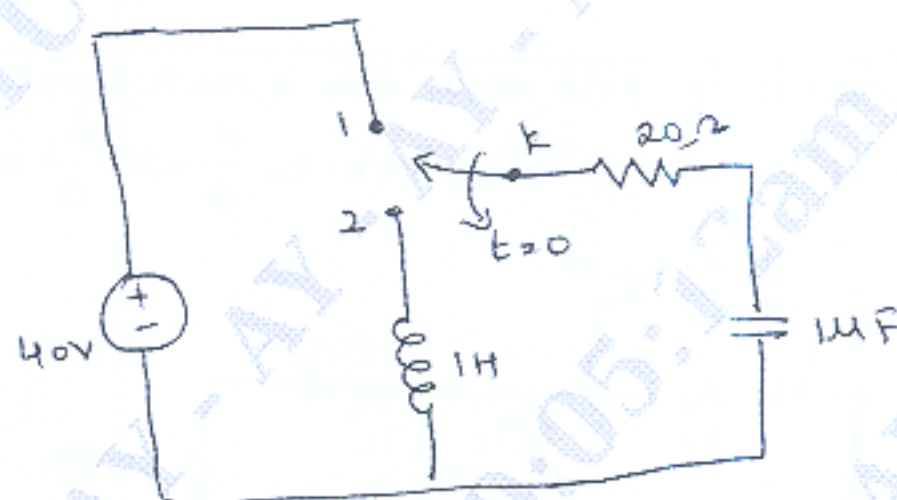


Fig.Q5(a)

- b. For the circuit shown in Fig.Q5(b) steady state is reached with switch K open. At $t = 0$, the switch is closed. Determine the values of $V_a(0^-)$ and $V_a(0^+)$.

10

L2
L3

CO2

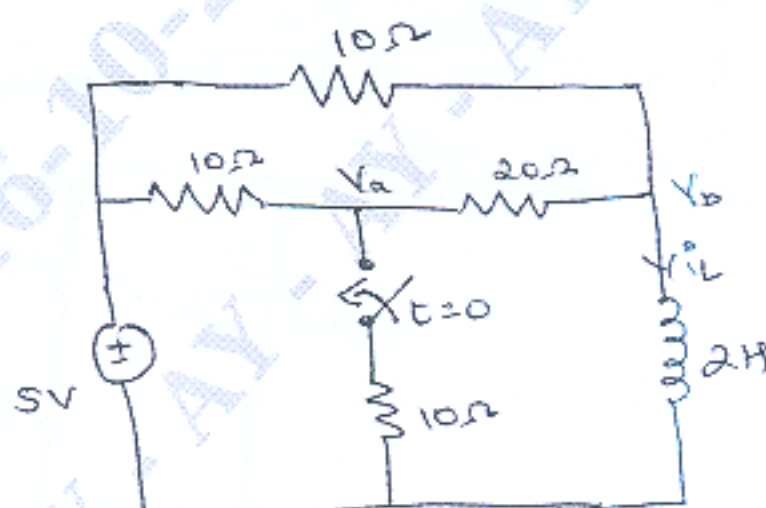
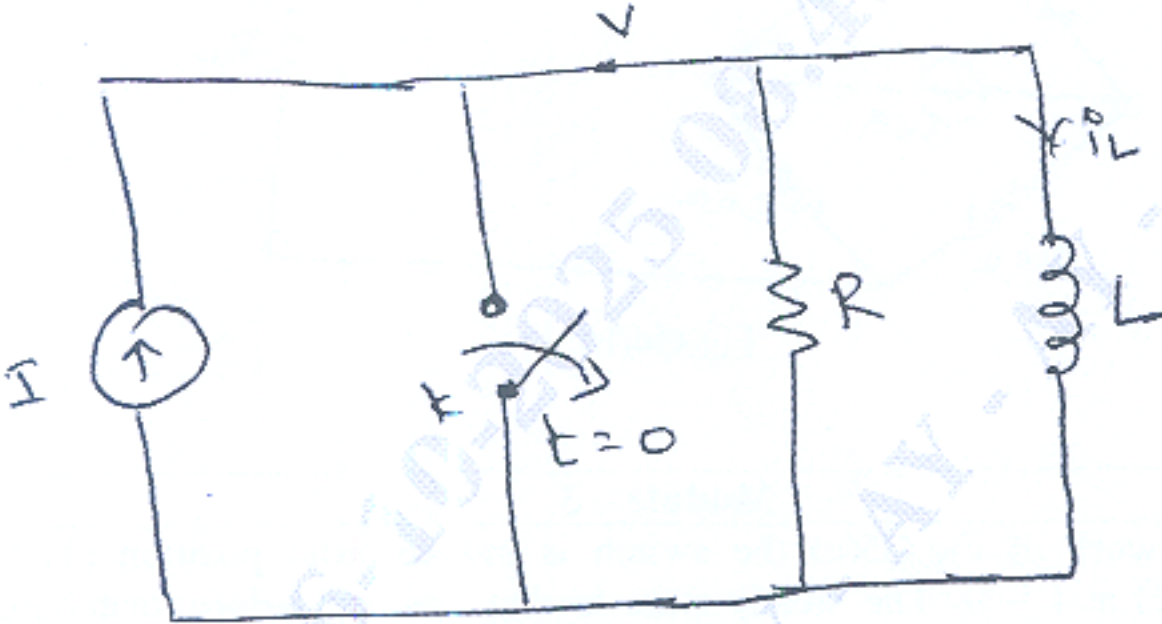
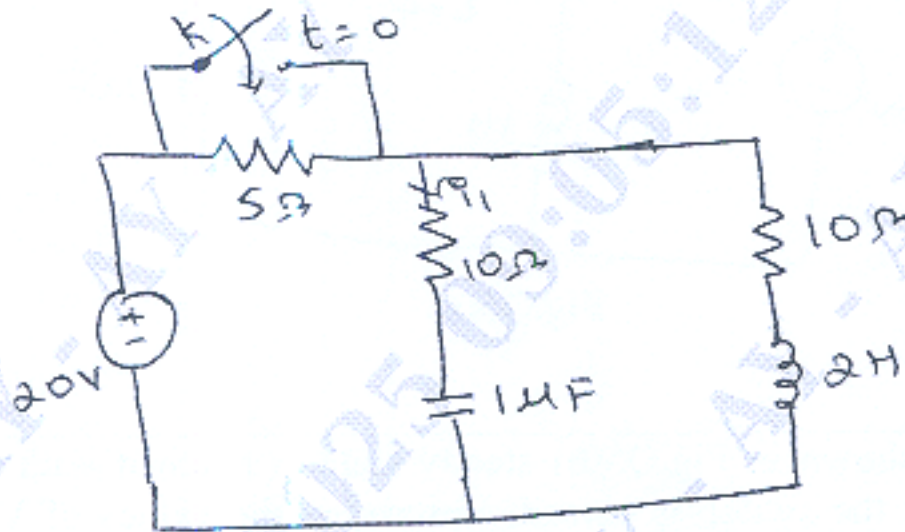
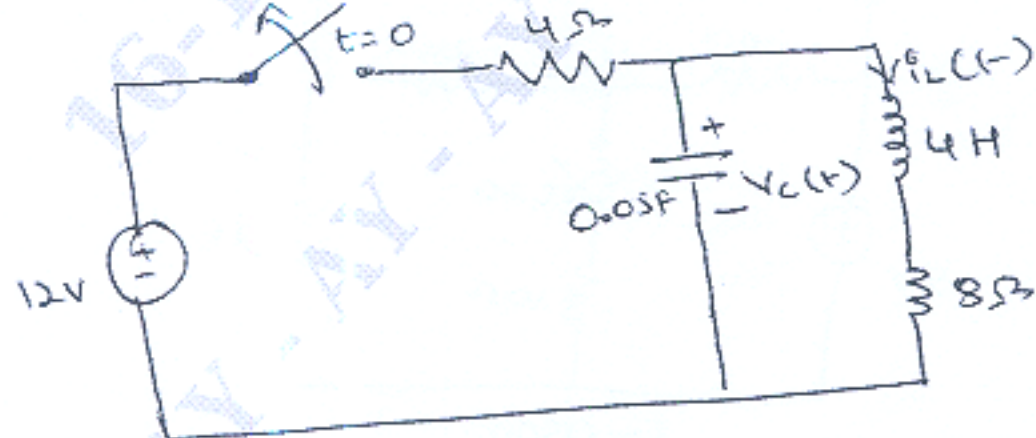


Fig.Q5(b)

OR

Q.6	a. In the given network Fig.Q6(a), the switch K is opened at $t = 0^+$, solve for the values of V, $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ if $I = 2A$, $R = 200\ \Omega$ and $L = 1\ H$.  Fig.Q6(a)	10	L2 L3	CO2
	b. In the circuit shown in Fig.Q6(b) steady state is reached with switch K open, the switch is closed at $t = 0$. Determine i_1, i_2, $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$ at $t = 0^+$.  Fig.Q6(b)	10	L2 L3	CO2
Q.7	a. Determine the current $i_L(t)$ for $t \geq 0$ for the circuit shown in Fig.Q7(a).  Fig.Q7(a)	10	L2 L3	CO3

- b. Refer the waveform shown in Fig.Q7(b). The equation for the waveform is $\sin t$ from 0 to π , $-\sin t$ from π to 2π . Show the Laplace transform of this waveform is $F(s) = \frac{1}{s^2 + 1} \coth\left(\frac{\pi s}{2}\right)$

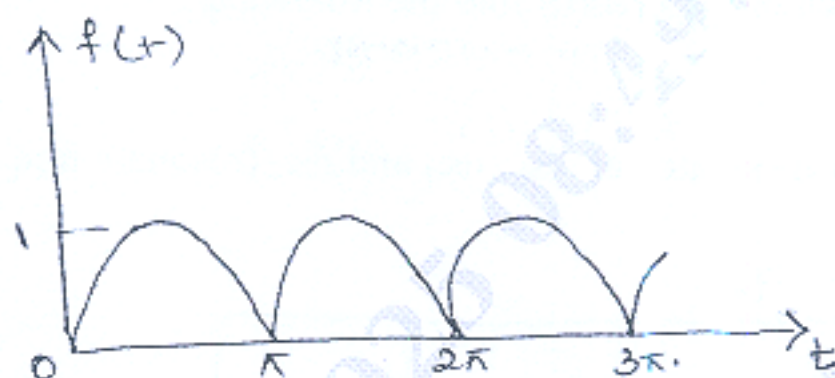


Fig.Q7(b)

OR

- Q.8 a. Determine the voltage $V_c(t)$ and the current $i_c(t)$ for $t \geq 0$ for the circuit shown in Fig.Q8(a).

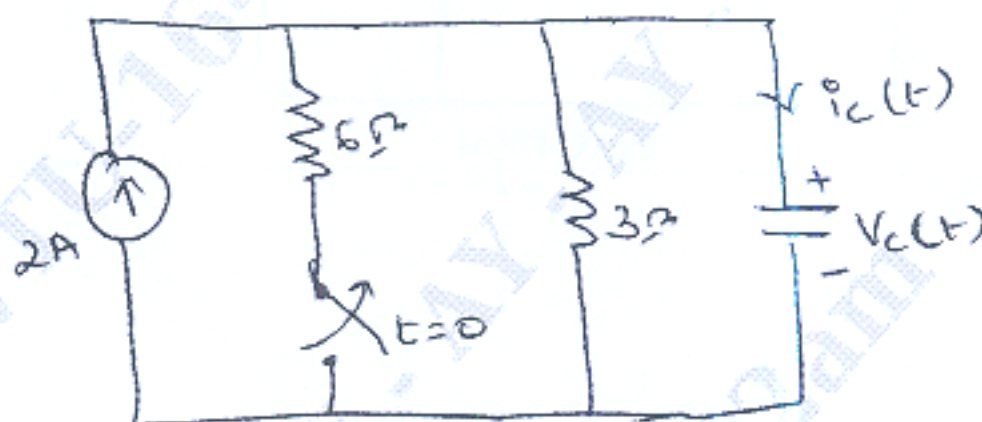


Fig.Q8(a)

- b. Express the function shown in Fig.Q8(b) using singularity function and then find $F(s)$.

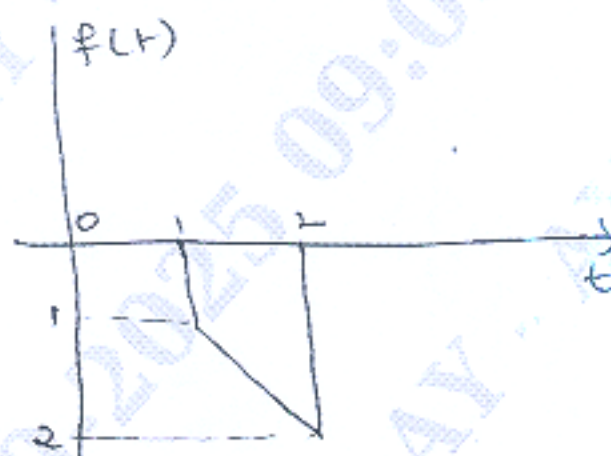


Fig.Q8(b)

Module – 5

- Q.9 a. Obtain Y parameters in terms of Z parameters and h-parameters.

- b. Determine the transmission parameters for the circuit shown in Fig.Q9(b).

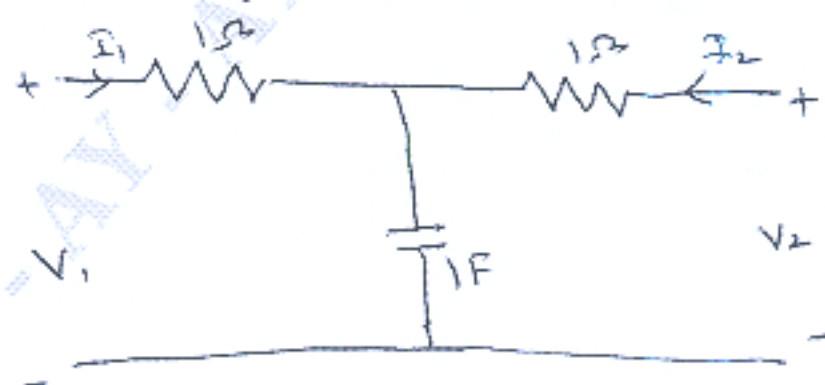
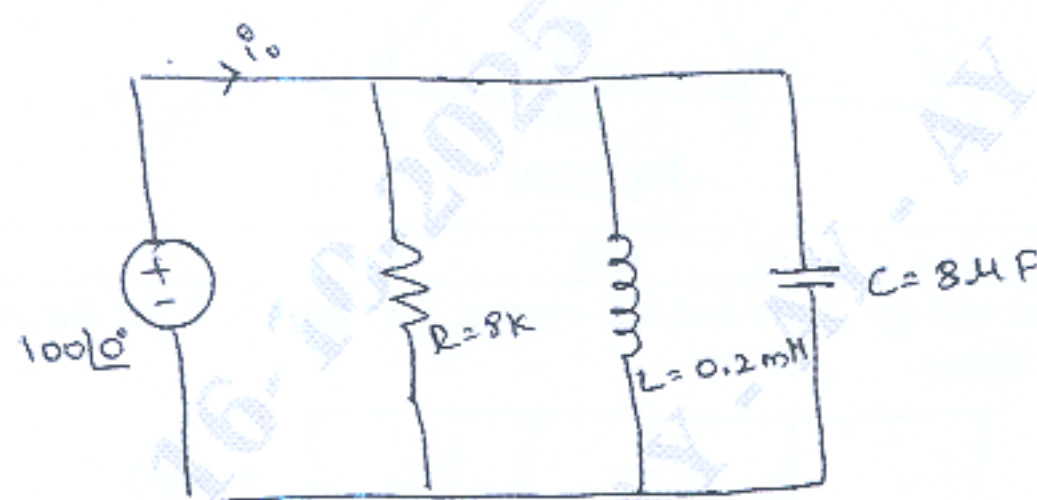


Fig.Q9(b)

OR

Q.10	a.	Derive an expression of Bandwidth, half power frequencies and quality factor of a series resonance circuit.	10	L1 L2	CO5
	b.	For the circuit shown in Fig.Q10(b) find the following : i) ω_0, Q, B ii) ω_1 and ω_2 iii) The max power dissipated at ω_0, ω_{c1} and ω_{c2} (resonate freq and cutoff freq.)  Fig.Q10(b) *****	10	L2 L3	CO5