



Sixth Semester B.E. Degree Examination, June/July 2025 Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define Power Electronics. List the applications of power electronics. (10 Marks)
b. Explain various types of power electronics converter circuits with the help of circuits and waveforms. (10 Marks)

OR

- 2 a. Write the symbol and control characteristics of the following devices:
i) SCR
ii) BJT
iii) MOSFET
iv) IGBT
v) GTO (10 Marks)
b. Explain the isolation of gate drive using
i) Pulse transformer
ii) Optocoupler. (10 Marks)

Module-2

- 3 a. Explain RC full wave triggering with neat circuit diagram. (10 Marks)
b. Explain two transistor model of SCR. (10 Marks)

OR

- 4 a. Define Commutation. Explain with neat circuit diagram and waveforms natural commutation. (10 Marks)
b. Define Forced Commutation. Explain class B commutation or resonant pulse commutation with neat circuit diagram. (10 Marks)

Module-3

- 5 a. What is AC voltage controller? Explain the principle of ON-OFF control with neat circuit diagram and waveforms. (10 Marks)
b. Explain the operation of single phase bidirectional AC voltage controller with resistive load with circuit diagram and waveforms. (10 Marks)

OR

- 6 a. Explain the principle of phase controlled converter operation with circuit diagram and waveforms. (10 Marks)
b. Explain Single Phase Semi-converter with circuit diagram and waveforms. (10 Marks)

Module-4

- 7 a. Explain the principle of step down chopper with neat circuit diagram and waveforms. (10 Marks)
b. Explain class D chopper operation with neat circuit diagram. (10 Marks)

OR

- 8 a. Explain the principle of step up clopper with neat circuit diagram and waveforms. (10 Marks)
b. Explain the operation of class B chopper with neat circuit diagram. (10 Marks)

Module-5

- 9 a. What is Inverter? Explain performance parameters of inverters. (10 Marks)
b. Explain principle of operation of inverters with neat circuit diagram and waveforms. (10 Marks)

OR

- 10 a. Explain single phase bridge inverter with neat circuit diagram and waveforms. (10 Marks)
b. Explain the following two types of voltage control in single phase inverters:
i) Single pulse width modulation
ii) Multiple pulse width modulation. (10 Marks)

* * * * *